

Unit III: Assessment: Assignments

Assignment Class 41

1. It is observed that second line voltage in a balanced star system is $200\sin(\omega t - 60^\circ)$ V. Express all the three phase voltages and all the three line voltages in both time form and phasor form.