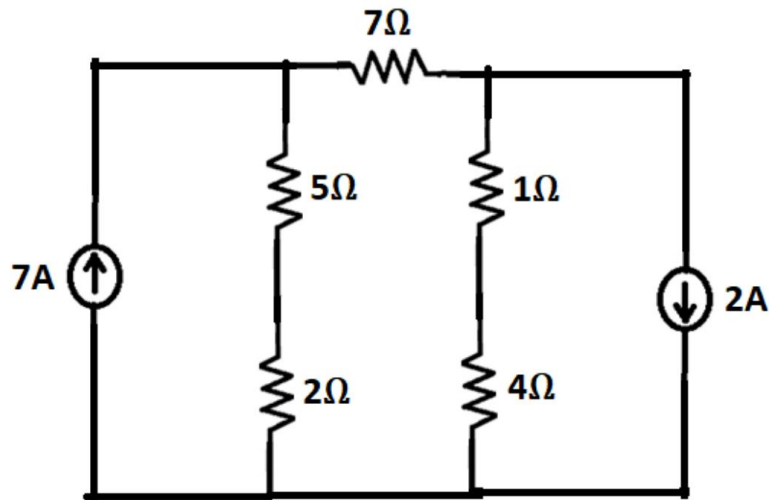


Unit I: Assessment Question Bank

Lecture 13

- Find the voltage across 7Ω resistor using Superposition Theorem.



- Find the voltage V_{AB} using Superposition Theorem.

