


Unit I: DC Circuits

NOTES – CLASS 3

Practical Voltage & Current Sources:

Practical Voltage Source:

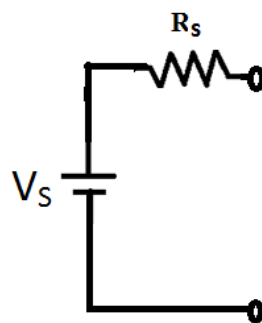In a practical voltage source, terminal voltage falls as load current increases. It is modelled as an ideal voltage source in series with internal resistance. A practical voltage source is represented as shown below:




Here, R_S represents its internal resistance.

Internal resistance of a practical voltage source is small, usually few $m\Omega$.

Internal resistance of an ideal voltage source is Zero.

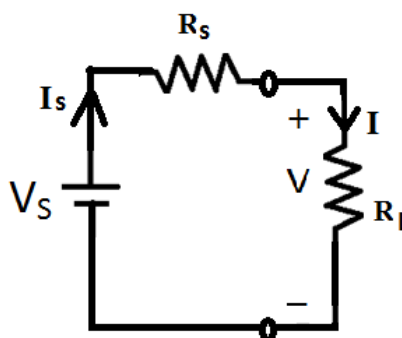
When terminated with a load resistance R_L , the terminal voltage is given by the following equation:



$$V = V_S - I \cdot R_S$$


Unit I: DC Circuits

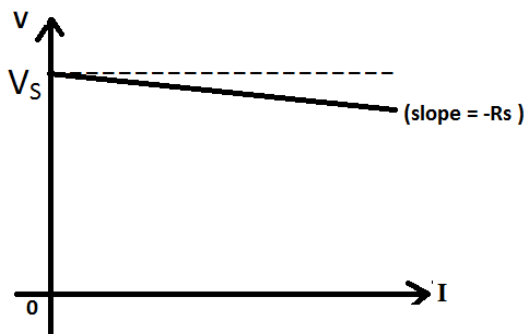It exhibits a terminal voltage current characteristic as shown below:



Practical Current Source:

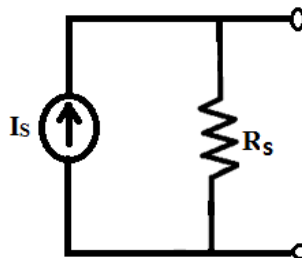In a practical current source, load current falls as terminal voltage increases. It is modelled as an ideal current source in parallel with internal resistance. A practical current source is represented as shown below:




Here, R_s represents its internal resistance.

Internal resistance of a practical current source is very high, usually few $M\Omega$.


When terminated with a load resistance R_L , the terminal current is given by the following equation:

Unit I: DC Circuits

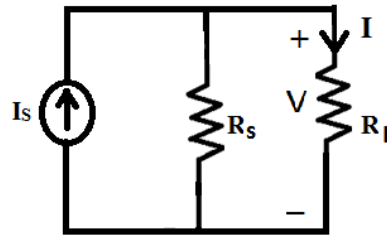

$$I = I_s - \left(\frac{V}{R_s}\right)$$

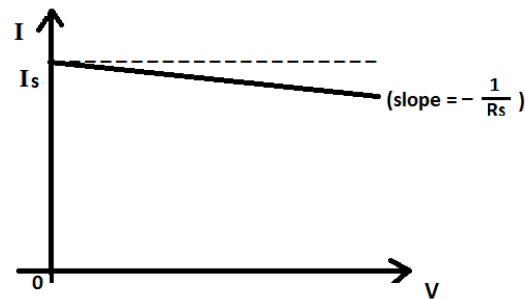
It exhibits a terminal voltage current characteristic as shown below:



Source Transformation:

Source Transformation is applicable to practical sources only.

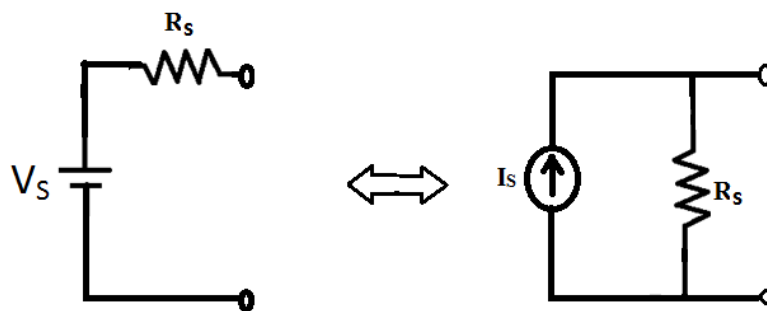A Practical Voltage Source can be transformed to a Practical Current Source & Vice versa by Source Transformation.




Here, V_s and I_s are related by, $V_s = I_s \cdot R_s$


Numerical Example on Source Transformation:

Unit I: DC Circuits

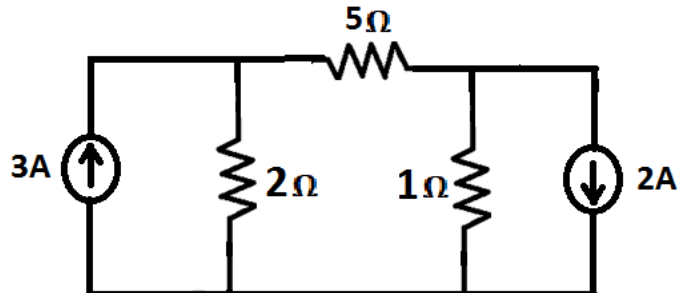Find the current through 5Ω resistor in the network shown using source transformation.




Solution:

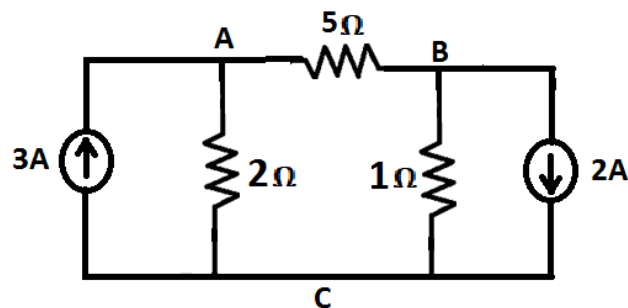


Replace 3A current source & 2Ω resistance with equivalent practical voltage source of EMF = $(3A \cdot 2\Omega) = 6V$ in series with 2Ω resistance.

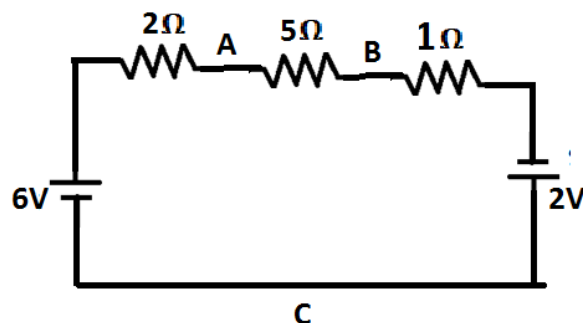Replace 2A current source & 1Ω resistance with equivalent practical voltage source of EMF = $(2A \cdot 1\Omega) = 2V$ in series with 1Ω resistance.



Consider a current I in this network.

Unit I: DC Circuits

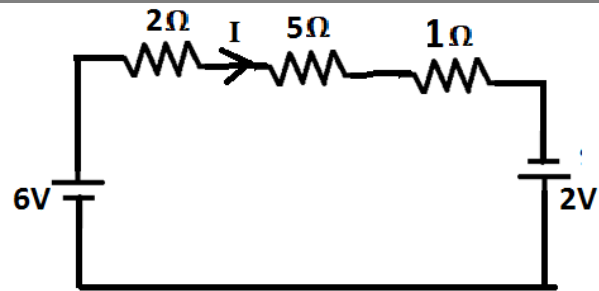

By applying KVL, $+6 - 2 \cdot I - 5 \cdot I - 1 \cdot I + 2 = 0$

$$I = 1\text{A}$$

Hence, current through 5Ω resistor is 1A.