



# ELEMENTS OF ELECTRICAL ENGINEERING

**Course Code : UE25EE141A/B**

---

## **FACULTY CONTRIBUTED:**

Department of EEE, RR Campus

Prof . Jyothi T N  
Prof. Vadhiraj K P P  
Prof. Kruthika N  
Prof. Suma S  
Prof. Pushpa K R  
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L  
Prof. Dhanashree G Bhate  
Dr. Renuka R Kajur  
Prof. Rajesh Chandrashekar  
Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)

---


## Numerical Examples on Series- Parallel AC Circuits

Jyothi T N

Department of Electrical & Electronics Engineering

## Numerical Example 1


### Question:

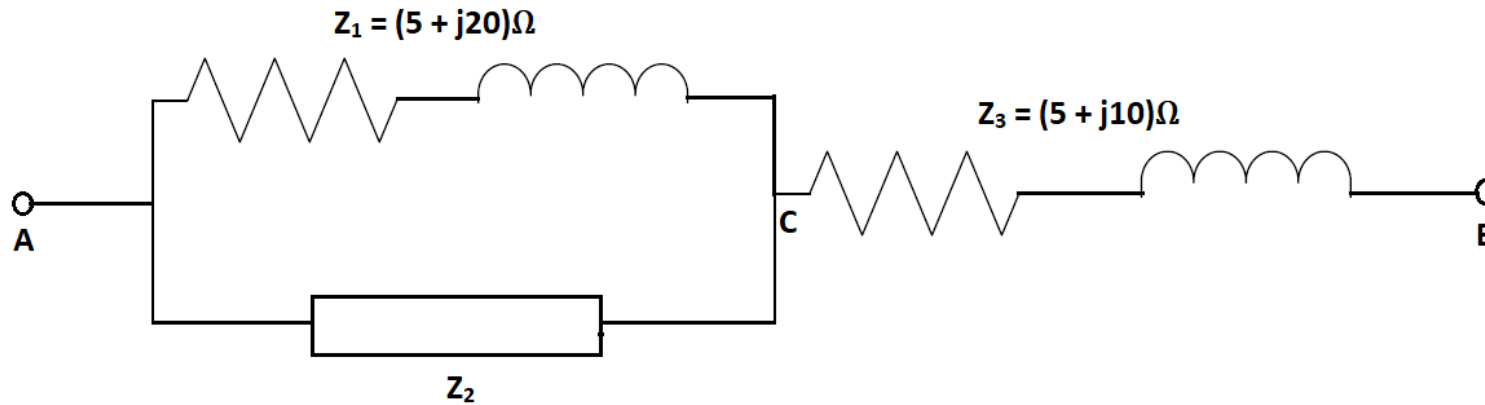

When a 220V AC supply is applied across terminals A & B of the circuit shown, the total power input is 3.25kW and the total current is 20A, lag. Find the complex expressions for currents through  $Z_1$  and  $Z_2$ , taking  $V_{AC}$  as reference phasor.

## Numerical Example 1

**Solution:**

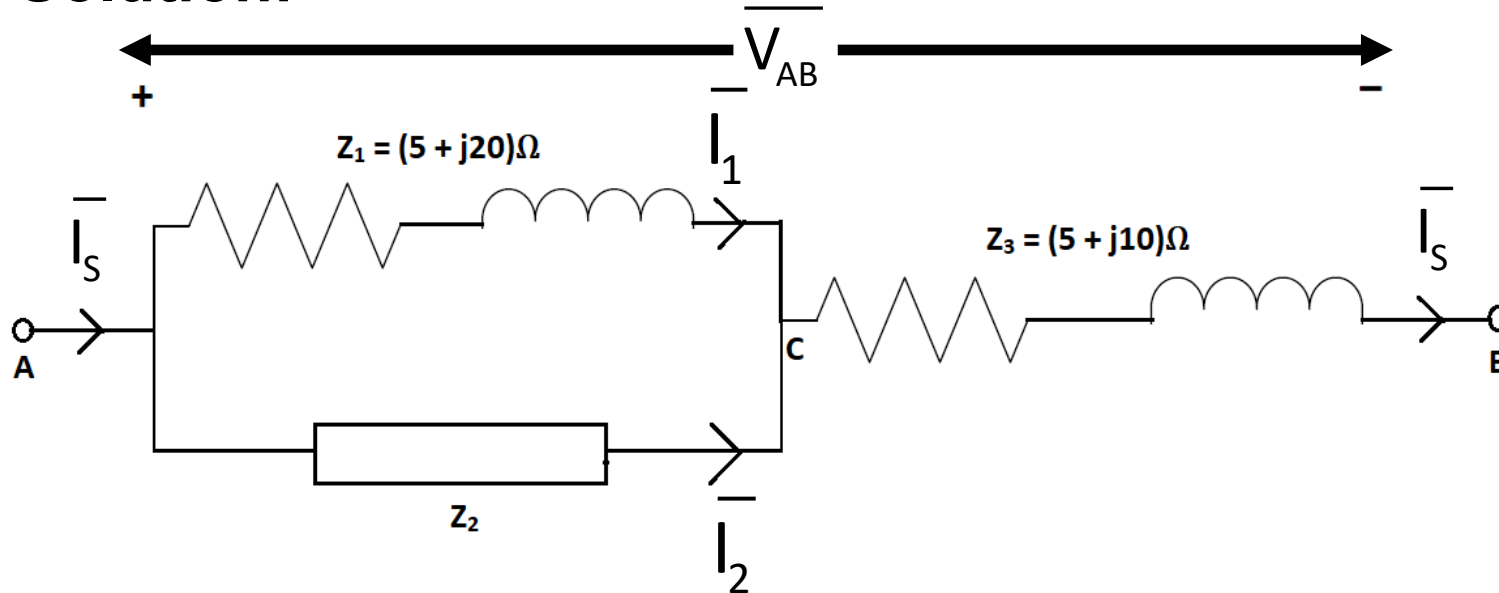

Considering supply voltage as reference,  $\overline{V}_{AB} = 220\angle 0^\circ \text{ V}$


Given, total power input = 3.25KW

$$\text{i.e., } \overline{V}_{AB} * I_S * \cos\phi = 3.25\text{KW} = 220 * 20 * \cos\phi$$

$$\Rightarrow \phi = 42.38^\circ$$

## Numerical Example 1

**Solution:**

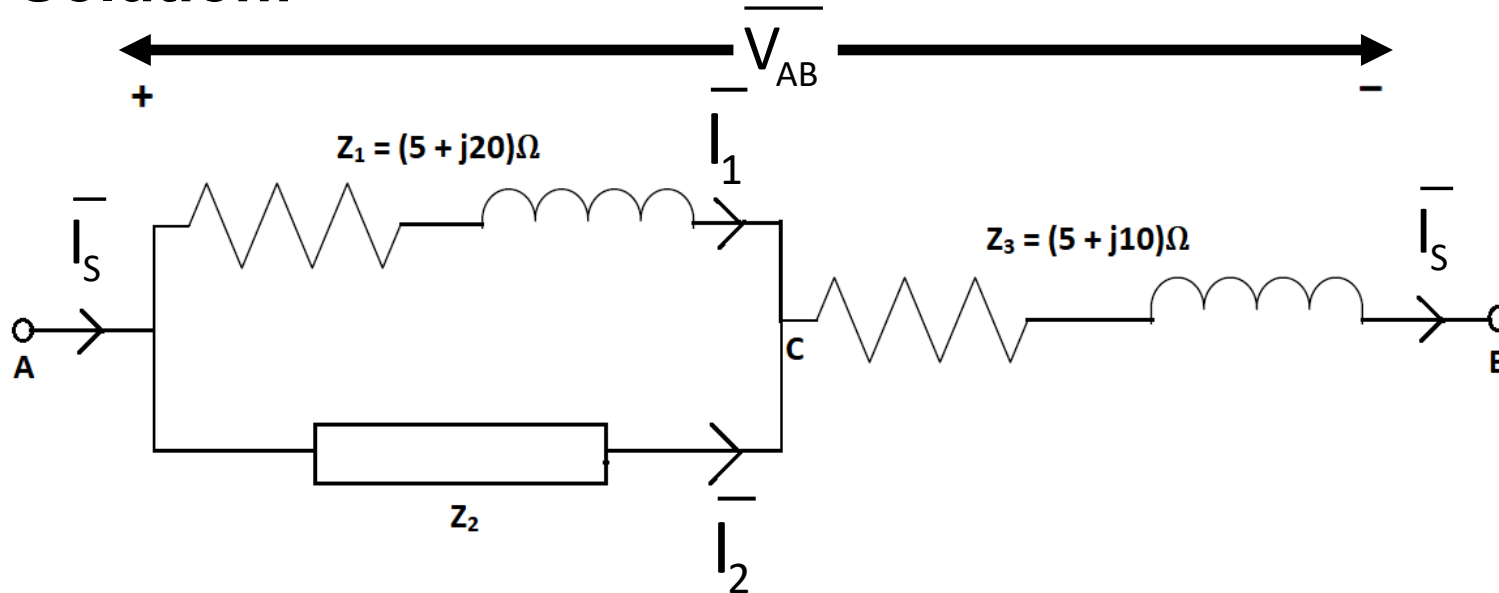

Since supply current is given as lag,  $\overline{I}_s = 20\angle -42.38^\circ \text{ A}$


$$\overline{V}_{CB} = \overline{I}_s * Z_3 = 223.61\angle 21.05^\circ \text{ V}$$

$$\overline{V}_{AC} = \overline{V}_{AB} - \overline{V}_{CB} = 81.11\angle -81.98^\circ \text{ V}$$

$$\overline{I}_1 = \frac{\overline{V}_{AC}}{Z_1} = 3.93\angle -157.95^\circ \text{ A}$$

## Numerical Example 1

**Solution:**

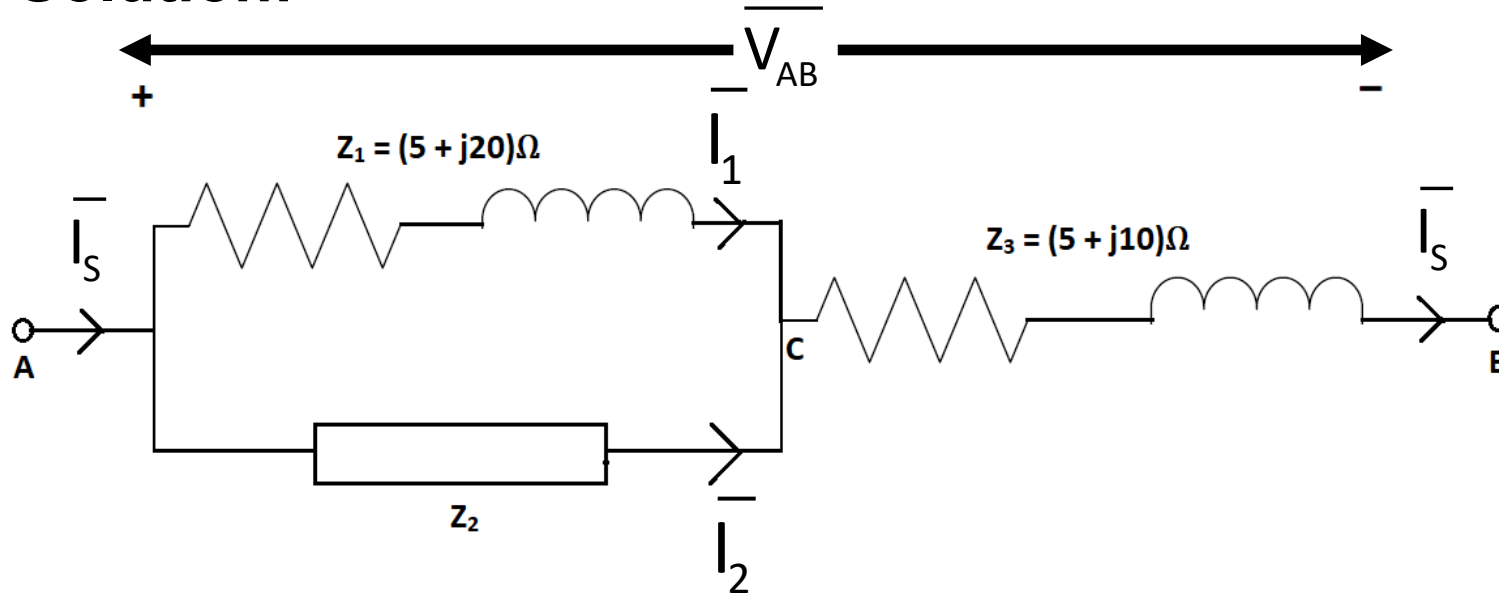

$$\bar{I}_2 = \bar{I}_s - \bar{I}_1 = 21.98 \angle -33.1^\circ \text{ A}$$

We found that  $\bar{V}_{AC} = 81.11 \angle -81.98^\circ \text{ V}$

To make  $\bar{V}_{AC}$  as reference, add  $81.98^\circ$  to its phase angle.

Also, Add the same angle to all other phasors.


Thus,  $\bar{I}_1 = 3.93 \angle -75.97^\circ \text{ A}$  ;  $\bar{I}_2 = 21.98 \angle 48.88^\circ \text{ A}$

### Question:

A voltage of 200 V is applied to a pure resistor (R), a pure capacitor, C and a lossy inductor coil with resistance of  $100\ \Omega$ , all of them connected in parallel. The total current is 2.45 A, while the component currents are 1.5, 2.0 and 1.2 A respectively. Find the total power factor and also the power factor of the coil. Also find the total active and reactive power.

## Numerical Example 2

**Solution:**

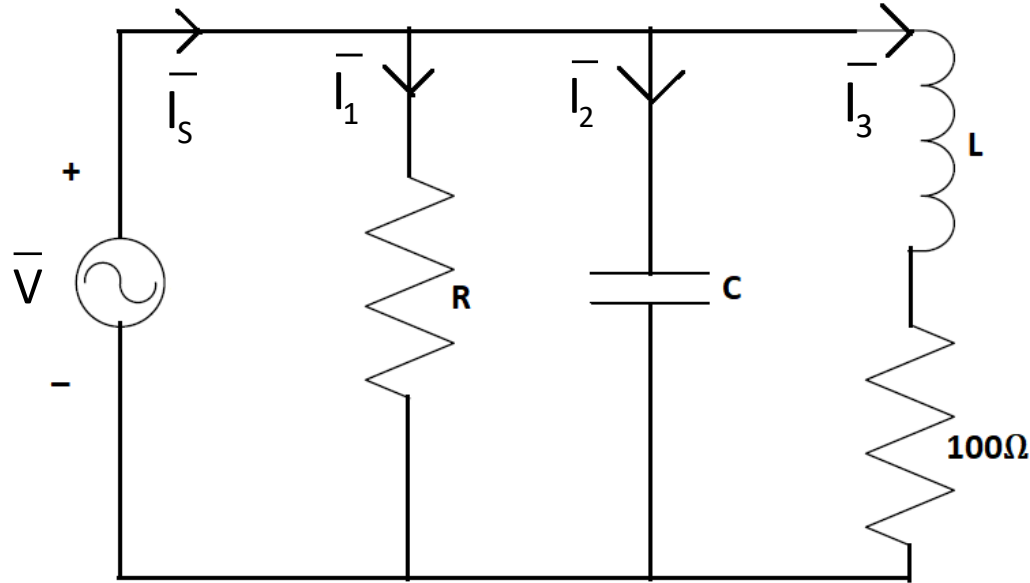

Let us consider supply voltage as reference

$$\Rightarrow \bar{V} = 200 \angle 0^\circ \text{ V}$$


Therefore  $\bar{I}_1 = 1.5 \angle 0^\circ \text{ A}$  ;  $\bar{I}_2 = 2 \angle 90^\circ \text{ A}$

$$\text{In branch 3, } |Z_3| = \frac{200}{1.2} = 166.66\Omega$$



## Numerical Example 2

**Solution:**

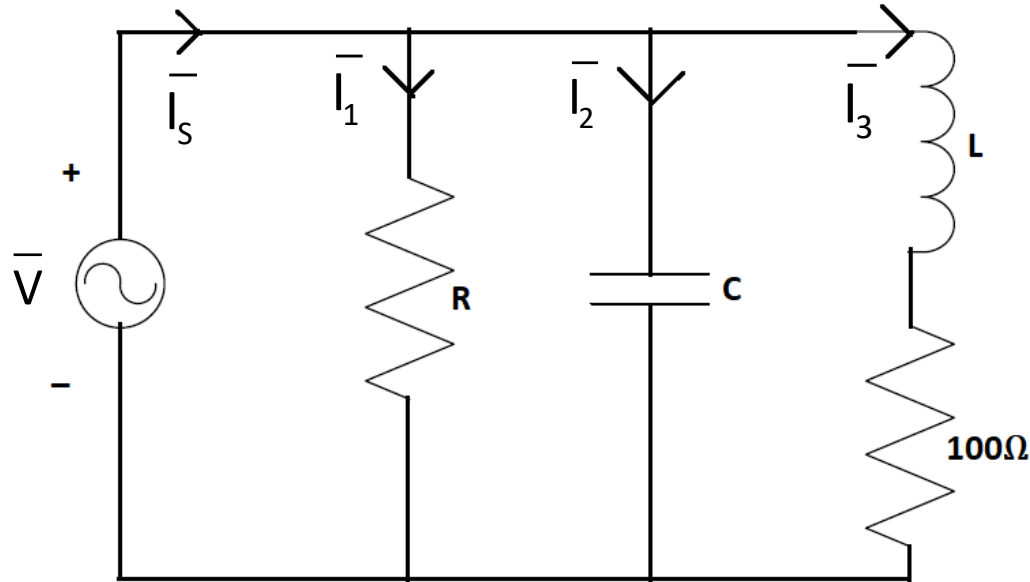

$$\text{Therefore, } \phi_3 = \cos^{-1}\left(\frac{r_3}{|Z_3|}\right) = 53.13^\circ \Rightarrow \bar{I}_3 = 1.2 \angle -53.13^\circ \text{ A}$$


$$\text{Hence, } \bar{I}_s = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 2.45 \angle 25.1^\circ \text{ A}$$

$$\text{Phase Angle of the network} = \phi = \angle \bar{V} - \angle \bar{I}_s = -25.1^\circ$$

$$\text{Overall Power factor} = \cos \phi = 0.905 \text{ Lead}$$

## Numerical Example 2

**Solution:**

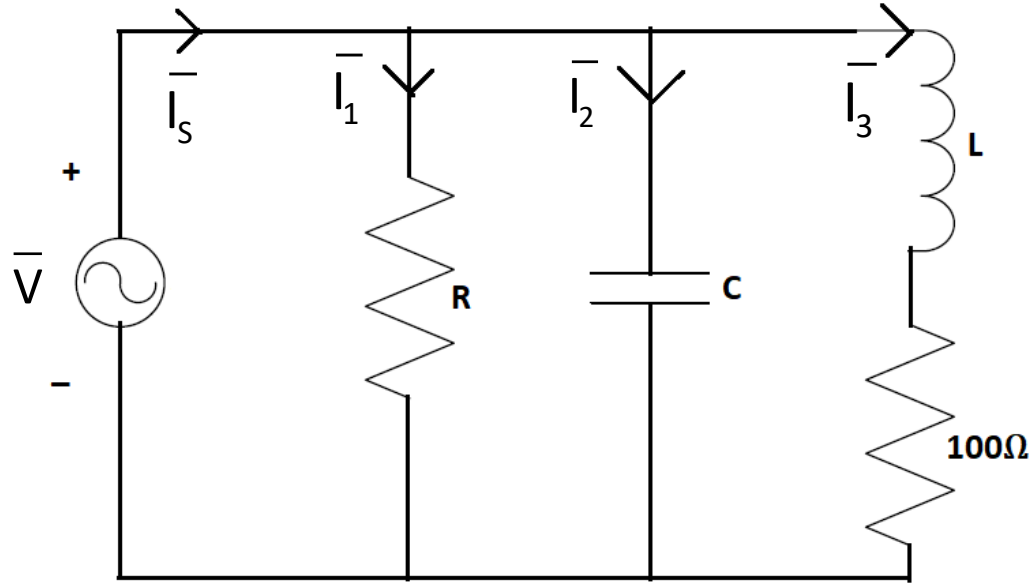

Power factor of the coil =  $\cos\phi_3 = 0.6$  Lag

Total Active Power,  $P_T = V \cdot I_S \cdot \cos\phi = 443.45\text{W}$

Total Reactive Power,  $Q_T = V \cdot I_S \cdot \sin\phi = -207.85 \text{ VAR}$

### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



# THANK YOU

---

**Jyothi T.N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**