

Unit I: Assessment: Assignments

Assignment – Lecture 1

1. In the network shown in figure below, calculate
- the unknown currents
 - the value of the unknown resistance X
 - the equivalent resistance between the points A and B

