

### Unit III : Assessment Question Bank

#### Lecture 44

1. A balanced 3 $\phi$  star connected load is supplied from a symmetrical 3 $\phi$  400V system. The current in each phase is 30A and lags by 30° behind the voltage.

Find

i) Impedance in each phase

ii) total power drawn.

Draw phasor diagram.

2.

A 415V, 50 Hz, three phase voltage is applied to three star-connected identical impedances. Each impedance consists of a resistance of 15 $\Omega$ , a capacitance of 177 $\mu$ F and an inductor of 0.1H in series. Find the

- Power factor (ANS: 0.744(lag))
- Phase current (ANS: 11.9A)
- Line current (ANS: 11.9A)
- Active power (ANS: 6.36kW)
- Reactive power (ANS: 5.71kVAR)
- Total VA (ANS: 8.55kVA)