

## Unit I: Assessment: Assignments

### Assignment – Lecture 2

1. Find the current through  $500\Omega$  resistor in the given network.

