

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H


ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)

Analysis of Parallel RLC circuit

Jyothi T N

Department of Electrical & Electronics Engineering

Parallel RLC Circuit

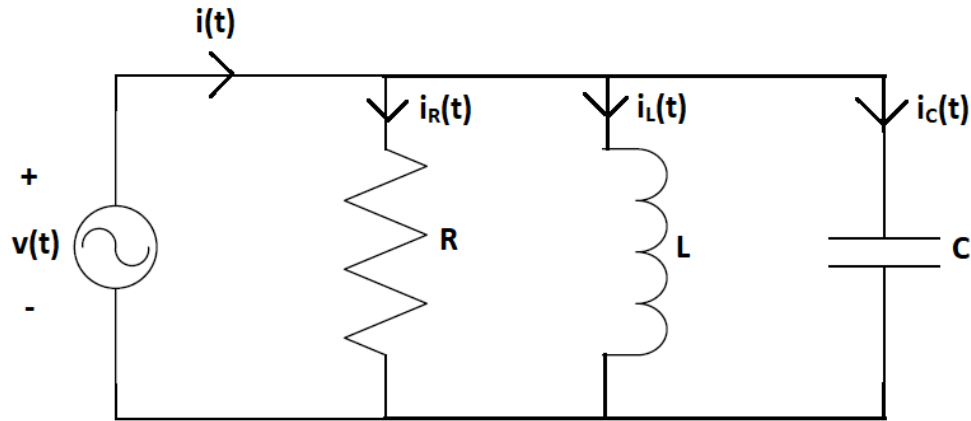

By KCL, $i(t) = i_R(t) + i_L(t) + i_C(t)$

In Phasor form, $\bar{i} = \bar{i}_R + \bar{i}_L + \bar{i}_C$

$$\bar{i}_R = \bar{V} * G \quad \bar{i}_L = \bar{V} * (-jB_L) \quad \bar{i}_C = \bar{V} * (jB_C)$$

$$\bar{i} = \bar{V} * (G - jB_L + jB_C)$$

$$Y_T = \frac{\bar{i}}{\bar{V}} = (G - jB_L + jB_C) = \sqrt{G^2 + (B_L - B_C)^2} \angle \tan^{-1}\left(\frac{B_C - B_L}{G}\right)$$


Case 1: $B_L > B_C$

If $B_L > B_C$ then $VB_L > VB_C$

i.e., $|\bar{I}_L| > |\bar{I}_C|$

The circuit behaves effectively as inductive circuit i.e., parallel RL type.

Phasor Diagram:

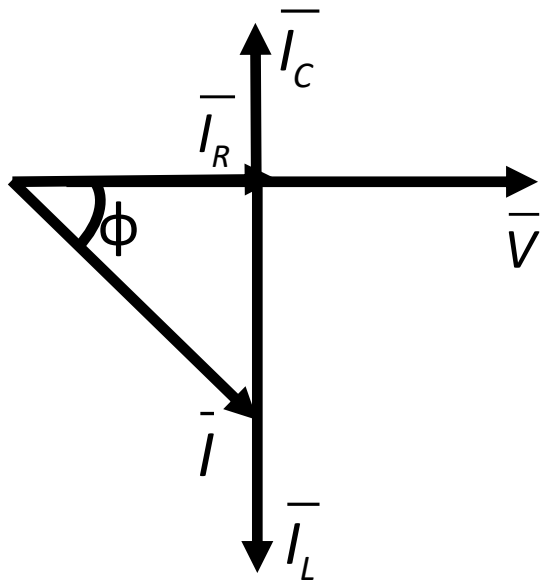

$$= \tan^{-1}\left(\frac{B_L - B_C}{G}\right)$$


Case 2: $B_C > B_L$

If $B_C > B_L$ then $VB_C > VB_L$

i.e., $|\bar{I}_C| > |\bar{I}_L|$

The circuit behaves effectively as a capacitive circuit i.e., parallel RC type.

Phasor Diagram:

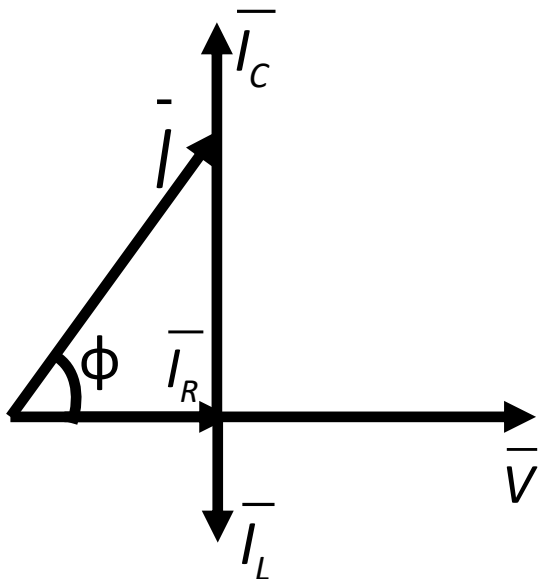

$$= \tan^{-1}\left(\frac{B_L - B_C}{G}\right)$$


Note: ϕ will be negative in this case since $B_L < B_C$

Case 3: $B_L = B_C$

If $B_L = B_C$ then $VB_L = VB_C$ i.e., $|\bar{I}_L| = |\bar{I}_C|$

The circuit behaves effectively as a purely resistive circuit. This case is called '**Parallel Resonance**' case.

Phasor Diagram:

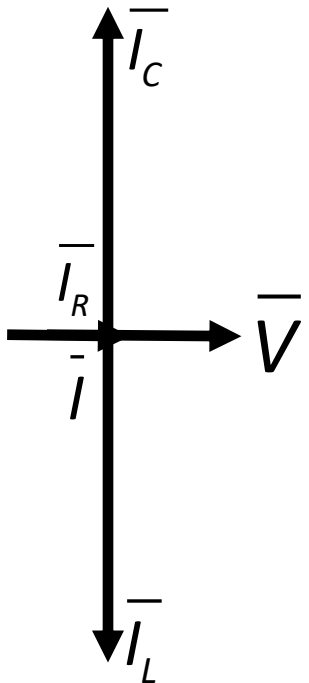

$$\bar{I} = \bar{I}_R$$

$$Y = G$$

$$\phi = 0^\circ$$

Numerical Example


Question:

Three circuit elements $R=2.5\Omega$, $X_L=4\Omega$ and $X_C=10\Omega$ are connected in parallel, the reactances being at 50Hz.

- a) Determine the admittance of each element and hence obtain the input admittance.
- b) If this circuit is connected across a 10V, 50Hz AC source, determine the current in each branch and the total input current.

Numerical Example

Solution:

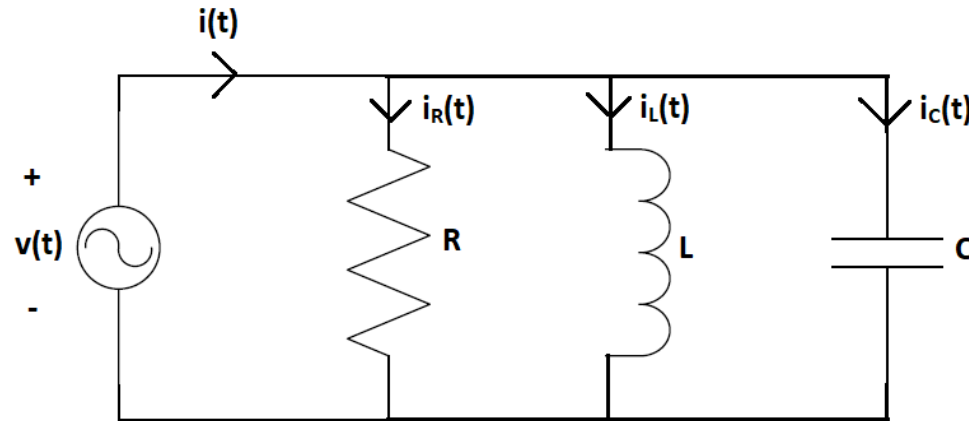

i) Admittance of branch1, $Y_1 = \frac{1}{Z_1} = \frac{1}{R} = G = 0.4S$


Admittance of branch2, $Y_2 = \frac{1}{Z_2} = \frac{1}{jX_L} = -jB_L = -j0.25S$

Admittance of branch3, $Y_3 = \frac{1}{Z_3} = \frac{1}{-jX_C} = jB_C = j0.1S$

Input Admittance $Y_{in} = Y_T = Y_1 + Y_2 + Y_3 = (0.4 - j0.15)S$

Numerical Example

Solution (Continued..) :

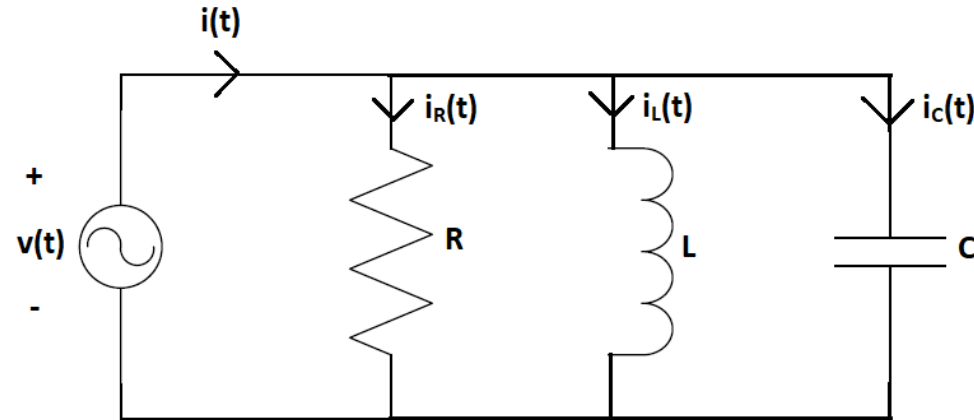

ii) Taking supply voltage as reference, $\bar{V} = 10\angle 0^\circ \text{V}$

current in branch 1, $\bar{I}_R = \frac{\bar{V}}{Z_1} = \bar{V}Y_1 = 10\angle 0^\circ * 0.4 = 4\angle 0^\circ \text{A}$

current in branch 2, $\bar{I}_L = \bar{V}Y_2 = 10\angle 0^\circ * (-j0.25) = 2.5\angle -90^\circ \text{A}$

current in branch 3, $\bar{I}_C = \bar{V}Y_3 = 1\angle 90^\circ \text{A}$

Input current, $\bar{I}_S = \bar{I}_R + \bar{I}_L + \bar{I}_C = 4.27\angle -20.55^\circ \text{A}$

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T.N

Department of Electrical & Electronics Engineering
jyothitn@pes.edu