

# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---



## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING

---



## Variation in Wattmeter readings with power factor of the load

**Jyothi T.N**

Department of Electrical & Electronics Engineering

For inductive loads,

$$W_1 = V_L * I_L * \cos(30 + \phi)$$

&

$$W_2 = V_L * I_L * \cos(30 - \phi)$$

As phase angle  $\phi$  increases, load power factor decreases.

With an increase in the phase angle  $\phi$ ,

$$W_1 = V_L * I_L * \cos(30 + \phi) \text{ decreases}$$

&


$$W_2 = V_L * I_L * \cos(30 - \phi) \text{ increases}$$

## Variation in wattmeter readings – Inductive load (contd..)

Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30+\phi)$	$W_2 = V_L I_L \cos(30-\phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3}V_L I_L}{2}$	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lag	$\frac{V_L I_L}{2}$	$V_L I_L$	$W_1 = \frac{W_2}{2}$
$60^\circ$	0.5 Lag	0	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = 0;$ $W_2 = P_{3\text{-phase}}$
$>60^\circ$	$< 0.5$ Lag	Negative	Positive	$W_1 = \text{-ve};$ $W_2 = \text{+ve}$
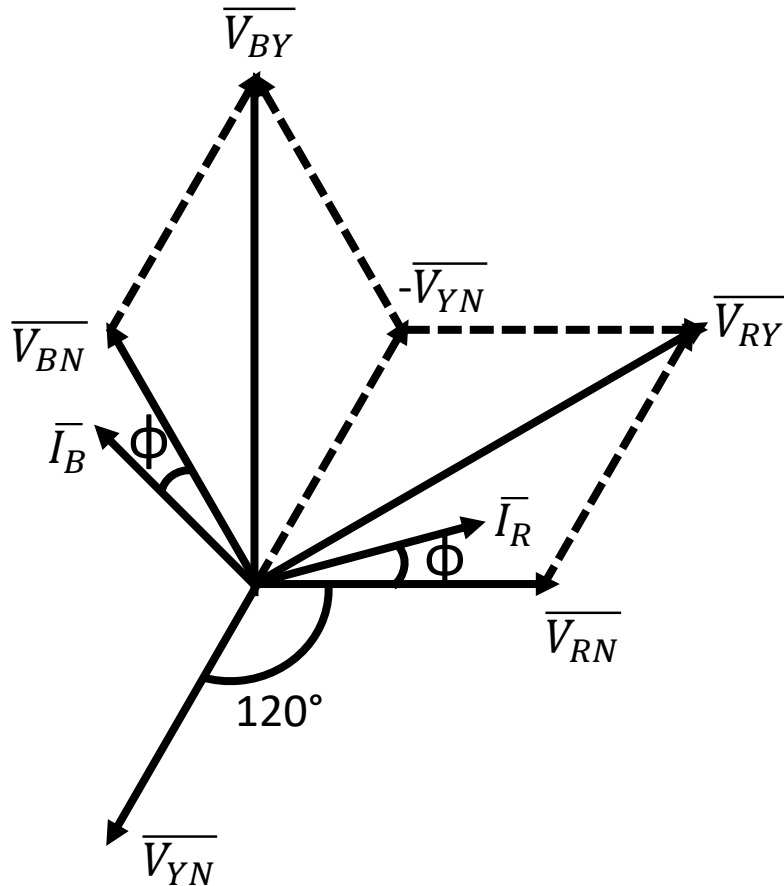
#### Important observations:

- When phase angle is  $<60^\circ$  (or) power factor of the load is  $> 0.5$  Lag, both the wattmeters read positive readings.
- When phase angle =  $60^\circ$  (or) power factor of the load is  $= 0.5$  Lag, one of the wattmeters reads zero and the other reads the total three phase active power.
- When phase angle is  $>60^\circ$  (or) power factor of the load is  $< 0.5$  Lag, one of the wattmeters reads negative i.e., its pointer moves behind zero. To record its reading, either reverse its CC connections or PC connections (not both) & record this value with a negative sign.



Consider capacitive load. Then, phase current leads phase voltage.

$$W_1 = V_{RY} * I_R * \cos(30 - \phi) \quad \& \quad W_2 = V_{BY} * I_B * \cos(30 + \phi)$$

# ELEMENTS OF ELECTRICAL ENGINEERING

## Variation in wattmeter readings – Capacitive load



Phase Angle, $\phi$	Load Power factor, $\cos\phi$	$W_1 = V_L I_L \cos(30-\phi)$	$W_2 = V_L I_L \cos(30+\phi)$	Comments
$0^\circ$	1	$\frac{\sqrt{3}V_L I_L}{2}$	$\frac{\sqrt{3}V_L I_L}{2}$	$W_1 = W_2$
$30^\circ$	0.866 Lead	$V_L I_L$	$\frac{V_L I_L}{2}$	$W_2 = \frac{W_1}{2}$
$60^\circ$	0.5 Lead	$\frac{\sqrt{3}V_L I_L}{2}$	0	$W_1 = P_{3\text{-phase}};$ $W_2 = 0$
$>60^\circ$	$< 0.5$ Lead	Positive	Negative	$W_1 = +ve;$ $W_2 = -ve$

### Question:

In a two wattmeter method of measuring three phase power, it is observed that the wattmeter readings are in the ratio of 3:1. Determine the power factor of the Load.

### Solution:

#### Given Data:

$$W_1 : W_2 = 3:1$$

$$\text{Power factor} = \cos\phi = \cos\left(\tan^{-1}\left(\sqrt{3} \cdot \frac{(W_1 - W_2)}{(W_1 + W_2)}\right)\right)$$

$$\text{Therefore, Power factor} = 0.756$$



### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**