

### Unit III : Assessment Question Bank

#### Lecture 46

1. With a neat circuit diagram and phasor diagram, show that two wattmeters are sufficient to measure active power in a three phase system. Also derive an expression for the powerfactor of the system.

PES University