

Unit III: Assessment Question Bank

Lecture 42

1. Derive the relation between Line and Phase currents in a balanced delta connected three phase system.
2. It is observed that second phase current in a balanced delta system is $10\sin(\omega t - 60^\circ)\text{A}$. Express all the three phase currents and all the three line currents in both time form and phasor form.

PES University