

Unit III : Assessment: Assignments

Assignment – Lecture 45

1.

When three identical coils are connected in delta across a 3 phase, 400 V ,50 Hz supply the line current is 27.72 A and the total power consumed is 15.36kW. Find the resistance and the inductance of the coils.