

## Unit III: Assessment Question Bank

### Lecture 43

1. Define the following
  - i) Balanced Star Load
  - ii) Balanced Delta Load
  
2. In a balanced delta connected three phase load, phase current is 10A and lags behind phase voltage 200V by  $60^\circ$ . Determine
  - i) Three Phase Active Power
  - ii) Three Phase Reactive Power
  - iii) Three Phase Apparent Power

PES University