



ELEMENTS OF ELECTRICAL ENGINEERING

Vadhiraj K P P

Department of Electrical Engineering

ELEMENTS OF ELECTRICAL ENGINEERING


POWER FACTOR IMPROVEMENT

Vadhiraj K P P

Department of Electrical & Electronics Engineering

ELEMENTS OF ELECTRICAL ENGINEERING

Power Factor

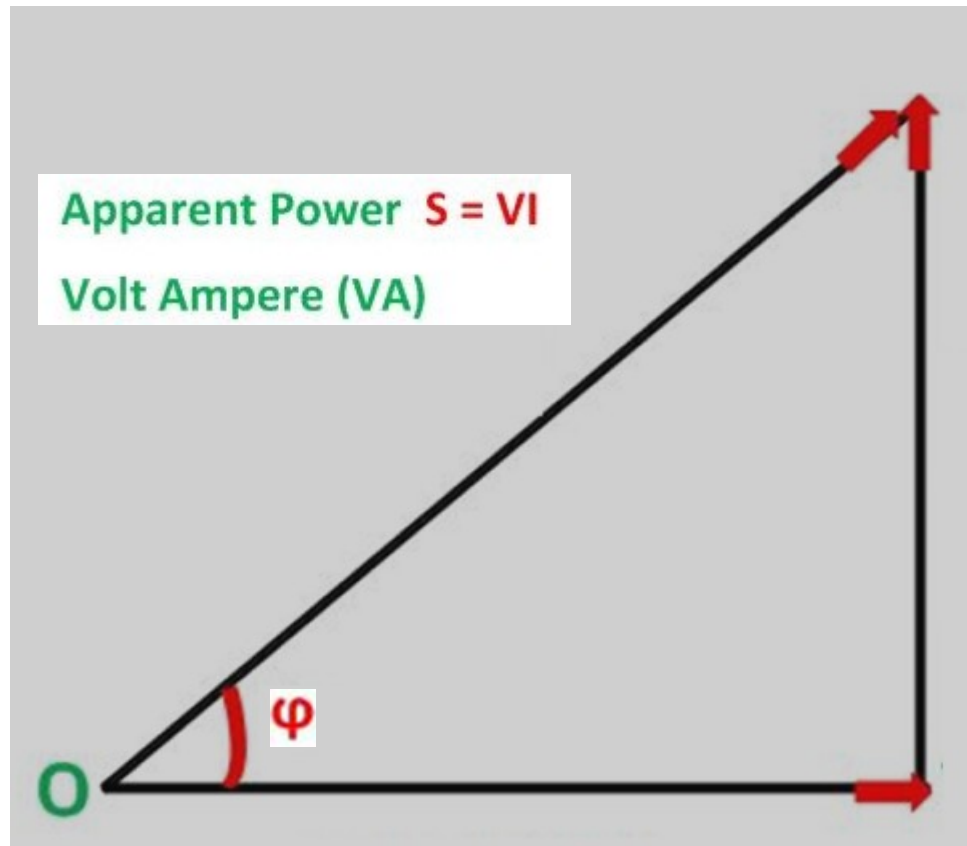

Apparent Power $S = VI$
Volt Ampere (VA)

Reactive Power $Q = VI \sin \phi$
Volt Ampere Reactive
(VAR)





True Power $P = VI \cos \phi$
Kilo watt(kW)

Power factor =

- Higher Reactive power flow in the system.
- I^2R Losses will be increased & hence lower efficiency.
- A Low Power Factor will lead to under utilisation of the installed capacity of the electrical systems.
- Leads to increase in the overall cost of the power system equipment.
- Inferior voltage profile at the load end.

ELEMENTS OF ELECTRICAL ENGINEERING

Power Factor Improvement

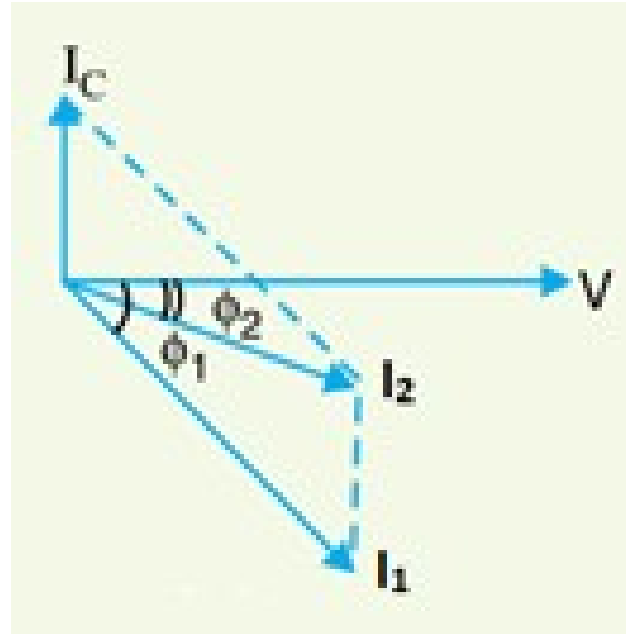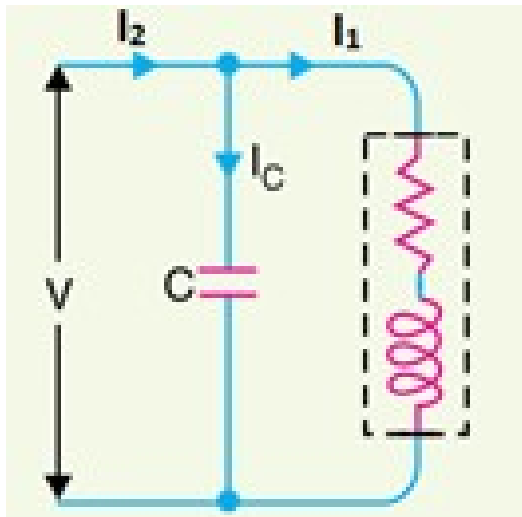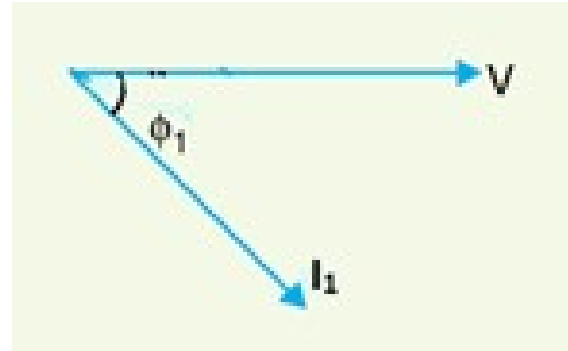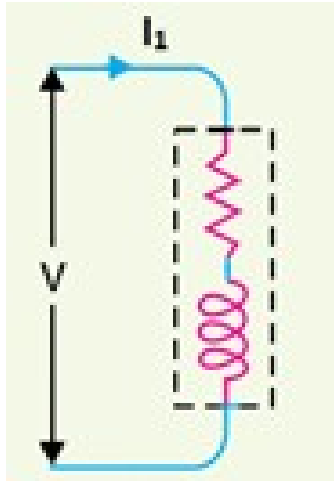


Question:

The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.

Numerical Example 1

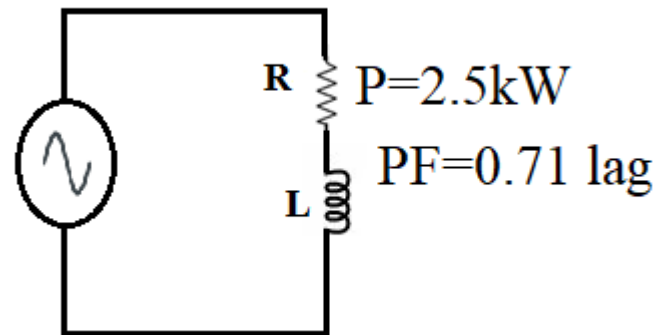Question:

The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.



ELEMENTS OF ELECTRICAL ENGINEERING

Numerical Example 1 (Solution contd..)



ELEMENTS OF ELECTRICAL ENGINEERING

Numerical Example 1 (Solution contd..)




Question:

The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.

Solution:
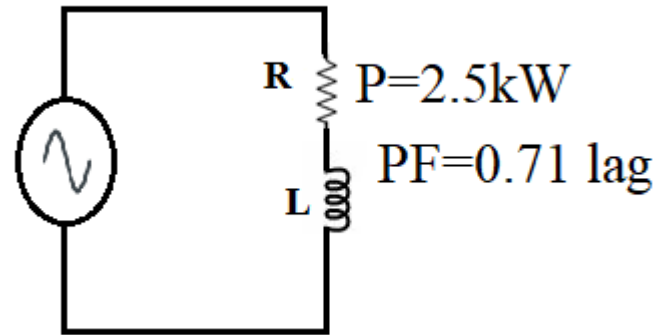
$$P = VI \cos \phi$$
$$I = 15.309 \text{ A}$$
$$\phi = \cos^{-1} 0.71 = 44.76^\circ$$
$$\therefore I = 15.309 \angle -44.76^\circ \text{ A}$$



ELEMENTS OF ELECTRICAL ENGINEERING

Numerical Example 1 (Alternative Solution)

By KCL

$$I_T \angle -30^\circ = (15.309 \angle -44.76^\circ) + (I_C \angle 90^\circ)$$

By equating real parts.

$$I_T \cos 30^\circ = (15.309 \cos 44.76^\circ) + (I_C \cos 90^\circ)$$


$$I_T = 12.55 \text{ A}$$

$$I_C = I_T - I_L$$

$$I_C = (12.55 \angle -30^\circ) - (15.309 \angle -44.76^\circ)$$

$$\therefore I_C = 4.504 \angle 90^\circ$$
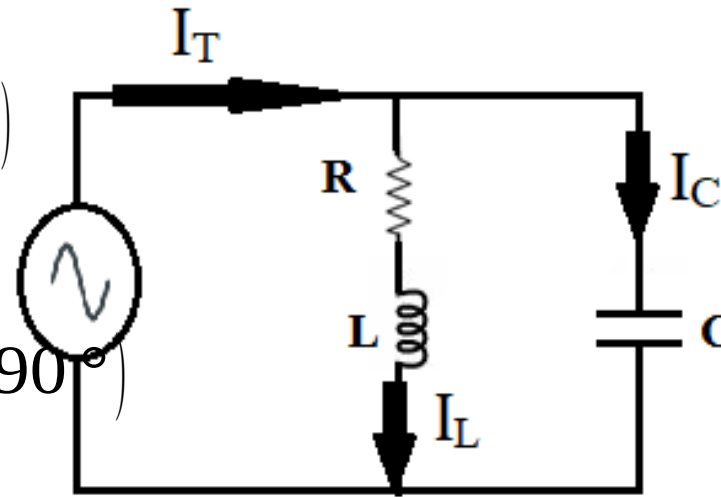
$$\therefore X_C = \frac{V_C}{I_C} = \frac{230}{4.504} = 51.065 \Omega = \frac{1}{2\pi f X_C} = 62.33 \mu f$$



Question:

The load connected across an AC supply consists of a heating load of 15KW, a motor load of 40KVA at 0.6 lag and a load of 20KW at 0.8 lag. Calculate the total power drawn from the supply in (KW and KVA) and its power factor. What would be the KVAR rating of a capacitor to bring the power factor to unity and how must the capacitor be connected?

Solution: Load 1: Heating Load

- $Q_1 = 0$

$$\text{so, } S_1 = \sqrt{P_1^2 + Q_1^2} = 15 \text{ kVA}$$

Load 2: Motor Load

$$P_2 = S_2 \cos \phi_2 = 24 \text{ kW}$$
$$Q_2 = S_2 \sin \phi_2 = 32 \text{ kVAR}$$

Load 3: Inductive Load

$$S_3 = 25 \text{ kVA}$$
$$Q_3 = S_3 \sin \phi_3 = 15 \text{ kVAR}$$

Numerical Example 2

$$P_T = P_1 + P_2 + P_3$$

$$\therefore P_T = 59 \text{ kW}$$

$$Q_T = Q_1 + Q_2 + Q_3$$

VAR

$$S_T = \sqrt{P_T^2 + Q_T^2}$$
$$= \sqrt{(59 \text{ k})^2 + (47 \text{ k})^2}$$

$$S_T = 75.43 \text{ kVA}$$

Overall Power Factor is

To bring the power Factor to Unity, must be 0.
Hence we need to connect a capacitor of 47kVAR rating in parallel with the circuit.