

# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---



## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraaj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar


Prof. Sangam Kumar G H

## Measurement of Power and Power factor using Two Wattmeter Method

**Jyothi T.N**

Department of Electrical & Electronics Engineering

- Wattmeter is a power measuring instrument.
- It consists of a fixed coil called 'Current Coil (CC)' and a moving coil called 'Pressure Coil' (PC). Pressure coil is also called 'Voltage coil' (VC).

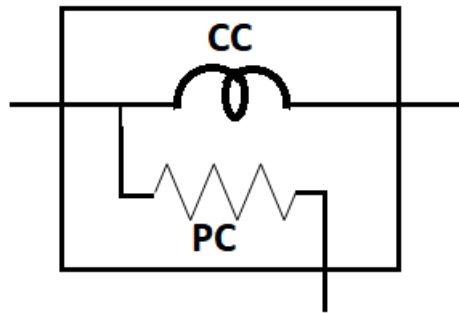

**Fig: Wattmeter symbol**

- PC carries the pointer of the instrument and indicates the average power.


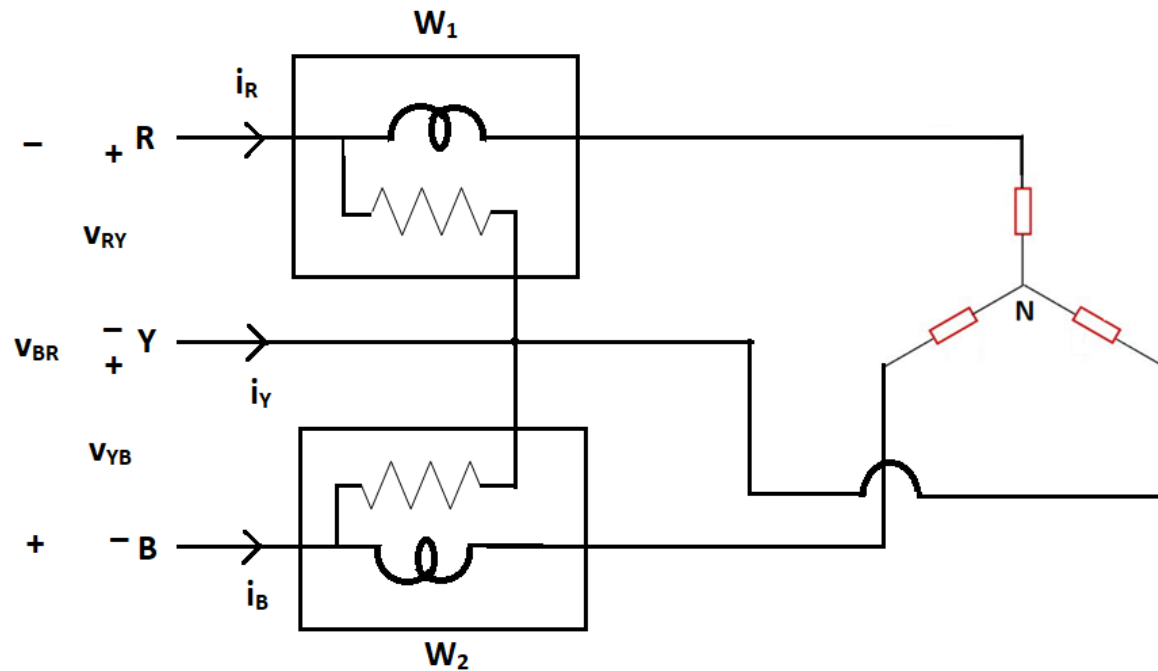



Fig: Two Wattmeter Method circuit diagram

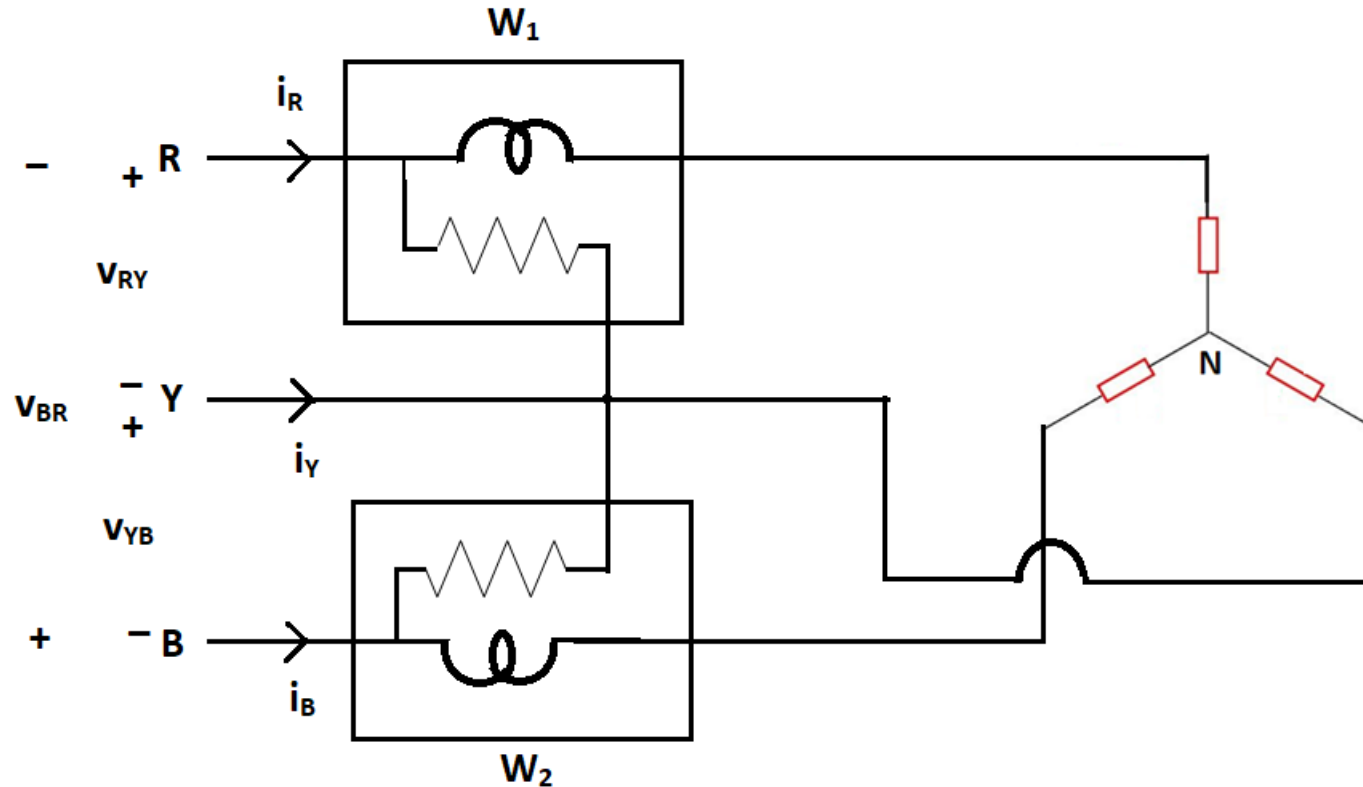Two wattmeters are sufficient to measure three phase active power irrespective of whether the load is star connected or delta connected and irrespective of whether the load is balanced or unbalanced.



$$W_1 = V_{RY} * I_R * \cos(\angle(V_{RY}, I_R))$$
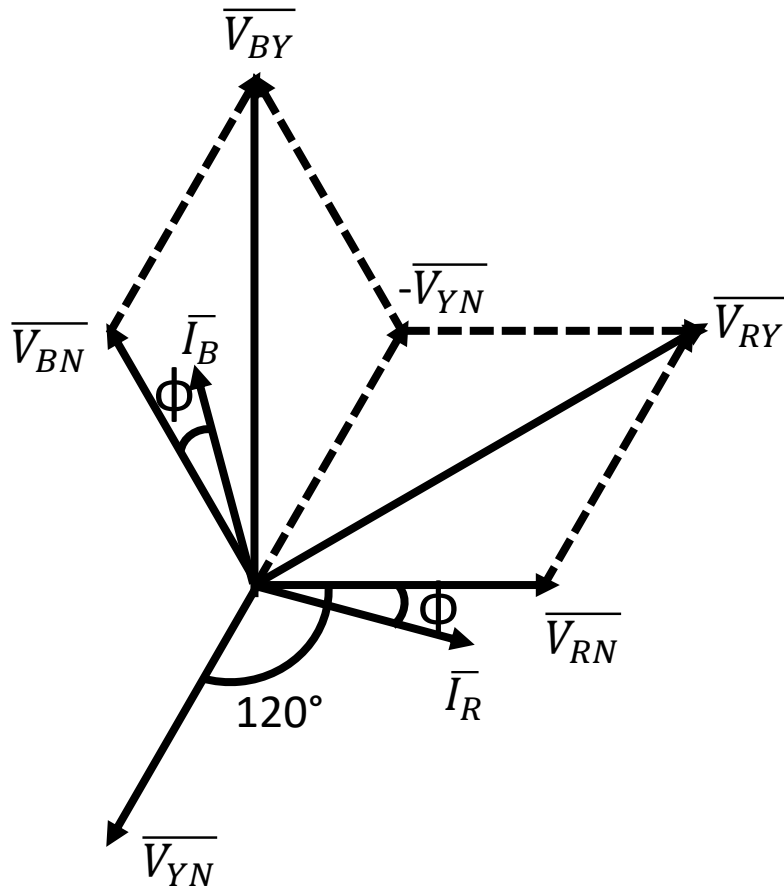
$$W_2 = V_{BY} * I_B * \cos(\angle(V_{BY}, I_B))$$



$$\overline{V_{RY}} = \overline{V_{RN}} - \overline{V_{YN}}$$

$$\overline{V_{BY}} = \overline{V_{BN}} - \overline{V_{YN}}$$

Consider inductive load. Then, phase current lags phase voltage.

$$W_1 = V_{RY} * I_R * \cos(30 + \phi) \quad \& \quad W_2 = V_{BY} * I_B * \cos(30 - \phi)$$

$$W_1 = V_{RY} * I_R * \cos(30+\phi) \quad \& \quad W_2 = V_{BY} * I_B * \cos(30-\phi)$$

$$W_1 = V_L * I_L * \cos(30+\phi) \quad \& \quad W_2 = V_L * I_L * \cos(30-\phi)$$

$$\text{Therefore, } W_1 + W_2 = \sqrt{3} * V_L * I_L * \cos\phi = P_{3\text{-phase}} \text{ --- (1)}$$

$$\text{Similarly, } \sqrt{3} * (W_2 - W_1) = \sqrt{3} * V_L * I_L * \sin\phi = Q_{3\text{-phase}} \text{ --- (2)}$$

$$\frac{(2)}{(1)} \rightarrow \frac{Q_{3\text{-phase}}}{P_{3\text{-phase}}} = \frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2} = \tan\phi$$

Hence, power factor of the system is,

$$\cos\phi = \cos\left(\tan^{-1}\left(\frac{\sqrt{3} * (W_2 - W_1)}{W_1 + W_2}\right)\right)$$

### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.





**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**