

Unit I: Assessment Question Bank

Lecture - 26

1. A series RC circuit with $R = 10 \, \Omega$, $C = 100 \, \mu\text{F}$ has frequency of 50 Hz. Obtain expression for the voltage if the current is given by

(i) $i = 30 \sin(\omega t)$

(ii) $i = 30 \sin(\omega t + 45^\circ)$

(iii) $i = 3 \sin(\omega t - 60^\circ)$

(iv) $i = 3 \sin(\omega t + 300^\circ)$

2. A capacitor is used in series with a tungsten- filament bulb rated at 500W,100V, so that it gives its rated illumination when connected to a 220V,50Hz supply. Calculate the value of the capacitance, current drawn by the supply. Find the power factor.