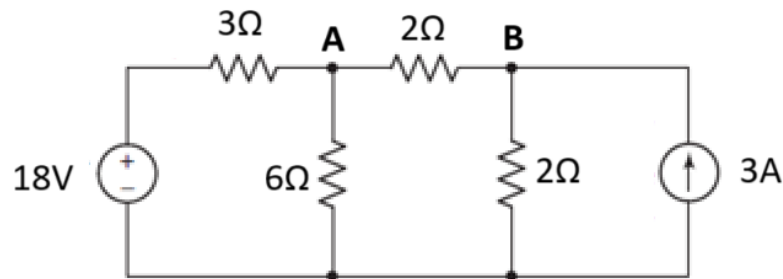


Unit I: Assessment: Q & A (Selected)

Lecture 6


1. Apply Source Transformation to find the current flowing through branch AB in the given network.



Solution :


(Ans : 1A)

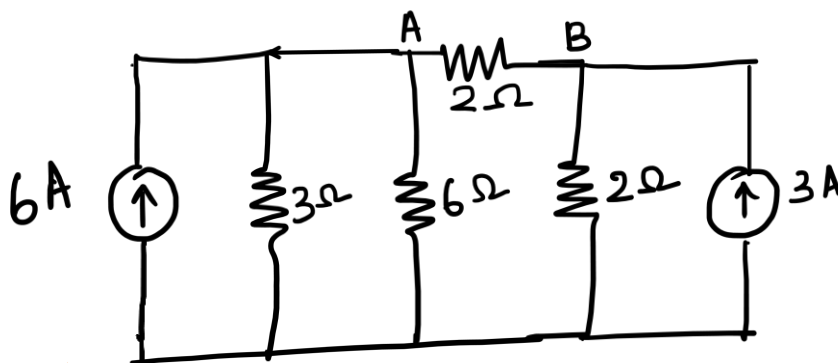Step 1 : Converting 18V voltage source to current source.




$$I = \frac{18}{3} = 6A$$

Resistances 3 & 6 are in parallel $(3 \parallel 6) = 2\Omega$

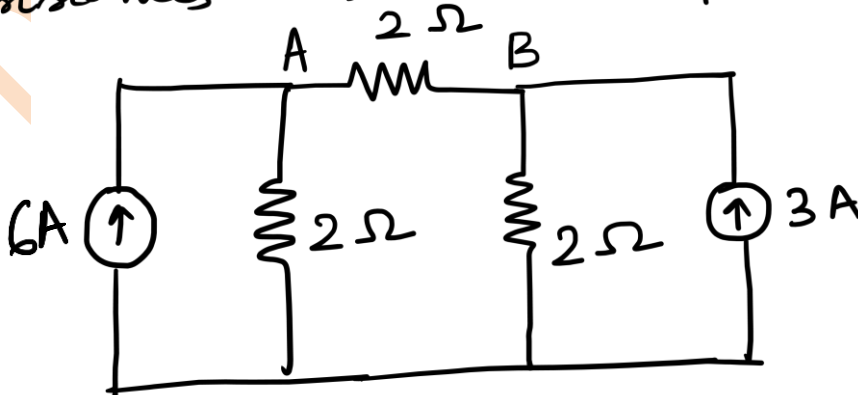

Unit I: Assessment: Q & A (Selected)

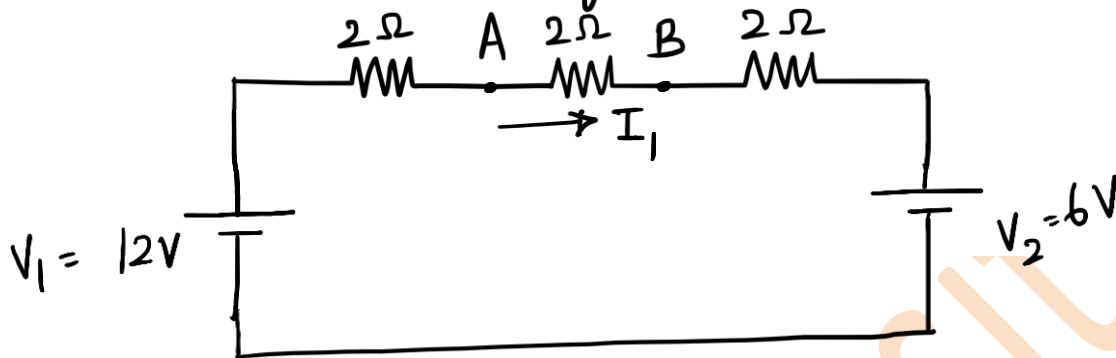Step 2 : Converting 6A & 3A current source to voltage source



Apply KVL

$$12 - 6I_1 - 6 = 0$$

$$6I_1 = 6$$

$$I_1 = 1A$$

$$V_1 = 6 \times 2 = 12V$$

$$V_2 = 3 \times 2 = 6V$$