

Unit IV : Assessment Question Bank

Lecture 63

1. Explain in brief with the help of a circuit diagram, how OC & SC are conducted on a single-phase transformer.

PES University