

Unit I: Assessment: Assignments**Assignment – Lecture 29**

1. When a two element parallel circuit is connected across an AC source of frequency 50 Hz, it offers an impedance $(10-j10)\Omega$. Determine the values of the two elements.