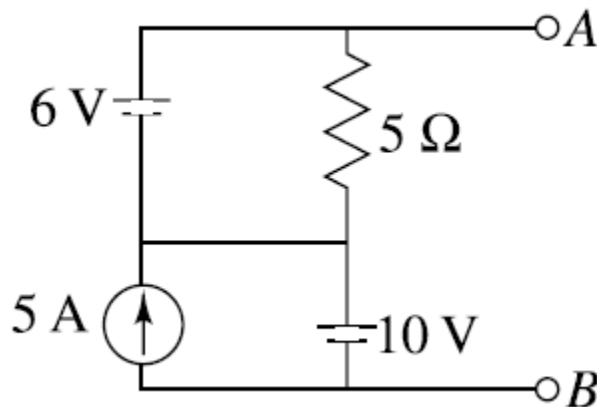


## Unit I: Assessment: Q & A (Selected)


### Lecture 13

1. Find the voltage  $V_{AB}$  using Superposition Theorem.



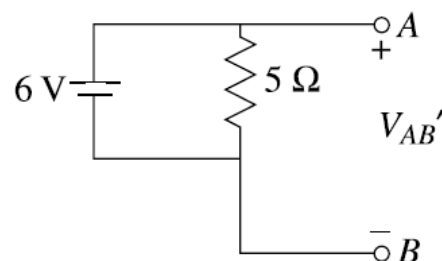
**Solution:**

**Step I:** When the 6-V source is acting alone



$$V_{AB}' = 6 \text{ V}$$

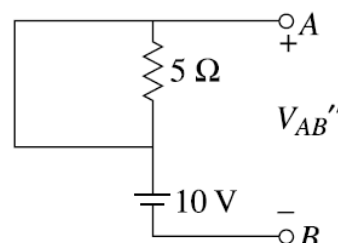
**Step II:** When the 10-V source is acting alone



# Unit I: Assessment: Q & A (Selected)

Since the resistor of  $5\ \Omega$  is shorted, the voltage across it is zero.

$$V_{AB}'' = 10\ \text{V}$$

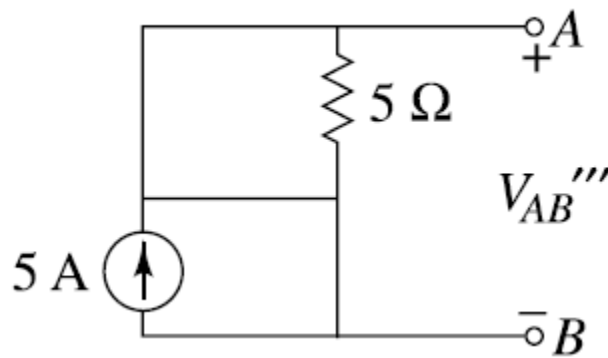

**Step III:** When the 5-A source is acting alone

Due to short circuit in both the parts,

$$V_{AB}''' = 0\ \text{V}$$

**Step IV:** By superposition theorem,

$$\begin{aligned} V_{AB} &= V_{AB}' + V_{AB}'' + V_{AB}''' \\ &= 6 + 10 + 0 = 16\ \text{V} \end{aligned}$$