

# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---



## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING

---


## Numerical Examples on Thevenin's Theorem

**Jyothi T N**

Department of Electrical & Electronics Engineering
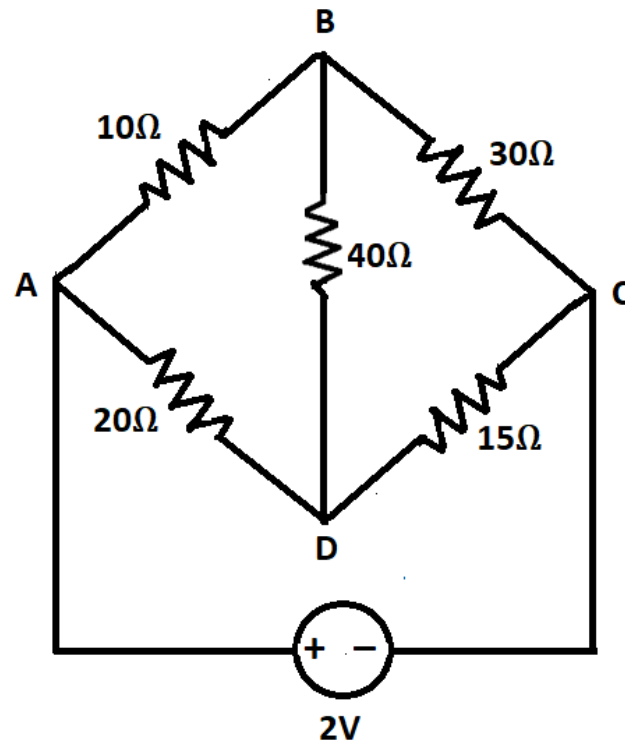
### Question:

Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown.




# ELEMENTS OF ELECTRICAL ENGINEERING

## Numerical Example 1

$$I_1 = \frac{2V}{40\Omega} = 0.05A ; I_2 = \frac{2V}{35\Omega} = 0.057A$$

**Solution :**

Finding  $V_{TH}$  :

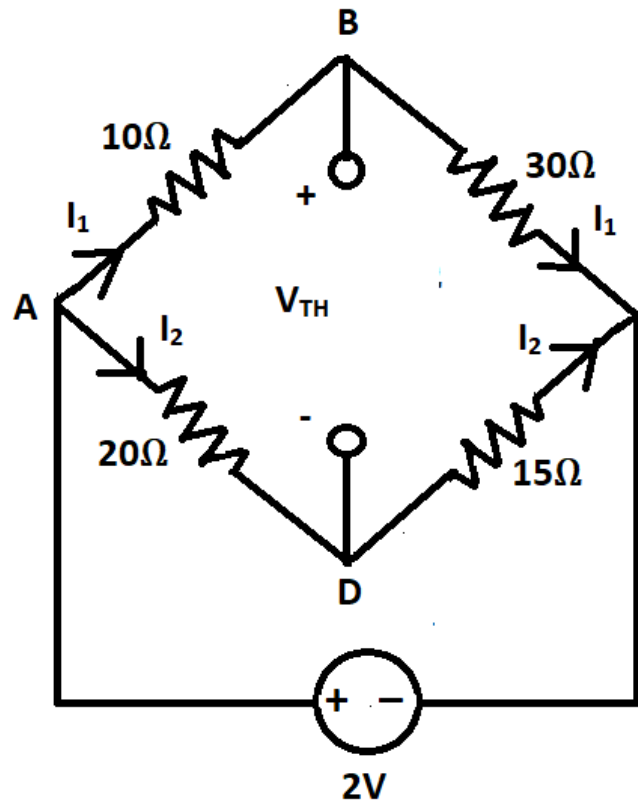


$$I_1 = \frac{2V}{40\Omega} = 0.05A ; I_2 = \frac{2V}{35\Omega} = 0.057A$$

By KVL (ABDA),  $-10 \cdot I_1 - V_{TH} + 20 \cdot I_2 = 0$


$$V_{TH} = 0.64V$$

**Solution (Continued..) :**

Finding  $R_{TH}$  :

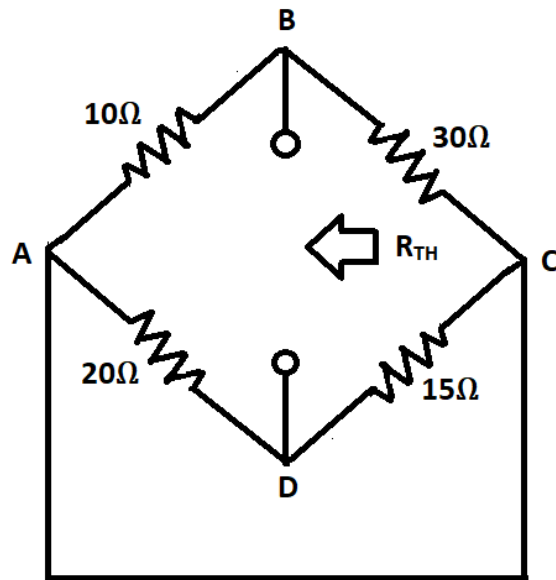

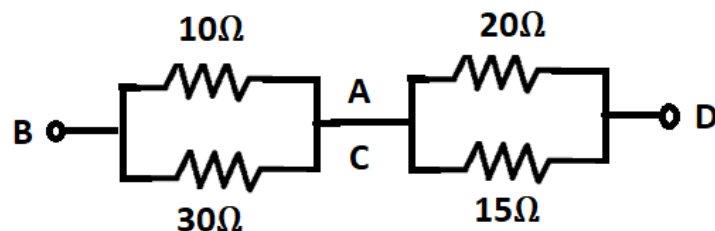
$$R_{TH} = (10\Omega \parallel 30\Omega) + (20\Omega \parallel 15\Omega) = 16.07\Omega$$



**Solution (Continued..) :**

**Thevenin's Equivalent Circuit:**

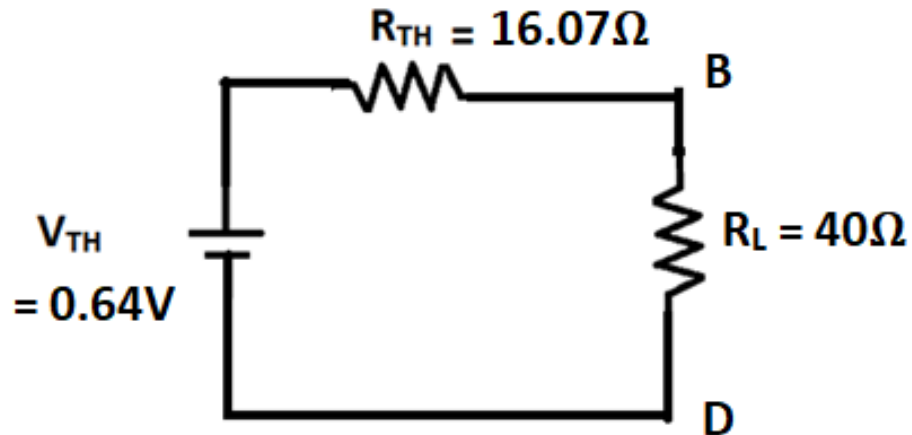


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Hence, current through the branch BD is 11.41mA and flows from terminal B to terminal D

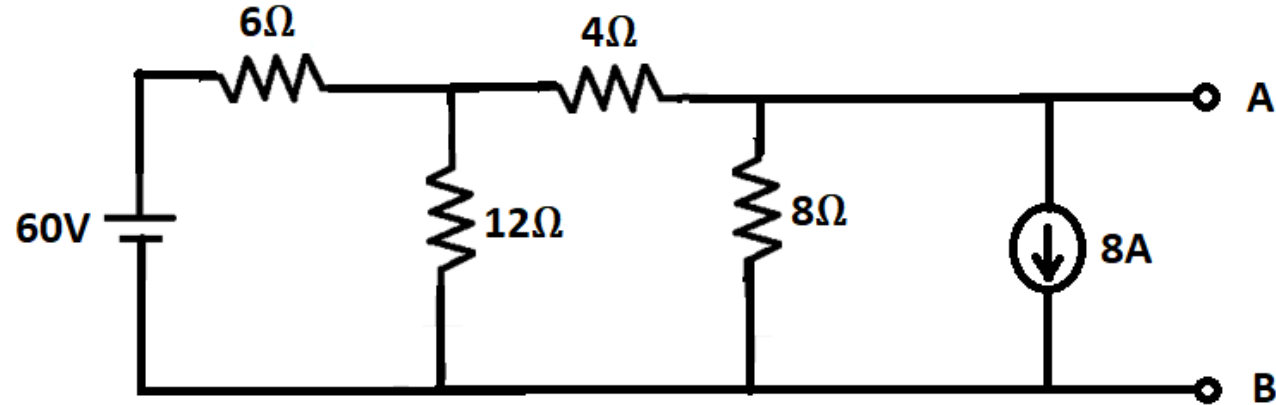
### Question:

Obtain the Thevenin's Equivalent across the terminals A & B for the network given.



### Solution :

Finding  $V_{TH}$  :

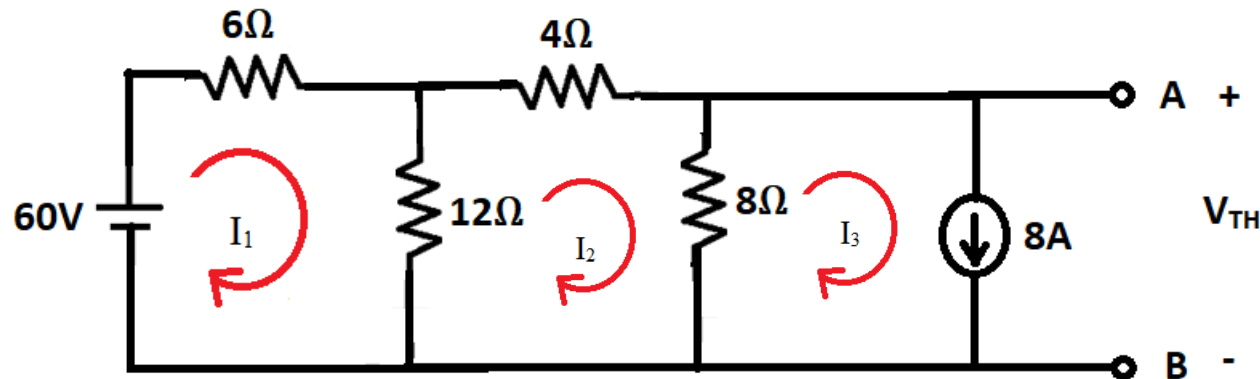

$$\text{KVL (Mesh 1)} : 18I_1 - 12I_2 - 0I_3 = 60 \quad \text{---- (1)}$$

$$\text{KVL (Mesh 2)} : -12I_1 + 24I_2 - 8I_3 = 0 \quad \text{---- (2)}$$

$$\text{Current Equation (Mesh 3)} : I_3 = 8 \quad \text{---- (3)}$$


Solving (1), (2) & (3),  $I_1 = 7.66\text{A}$  ;  $I_2 = 6.5\text{A}$

$$V_{TH} = (I_2 - I_3) * 8\Omega = -12\text{V}$$



**Solution (Continued..) :**


Finding  $R_{TH}$  :

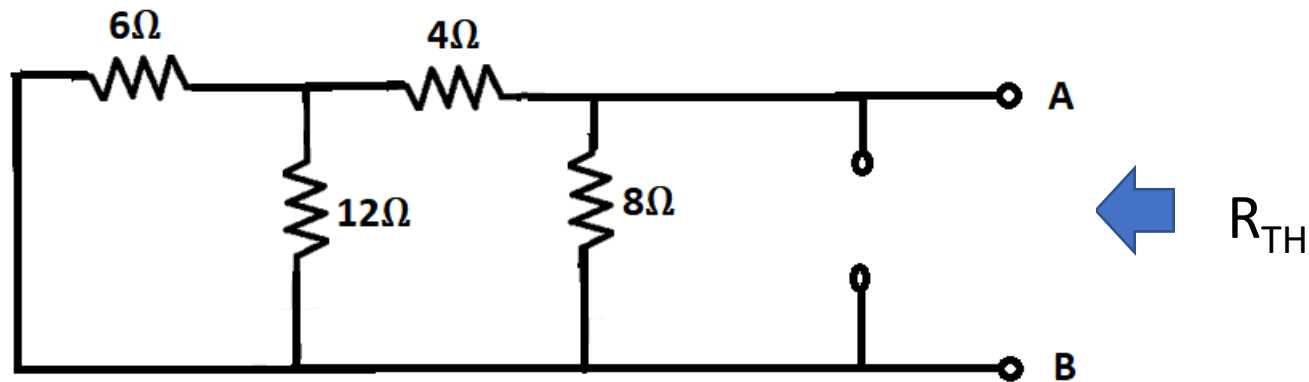


$$R_{TH} = \{(6\Omega \parallel 12\Omega) + 4\Omega\} \parallel 8\Omega = 4\Omega$$

**Solution (Continued..) :**

**Thevenin's Equivalent Circuit:**

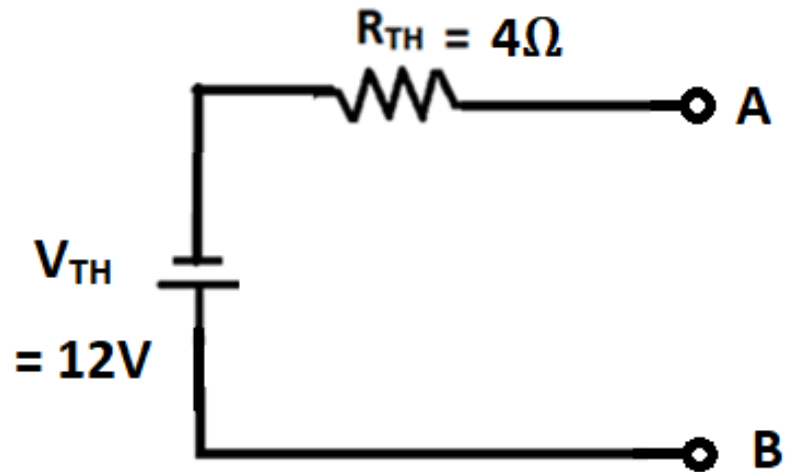

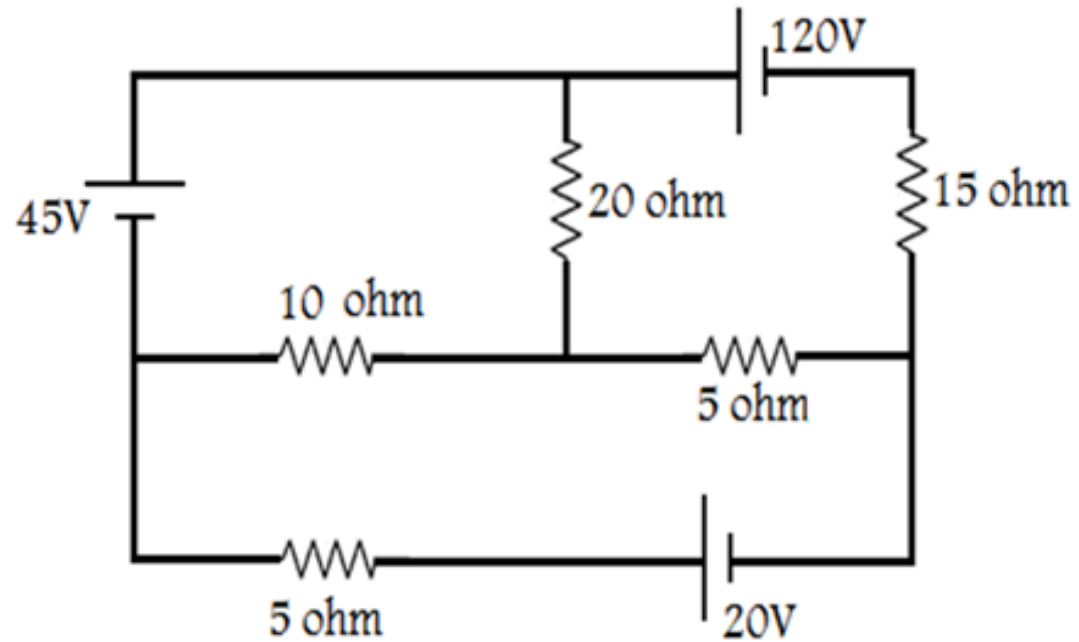Find the current through  $20\Omega$  resistor using Thevenin's theorem



### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**