

## Unit I: Assessment: Assignments

### Assignment – Lecture 12

1. Using Superposition Theorem, Find current through  $8\Omega$  resistor in the network below.

