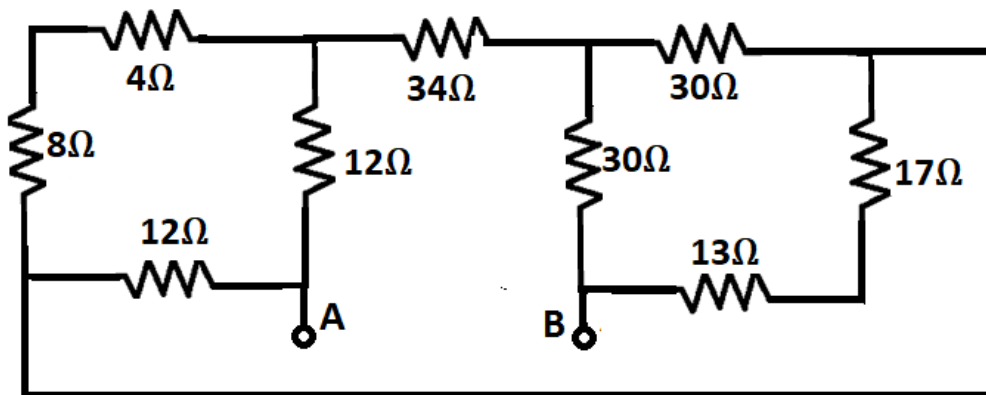


## Unit I: Assessment Question Bank

### Lecture 9

- Find the equivalent resistance between the terminals A and B in the given network.



- Find the equivalent resistance between the terminals A & B in network shown.

