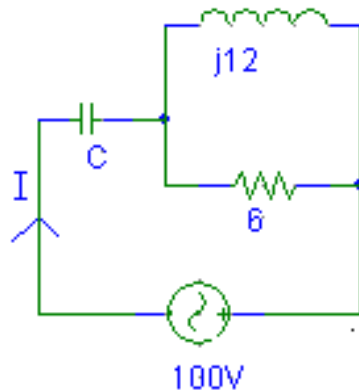


Unit I: Assessment: Q & A (Selected)

Lecture 32

Q1. The circuit shown in figure operates at a frequency of 50Hz. Determine the value of C such that the input voltage V and the input current I are in the same phase.



Solution:

Since V & I are in phase, circuit must be resistive in nature. Hence, total impedance is resistive which means its j-term is zero.

$$\begin{aligned} \text{Total impedance} &= -jXC + (j12) \parallel 6 \\ &= -jXC + 4.8 + j2.4 \end{aligned}$$

$$= 4.8 + j(2.4 - XC)$$

Equating j-term to zero,

$$XC = 2.4\Omega$$

$$\text{Hence, } C = 1.326\text{mF}$$