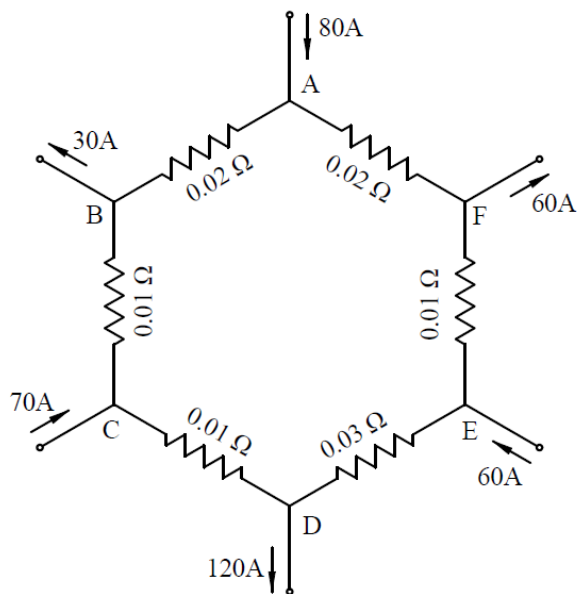


Unit I: Assessment: Assignments

Assignment – Lecture 5

- Find the current in all the branches in the network shown.



(Ans : $I_{AF} = 39A$; $I_{FE} = -21A$; $I_{ED} = 39A$; $I_{DC} = -81A$; $I_{CB} = -11A$; $I_{BA} = -41A$)