

Unit III : Assessment: Assignments**Assignment – Lecture 47**

1.

In a balanced three phase system, power is measured by two wattmeter method. The ratio of two readings of wattmeters are found to be 4:1. Find the powerfactor of the system.