

Unit I: Assessment: Assignments

Assignment – Lecture 8

1. Find current delivered by 4V battery in the network shown using star-delta transformations:

