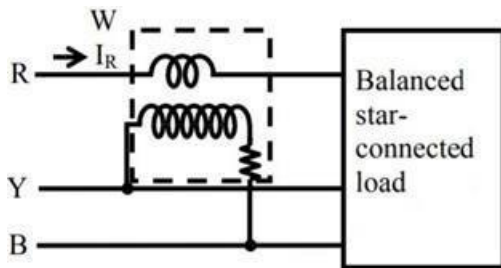


Unit III: Assessment Question Bank

Lecture 50

1. Calculate the reading of the wattmeter (W) connected as shown in Fig below. The load is a balanced star-connected one, with impedance of $(20+j15) \Omega$ per phase, fed from a three-phase, 400 V, balanced supply, with the phase sequence as R-Y-B.



2. Calculate the reading of the two watt-meters (W_1 , and W_2) connected to measure the power for a balanced three-phase load. The supply voltage is 200V for a star- connected balanced load with $(9-j5) \Omega$ per phase. The connections of the wattmeter, W_1 – current coil is in R line, and the voltage coil is across R and Y lines. The connections of the wattmeter, W_2 – current coil is in B line, and the voltage coil is across B and Y lines.