

Unit I: Assessment: Q & A (Selected)


Lecture 5

1. A current of 20A flows through two ammeters A and B joined in series. Across A the potential difference is 0.2V and across B it is 0.3V. Find how the same current will divide between A and B when they are joined in parallel.

SOLUTION:

An ideal ammeter has zero resistance. The voltage drop across an ideal ammeter is zero. Since there is potential difference across each ammeter, each of them has some internal resistance. Let R_A and R_B be the internal resistances of Ammeters A & B respectively.


When joined in series,

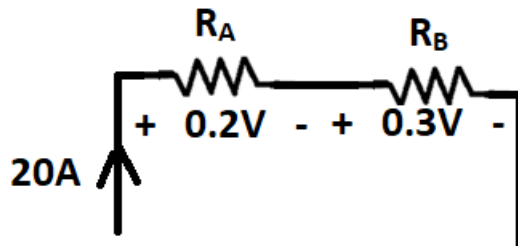

$$R_A = \frac{0.2V}{20A} = 0.01\Omega ; R_B = \frac{0.3V}{20A} = 0.015\Omega$$

When joined in parallel & for same total input current of 20A,

Unit I: Assessment: Q & A (Selected)

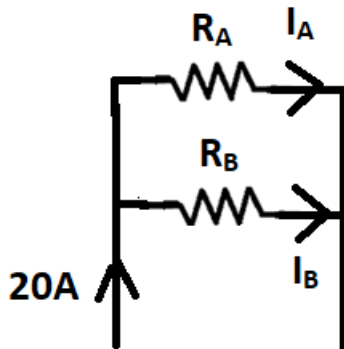

Let I_A & I_B be the currents through R_A & R_B respectively.

By current division rule,

$$I_A = 20A * \left(\frac{R_B}{R_A + R_B} \right) = 12A ; I_B = 20A * \left(\frac{R_A}{R_A + R_B} \right) = 8A$$