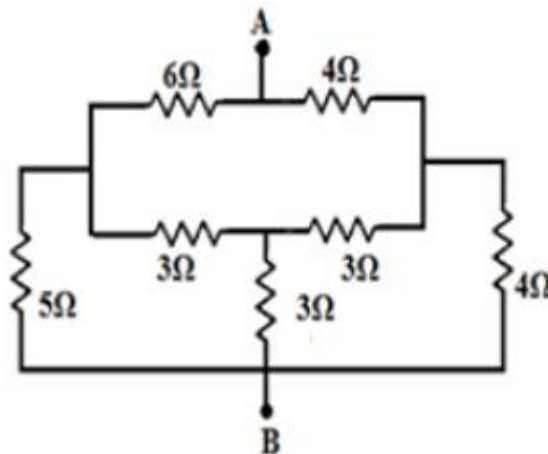


Unit I: DC Circuits

Notes Class - 9

Example: Using Star and Delta transformation determine the equivalent resistance between the terminals A & B.



Solution:

$3\Omega - 3\Omega - 3\Omega$ star when converted to delta would be $9\Omega - 9\Omega - 9\Omega$

9Ω is in parallel with 5Ω which gives 3.21Ω

9Ω is in parallel with 4Ω which gives 2.77Ω

Changing $6\Omega - 4\Omega - 9\Omega$ delta to star, we get $1.26\Omega - 1.89\Omega - 2.84\Omega$

Finally $(2.84\Omega + 3.21\Omega) \parallel (1.89\Omega + 2.77\Omega) + 1.26\Omega = 3.89\Omega$