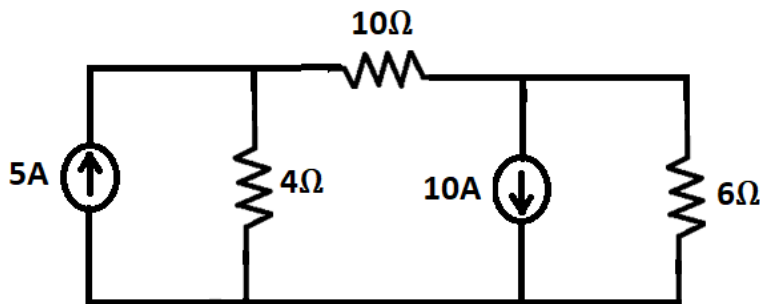


Class 17

Q1. Using Thevenin's Theorem, obtain the current through 10Ω resistor in the network shown.



Q2. Obtain Thevenin's equivalent across the terminals A & B in the network below:

