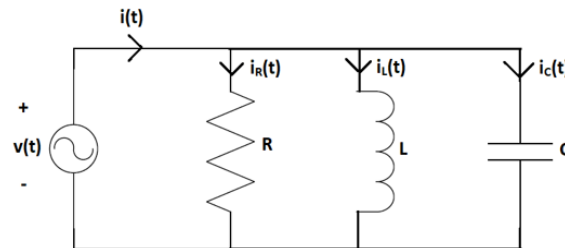


NOTES -Class 30

Analysis of Parallel RLC circuits

Parallel RLC Circuit:



$$\text{By KCL, } i(t) = i_R(t) + i_L(t) + i_C(t)$$

$$\text{In Phasor form, } \bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C$$

$$\bar{I}_R = \bar{V} * G \quad \bar{I}_L = \bar{V} * (-jB_L) \quad \bar{I}_C = \bar{V} * (jB_C)$$

$$\bar{I} = \bar{V} * (G - jB_L + jB_C)$$

$$Y_T = \frac{\bar{I}}{\bar{V}} = (G - jB_L + jB_C) = \sqrt{G^2 + (B_L - B_C)^2} \angle \tan^{-1} \left(\frac{B_C - B_L}{G} \right)$$


Case 1: $B_L > B_C$

If $B_L > B_C$ then $VB_L > VB_C$

$$\text{i.e., } |\bar{I}_L| > |\bar{I}_C|$$

The circuit behaves effectively as inductive circuit i.e., parallel RL type.

Phasor Diagram:

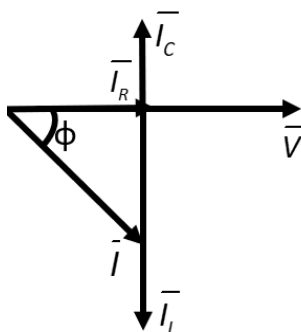

$$\phi = \tan^{-1} \left(\frac{|\bar{I}_L| - |\bar{I}_C|}{|\bar{I}_R|} \right) = \tan^{-1} \left(\frac{I_L - I_C}{I_R} \right)$$

$$= \tan^{-1} \left(\frac{B_L - B_C}{G} \right)$$

Unit II : Single Phase AC Circuits


Case 2: $B_C > B_L$

If $B_C > B_L$ then $VB_C > VB_L$

$$\text{i.e., } |\bar{I}_C| > |\bar{I}_L|$$

The circuit behaves effectively as a capacitive circuit i.e., parallel RC type.

Phasor Diagram:

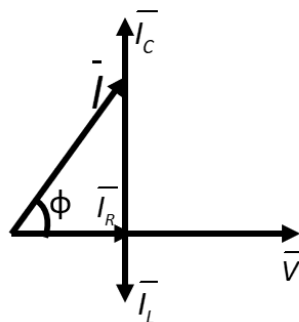

$$\begin{aligned}\phi &= \tan^{-1} \left(\frac{|\bar{I}_C| - |\bar{I}_L|}{|\bar{I}_R|} \right) = \tan^{-1} \left(\frac{I_L - I_C}{I_R} \right) \\ &= \tan^{-1} \left(\frac{B_L - B_C}{G} \right)\end{aligned}$$


Note: ϕ will be negative in this case since $B_L < B_C$

Case 3: $B_L = B_C$

If $B_L = B_C$ then $VB_L = VB_C$ i.e., $|\bar{I}_L| = |\bar{I}_C|$

The circuit behaves effectively as a purely resistive circuit. This case is called '**Parallel Resonance**' case.

Phasor Diagram:

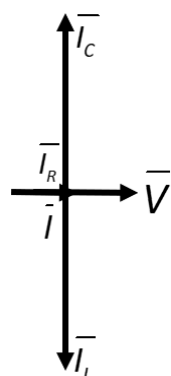


$$\bar{I} = \bar{I}_R$$

$$Y = G$$

$$\phi = 0^\circ$$

Unit II : Single Phase AC Circuits

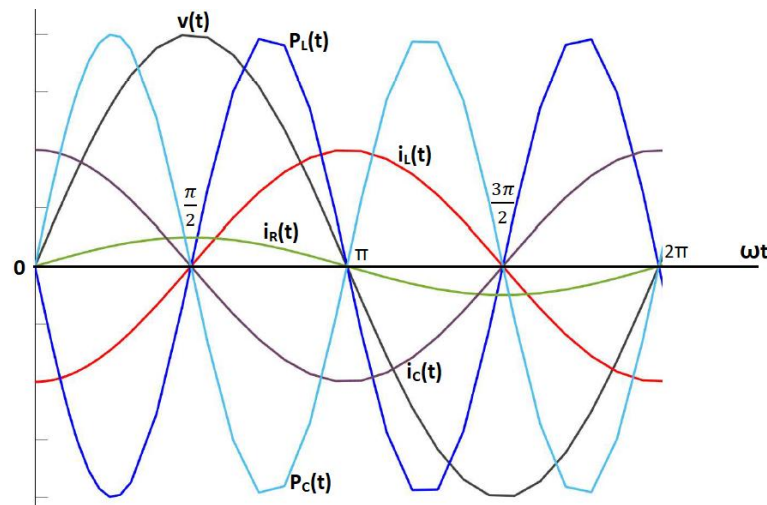


Question 12:

Three circuit elements $R=2.5\Omega$, $X_L=4\Omega$ and $X_C=10\Omega$ are connected in parallel, the reactance being at 50Hz.

- Determine the admittance of each element and hence obtain the input admittance.
- If this circuit is connected across a 10V, 50Hz AC source, determine the current in each branch and the total input current.

Solution:

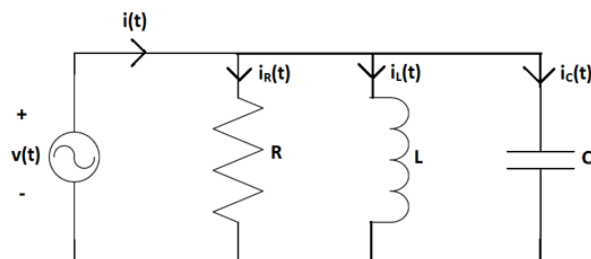

i) Admittance of branch1, $Y_1 = \frac{1}{Z_1} = \frac{1}{R} = G = 0.4S$

Admittance of branch2, $Y_2 = \frac{1}{Z_2} = \frac{1}{jX_L} = -jB_L = -j0.25S$

Admittance of branch3, $Y_3 = \frac{1}{Z_3} = \frac{1}{-jX_C} = jB_C = j0.1S$

Input Admittance $Y_{in} = Y_T = Y_1 + Y_2 + Y_3 = (0.4 - j0.15)S$

Unit II : Single Phase AC Circuits

ii) Taking supply voltage as reference, $\bar{V} = 10\angle 0^\circ \text{V}$

current in branch 1, $\bar{I}_R = \frac{\bar{V}}{Z_1} = \bar{V}Y_1 = 10\angle 0^\circ * 0.4 = 4\angle 0^\circ \text{A}$

current in branch 2, $\bar{I}_L = \bar{V}Y_2 = 10\angle 0^\circ * (-j0.25) = 2.5\angle -90^\circ \text{A}$

current in branch 3, $\bar{I}_C = \bar{V}Y_3 = 1\angle 90^\circ \text{A}$

Input current, $\bar{I}_S = \bar{I}_R + \bar{I}_L + \bar{I}_C = 4.27\angle -20.55^\circ \text{A}$