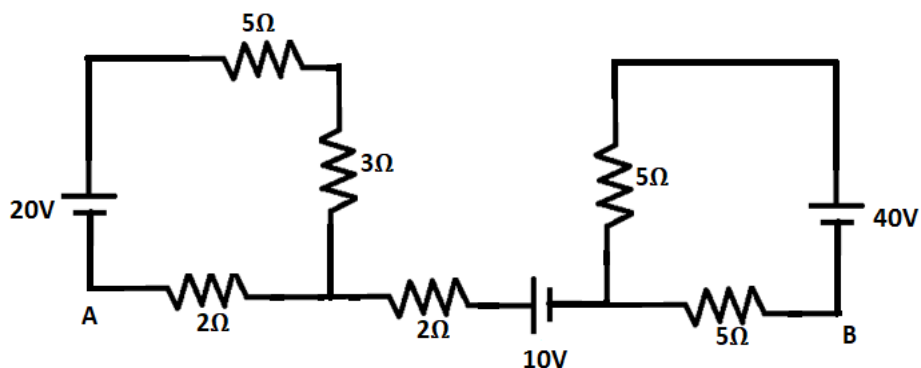



## Unit I: Assessment: Q &amp; A (Selected)

## Lecture 1

2. Find the voltage  $V_{AB}$  in the network shown:



SOLUTION:

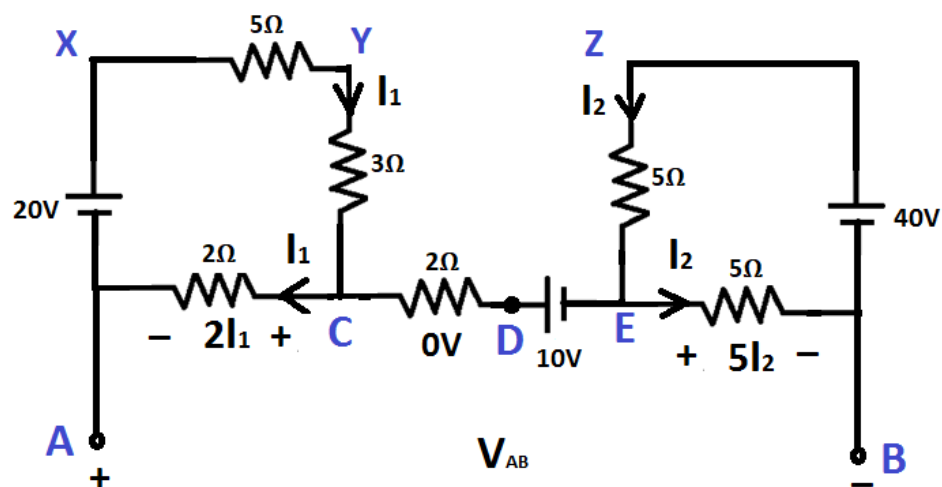

$$\text{KVL (AXYCA): } +20-5I_1-3I_1-2I_1 = 0; \text{ Hence, } I_1 = 2\text{A}$$

$$\text{KVL (BZEB): } +40-5I_2-5I_2 = 0; \text{ Hence, } I_2 = 4\text{A}$$

$$\text{KVL (ACDEBA): } +2I_1-10-5I_2+V_{AB} = 0; \text{ Hence, } V_{AB} = 26\text{V}$$