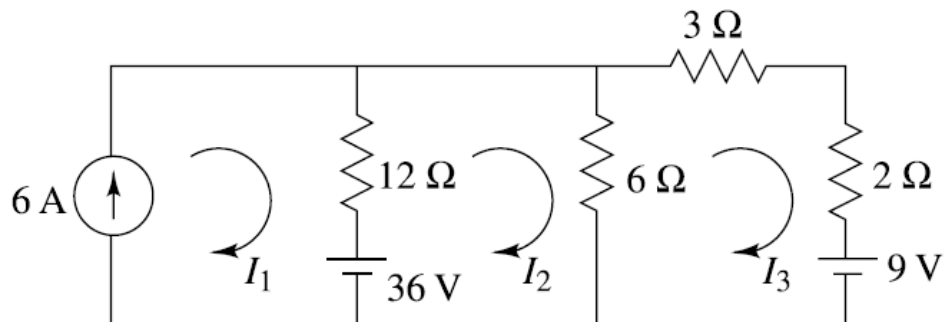


Unit I: Assessment Question Bank

Lecture 11

- Find the current through the 2Ω resistor.



- Find the current through 6Ω resistor using Mesh Analysis.

