

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING


Star Delta Transformations


Jyothi T N

Department of Electrical & Electronics Engineering


Sometimes resistors can neither be combined in series nor parallel.

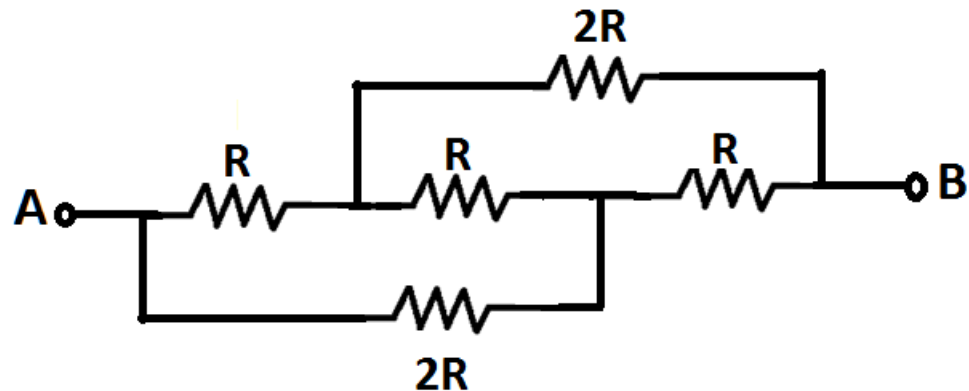For instance, consider the following network:




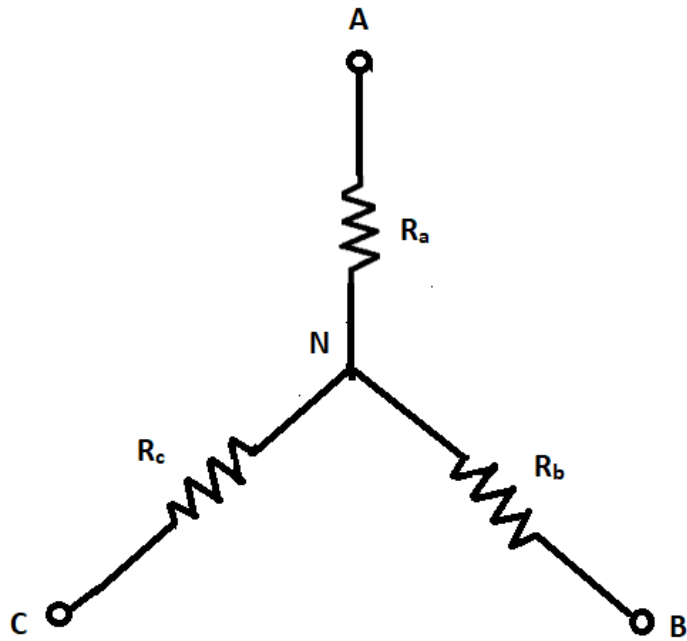

STAR (OR) WYE
CONNECTION

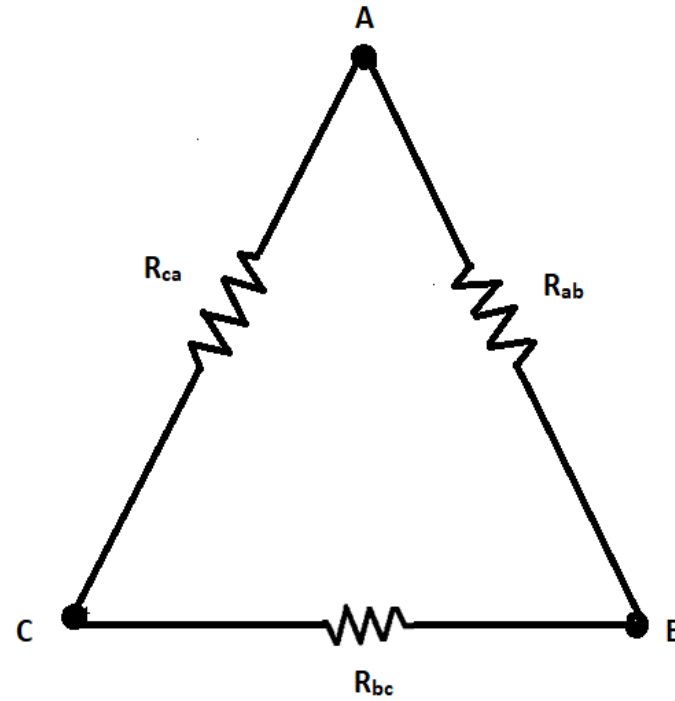

DELTA (OR) MESH
CONNECTION

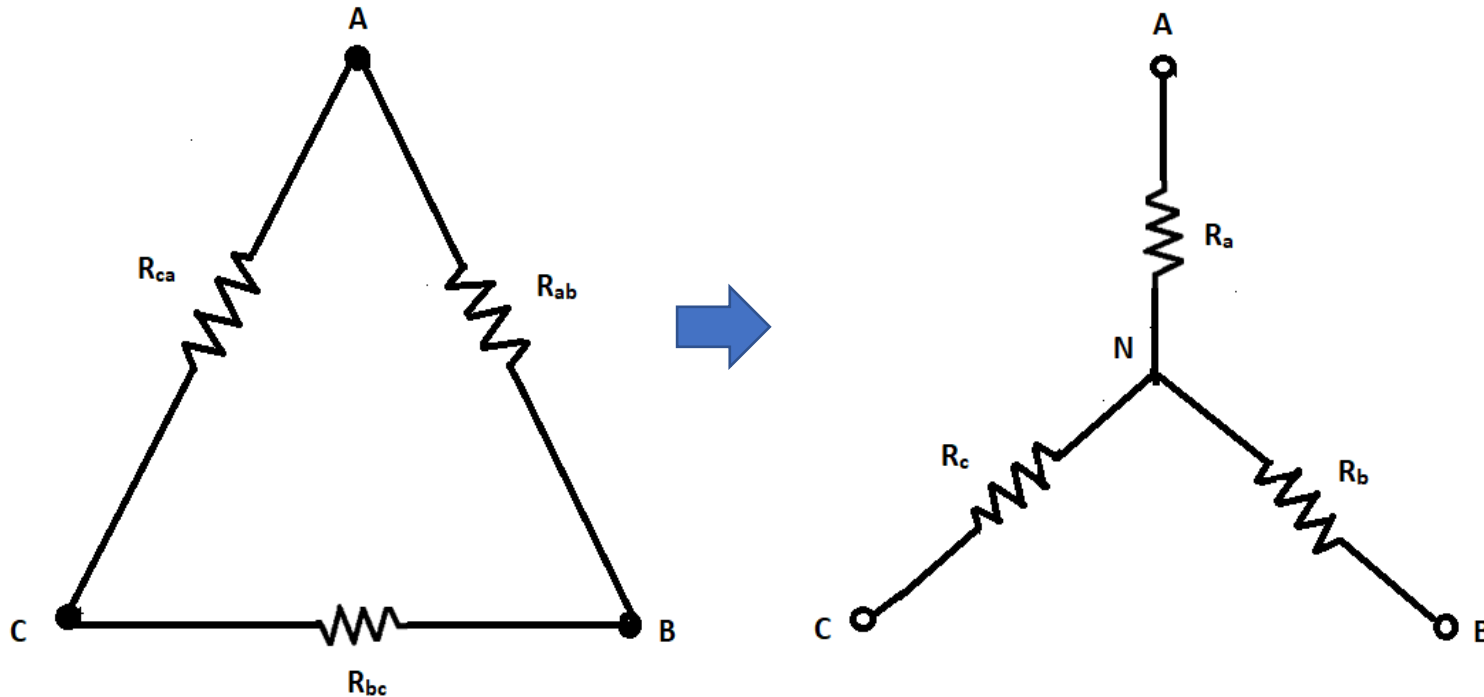

Equivalent resistance between terminals A & B:

For Delta, it is $\frac{R_{ab} * (R_{bc} + R_{ca})}{(R_{ab} + R_{bc} + R_{ca})}$

For Star, it is $(R_a + R_b)$

Since for the transformation, they must be equivalent,

$$(R_a + R_b) = \frac{R_{ab} * (R_{bc} + R_{ca})}{(R_{ab} + R_{bc} + R_{ca})} \text{ ----- (1)}$$

Similarly between the terminals B & C

$$(R_b + R_c) = \frac{R_{bc} * (R_{ca} + R_{ab})}{(R_{ab} + R_{bc} + R_{ca})} \text{ ----- (2)}$$

Similarly between the terminals C & A

$$(R_c + R_a) = \frac{R_{ca} * (R_{ab} + R_{bc})}{(R_{ab} + R_{bc} + R_{ca})} \text{ ----- (3)}$$

$$(1) - (2) + (3)$$

$$2R_a = \frac{2R_{ab} * R_{ca}}{(R_{ab} + R_{bc} + R_{ca})}$$

$$R_a = \frac{R_{ab} * R_{ca}}{(R_{ab} + R_{bc} + R_{ca})} \quad \text{-----} \quad (4)$$

$$R_b = \frac{R_{bc} * R_{ab}}{(R_{ab} + R_{bc} + R_{ca})} \quad \text{-----} \quad (5)$$

$$R_c = \frac{R_{ca} * R_{bc}}{(R_{ab} + R_{bc} + R_{ca})} \quad \text{-----} \quad (6)$$

Equations (4), (5), (6) represent Delta to Star Transformation

Manipulating Equations (4), (5) & (6), we get the star to delta transformation equations as follows:


$$R_{ab} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_c} \text{ ----- (7)}$$

$$R_{bc} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_a} \text{ ----- (8)}$$


$$R_{ca} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_b} \text{ ----- (9)}$$

Equations (7), (8), (9) represent Star to Delta Transformation

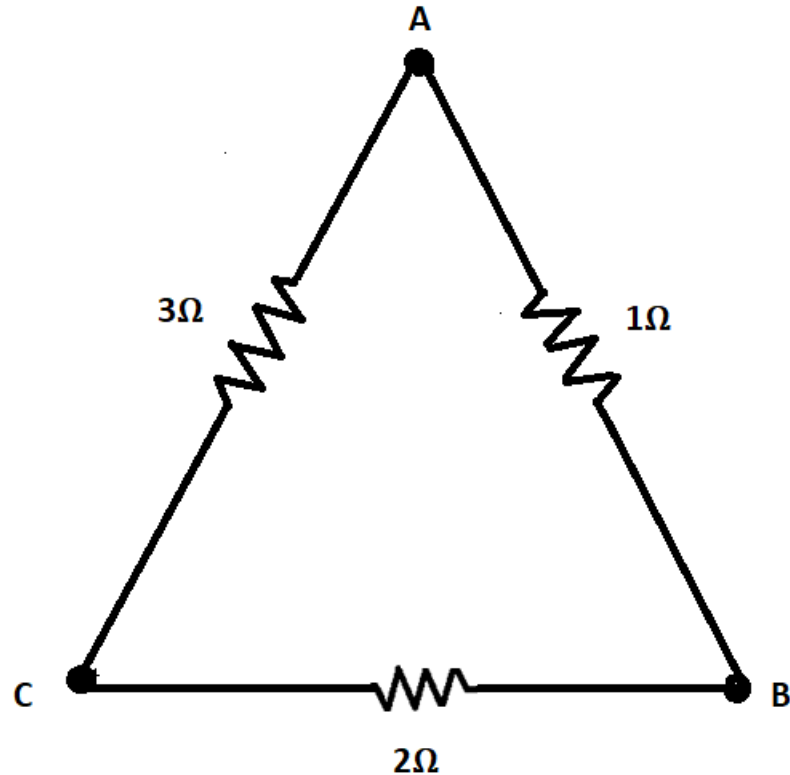Example 1: Transform the given delta to equivalent star




Solution:

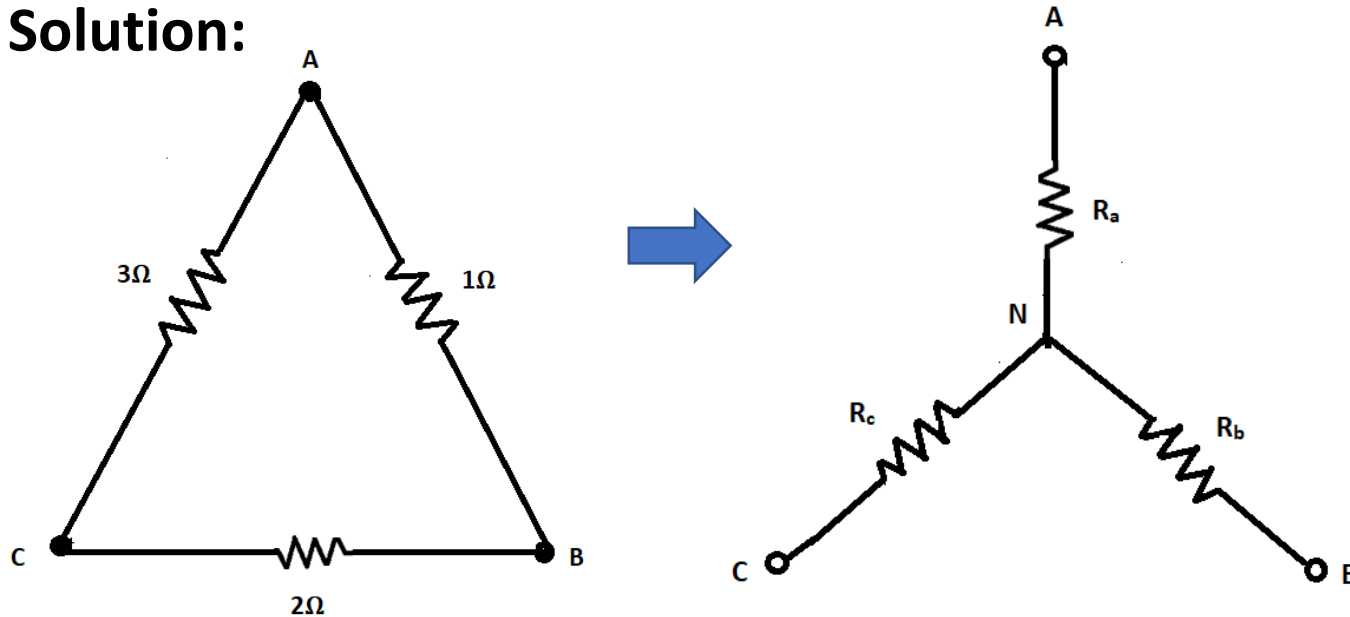


$$R_a = \frac{R_{ab} * R_{ca}}{(R_{ab} + R_{bc} + R_{ca})} = \frac{1 * 3}{(1 + 2 + 3)} = \frac{1}{2} \Omega$$

$$\text{Similarly, } R_b = \frac{1 * 2}{(1 + 2 + 3)} = \frac{1}{3} \Omega \quad \& \quad R_c = \frac{2 * 3}{(1 + 2 + 3)} = 1 \Omega$$

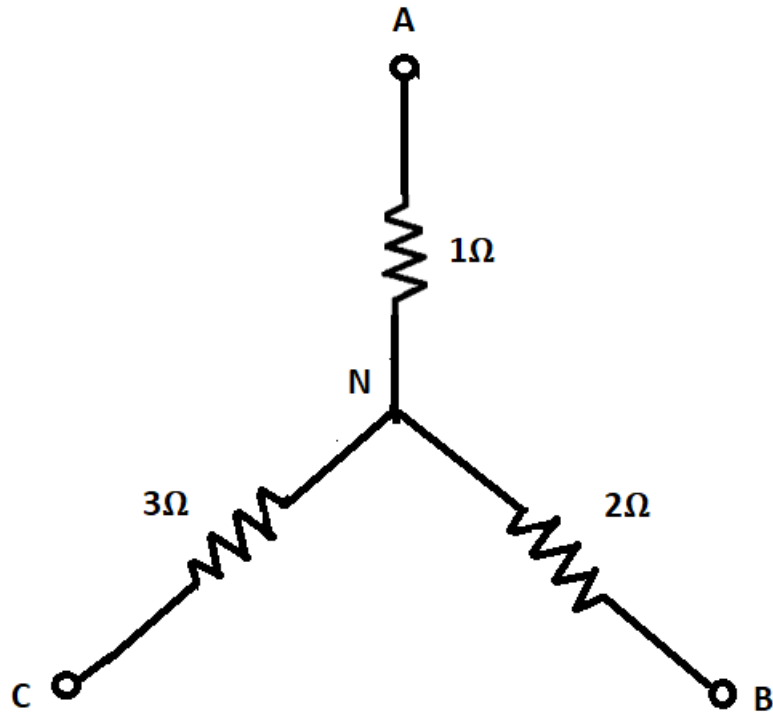Example 2: Transform the given star to equivalent delta



Solution:

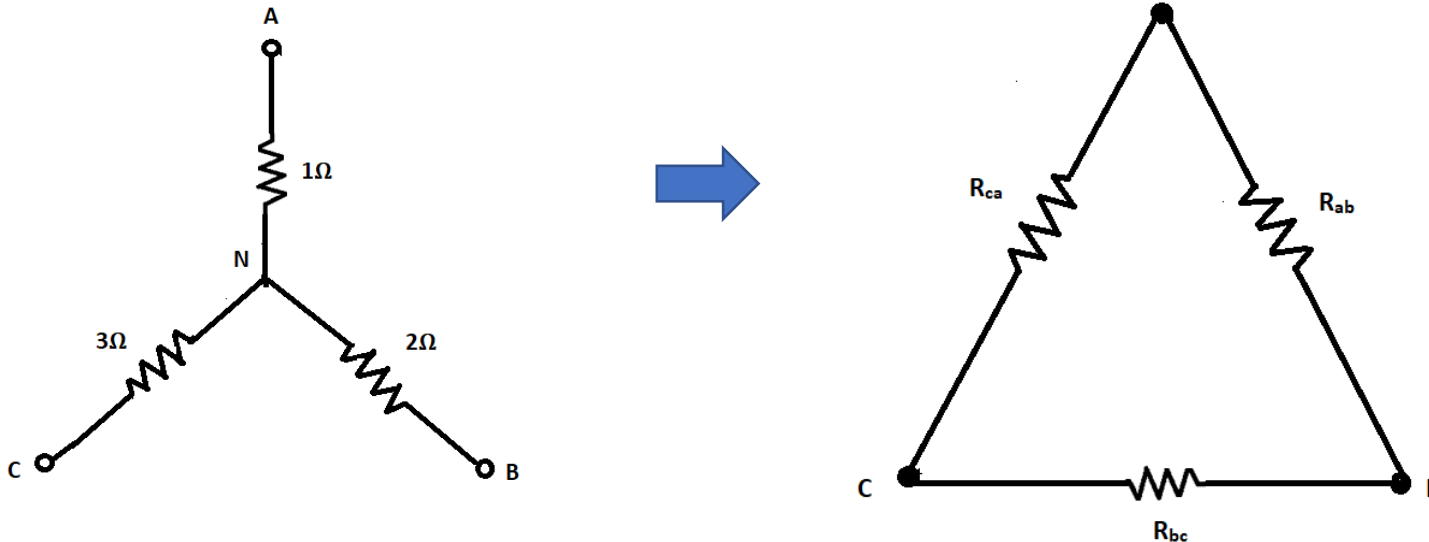

$$R_{ab} = \frac{R_a * R_b + R_b * R_c + R_c * R_a}{R_c} = \frac{1*2 + 2*3 + 3*1}{(3)} = \frac{11}{3} \Omega$$

$$\text{Similarly, } R_{bc} = \frac{11}{(R_a)} = 11 \Omega \text{ \& } R_{ca} = \frac{11}{(R_b)} = \frac{11}{2} \Omega$$

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu