

Unit I: Assessment Question Bank

Lecture 3

1. Write a short note on source transformation.
2. Find the current i_{out} when $R_{out} = 3\text{ k}\Omega$ using source transformation.

