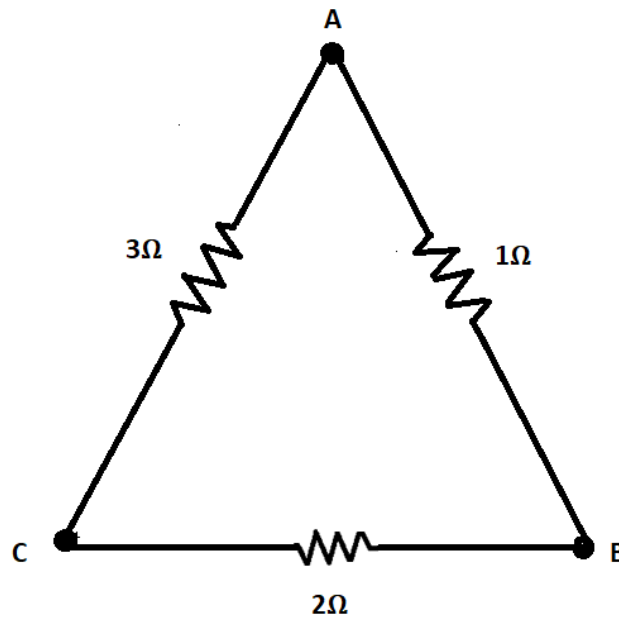


Unit I: Assessment Question Bank

Lecture 7

1. Derive how a delta set of resistors is transformed to its equivalent star.
2. Transform the given delta to equivalent star:



3. Transform the given star to equivalent delta:

