

Unit III: Three Phase Balanced Systems & Electrical Installations

NOTES Class 44

Examples on Balanced Star connected Three Phase System:

Numerical Example 1:


Question:

A balanced 3 phase load consists of three coils, each of 4Ω resistance and $0.02H$ inductance. Determine the total active and reactive power when the coils are connected in star, if the supply voltage is $400V$, 50 Hz .

Solution :

Note: In three phase systems, by default, the voltages and currents given are line voltage and line current respectively.

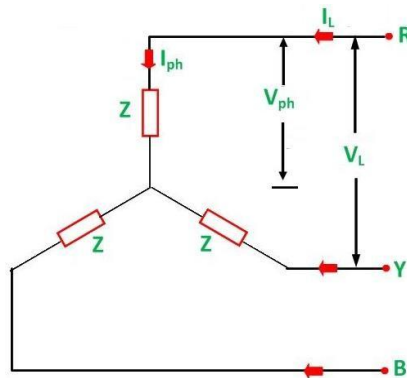Similarly, power given is three phase power by default.



Given Data:

Line voltage, $V_L = 400V$; $f = 50\text{Hz}$

Resistance per phase, $R = 4\Omega$

Inductance per phase, $L = 0.02H$

Unit III: Three Phase Balanced Systems & Electrical Installations

Calculations:

Inductive reactance per phase, $X_L = 2\pi fL = 6.28\Omega$

Impedance per phase, $Z = R + jX_L = (4 + j6.28)\Omega$

Hence, $|Z| = 7.45\Omega$; Phase Angle, $\phi = 57.5^\circ$

Since star connected system, Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = 230.94V$

Hence, Phase current, $I_{ph} = \frac{V_{ph}}{|Z|} = 31A$

Therefore, Line current, $I_L = I_{ph} = 31A$

Three phase Active Power, $P_{3-phase} = 3 \cdot P_{1-phase} = 3 \cdot V_{ph} \cdot I_{ph} \cdot \cos(\phi) = 11.54KW$

Alternatively, $P_{3-phase} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi) = 11.54KW$

Alternatively, $P_{3-phase} = 3 \cdot I_{ph}^2 \cdot R = 11.54KW$

Similarly, Three phase Reactive Power,

$Q_{3-phase} = 3 \cdot Q_{1-phase} = 3 \cdot V_{ph} \cdot I_{ph} \cdot \sin(\phi) = 18.11KVAR$

Alternatively, $Q_{3-phase} = \sqrt{3} \cdot V_L \cdot I_L \cdot \sin(\phi) = 18.11KVAR$

Alternatively, $Q_{3-phase} = 3 \cdot I_{ph}^2 \cdot X_L = 18.11KVAR$

Numerical Example 2

Question:

A balanced 3Φ , star connected load of 100KW takes a leading current of 80A when connected to a 3Φ , 1.1KV, 50Hz supply. Find the resistance, impedance, and the capacitance of the load per phase. Also calculate the power factor of the load.

Solution :

Given Data:

Line voltage, $V_L = 1.1KV$; $f = 50Hz$

Unit III: Three Phase Balanced Systems & Electrical Installations

Line current, $I_L = 80\text{A}$

Unit III: Three Phase Balanced Systems & Electrical Installations

Three phase Active Power, $P_{3\text{-phase}} = 100\text{KW}$

Calculations:

Since star connected system, Phase current, $I_{ph} = I_L = 80\text{A}$

And Phase voltage, $V_{ph} = \frac{L}{\sqrt{3}} = 635.08\text{V}$

Impedance per phase, $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$P_{3\text{-phase}} = 100\text{KW} = 3 \cdot I_{ph}^2 \cdot R$; Hence, $R = 5.21\Omega$

Capacitive reactance per phase, $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase, $C = \frac{1}{\omega X_C} = 531.25\mu\text{F}$

Powerfactor of the load, $\cos\phi = \frac{R}{Z} = 0.656$ Lead

Alternative solution:

Since star connected system, Phase current, $I_{ph} = I_L = 80\text{A}$

And Phase voltage, $V_{ph} = \frac{L}{\sqrt{3}} = 635.08\text{V}$

Impedance per phase, $Z = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$

$P_{3\text{-phase}} = 100\text{KW} = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos(\phi)$

Hence, Powerfactor of the load, $\cos\phi = 0.656$ Lead

Resistance per phase, $R = Z \cdot \cos\phi = 5.21\Omega$

Capacitive reactance per phase, $X_C = \sqrt{(Z^2 - R^2)} = 5.99\Omega$

Hence, Capacitance per phase, $C = \frac{1}{\omega X_C} = 531.25\mu\text{F}$