

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING



Network Terminology, Basic Concepts and Kirchhoff's laws

Jyothi T N

Department of Electrical & Electronics Engineering

Electrical Network:

An interconnection of electrical elements.

Electrical Circuit:

An electrical network with at least one source and a sink and having a closed path for current flow.

Active Element:

An element which supplies or delivers energy in an electrical network.

Eg: Voltage Sources & Current Sources

Passive Element:



An element which absorbs or stores energy in an electrical network.

Eg: Resistors, Inductors & Capacitors

An electric current is defined as the rate of flow of charges across the cross section of a conductor.

It is given by, $I = \frac{Q}{t}$ (or) $i = \frac{dq}{dt}$

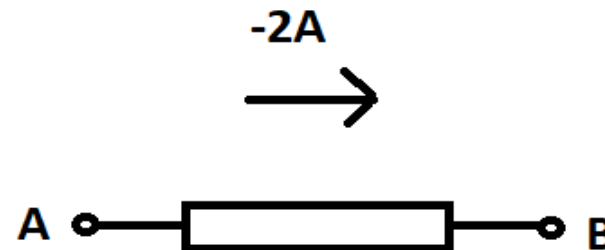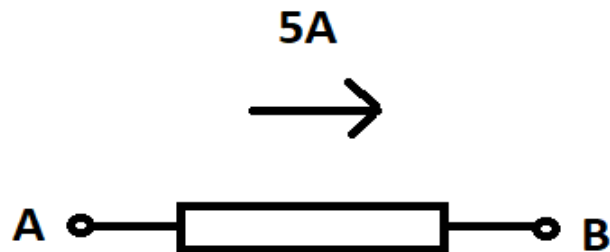
It is measured in Amperes (A) & 1 Ampere = 1 Coulomb/sec




The energy required to move unit positive charge from one terminal to another is defined as the potential difference between the terminals.

It is given by, $V = \frac{W}{Q}$

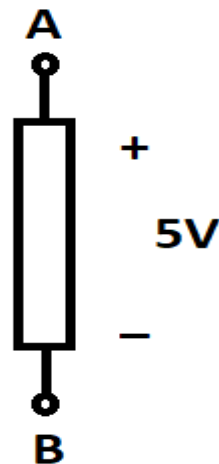
It is measured in Volts (V) & 1 Volt = 1 Joule/Coulomb



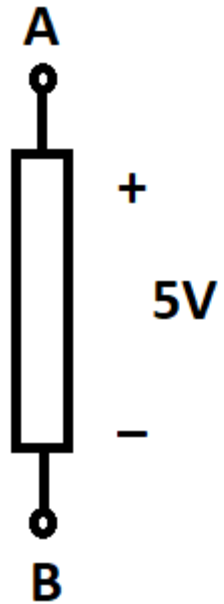


(a)

$$V_{AB} = 5V$$

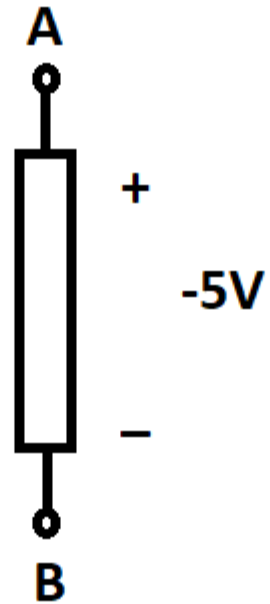

(b)

$$V_{AB} = -5V$$

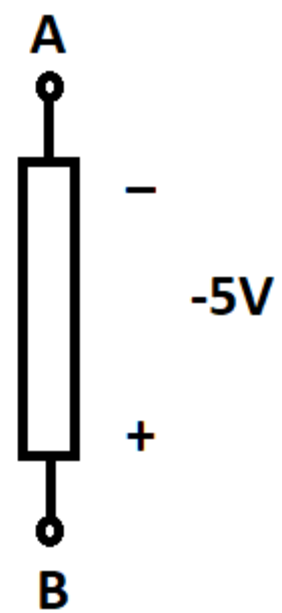


(c)

$$V_{AB} = 5V$$


The rate of absorption or delivery of Electrical energy is called Electrical Power.

It is given by, $P = V \cdot I$

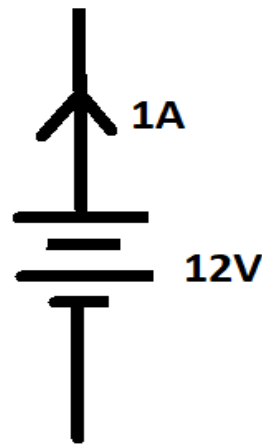It is measured in Watts (W) & 1 Watt = (1 Volt)*(1 Ampere)



$$P = -12W$$

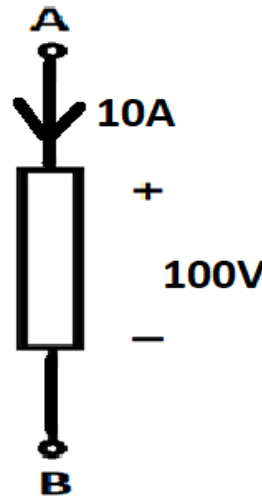

$$P = 1000W$$

At a constant temperature, the potential difference across the terminals of a conductor is directly proportional to the current flowing through it.

i.e., $V \propto I$

$$V = R \cdot I$$

Here, R is the electrical resistance of the conductor.

It is measured in Ohms (Ω) and $1 \text{ Ohm} = 1 \text{ Volt/Ampere}$



Resistance of a conductor is the opposition offered to the flow of current through it.

It depends on the resistivity of the material & its dimensions.

$$\text{i.e., } R = \frac{\rho l}{A}$$

Where, ρ is the resistivity measured in Ohm-m

$$\text{Conductance, } G = \frac{1}{R}$$

It is measured in Siemens (S)

Active sign convention:


Applicable to active elements

It says “current leaves positive terminal in an active element”.


Passive Sign Convention:

Applicable to passive elements

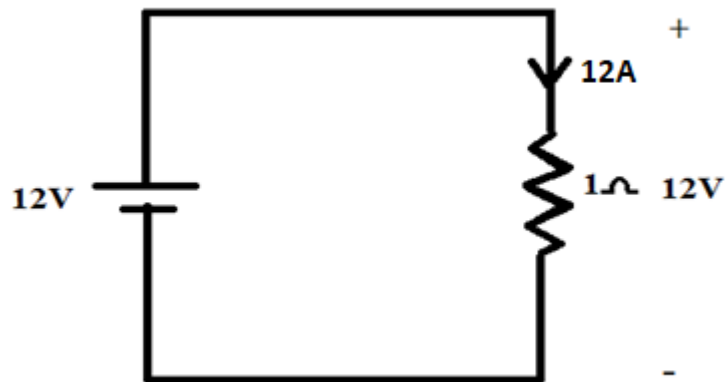It says “current enters positive terminal in a passive element”.




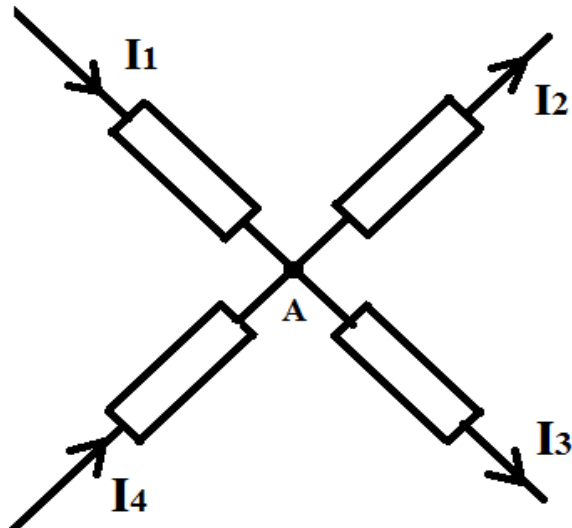- KCL States “At every node in an electric network, the algebraic sum of currents is Zero (or) sum of incoming currents is equal to the sum of outgoing currents”.
- A point at which two or more elements are interconnected is a node.
- KCL signifies the conservation of charge.




By KCL at node A,
 $I_1 + I_4 = I_2 + I_3$

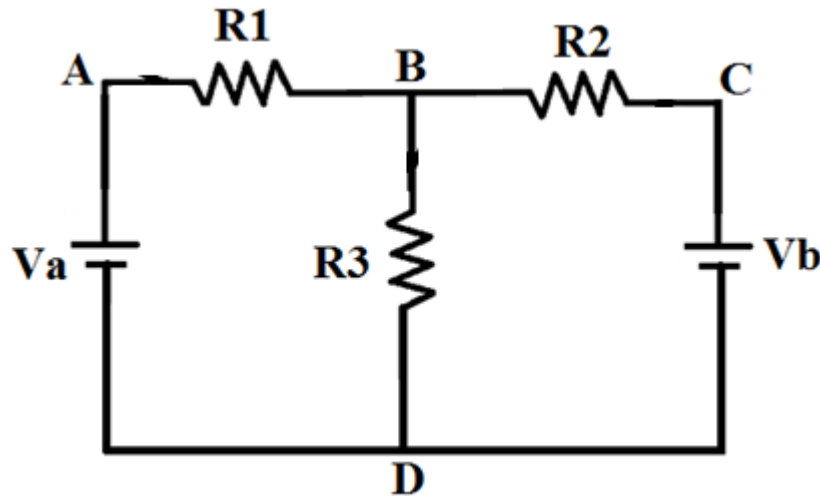- KVL States “Around every closed path in an electric network, the algebraic sum of voltages is Zero”.
- A path in an electrical network which starts and ends at the same terminal is called a closed path.



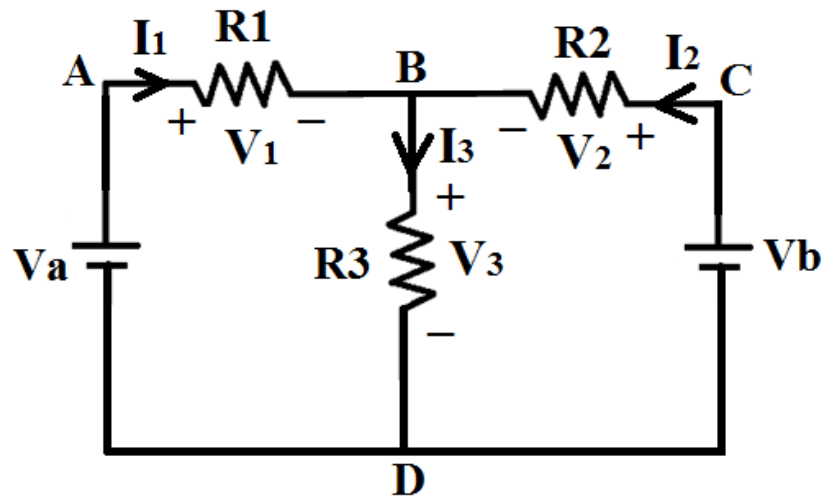
Conventionally, Voltage drop is considered negative and voltage rise as positive.




- KVL in the path ABDA:
 $-V_1 - V_3 + V_a = 0$
- KVL in the path BCDB:
 $V_2 - V_b + V_3 = 0$
- KVL in the path ABCDA:
 $-V_1 + V_2 - V_b + V_a = 0$

KVL signifies conservation of energy.

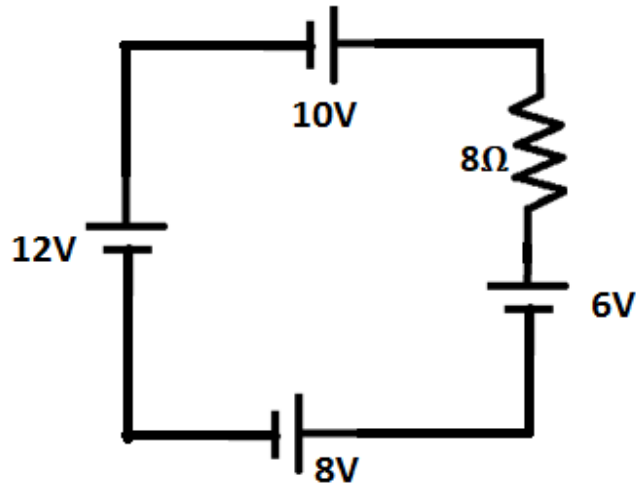Find the current through 8Ω resistor in the network given.



Solution:

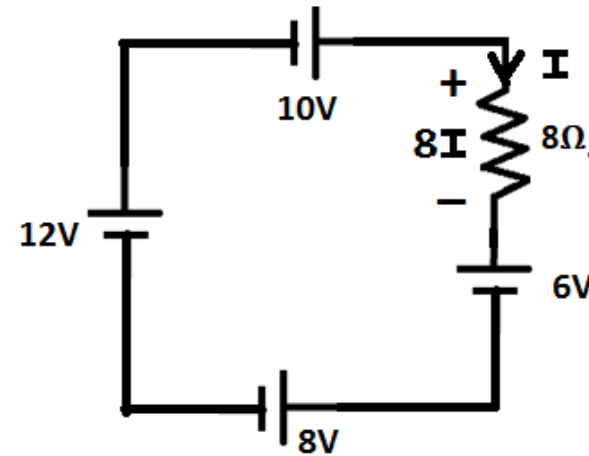

$$\text{KVL: } +10 - 8I - 6 - 8 + 12 = 0$$

$$\text{Hence, } I = 1A$$

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. 2.“Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu