

# ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B

---



## FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N  
Prof. Vadhiraj K P P  
Prof. Kruthika N  
Prof. Suma S  
Prof. Pushpa K R  
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L  
Prof. Dhanashree G Bhate  
Dr. Renuka R Kajur  
Prof. Rajesh Chandrashekar  
Prof. Sangam Kumar G H

# ELEMENTS OF ELECTRICAL ENGINEERING


---




## Balanced Star Connected Three Phase System; Voltage and Current Relations

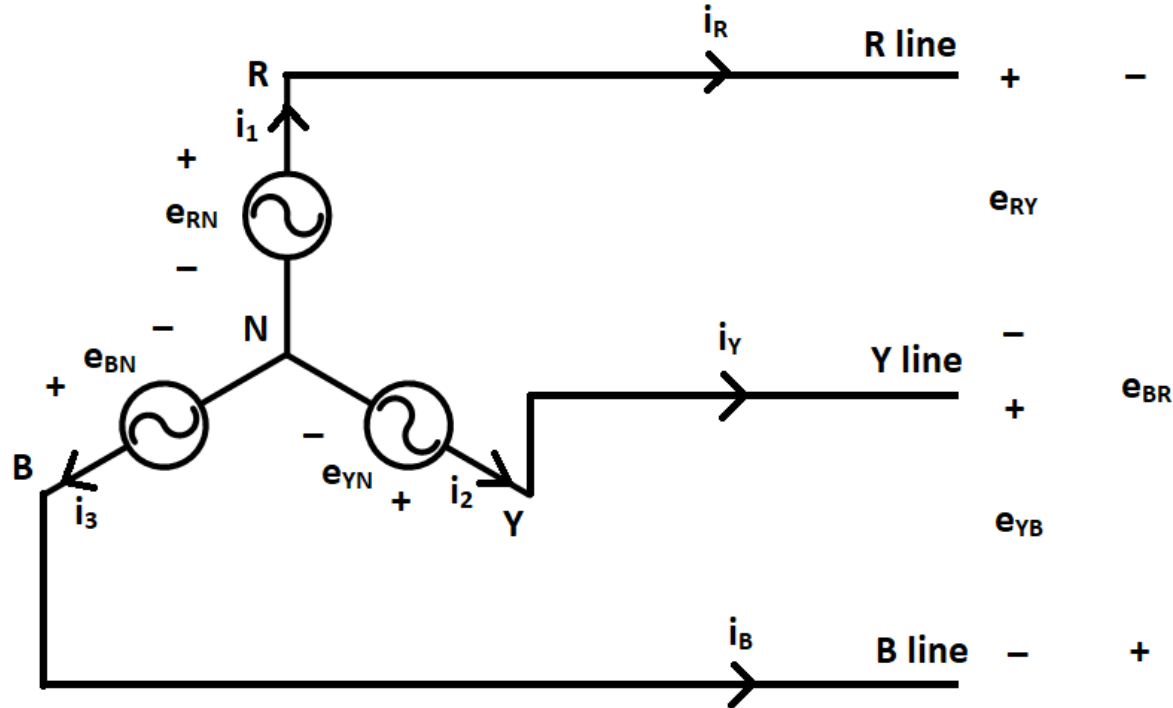**Jyothi T.N**

Department of Electrical & Electronics Engineering




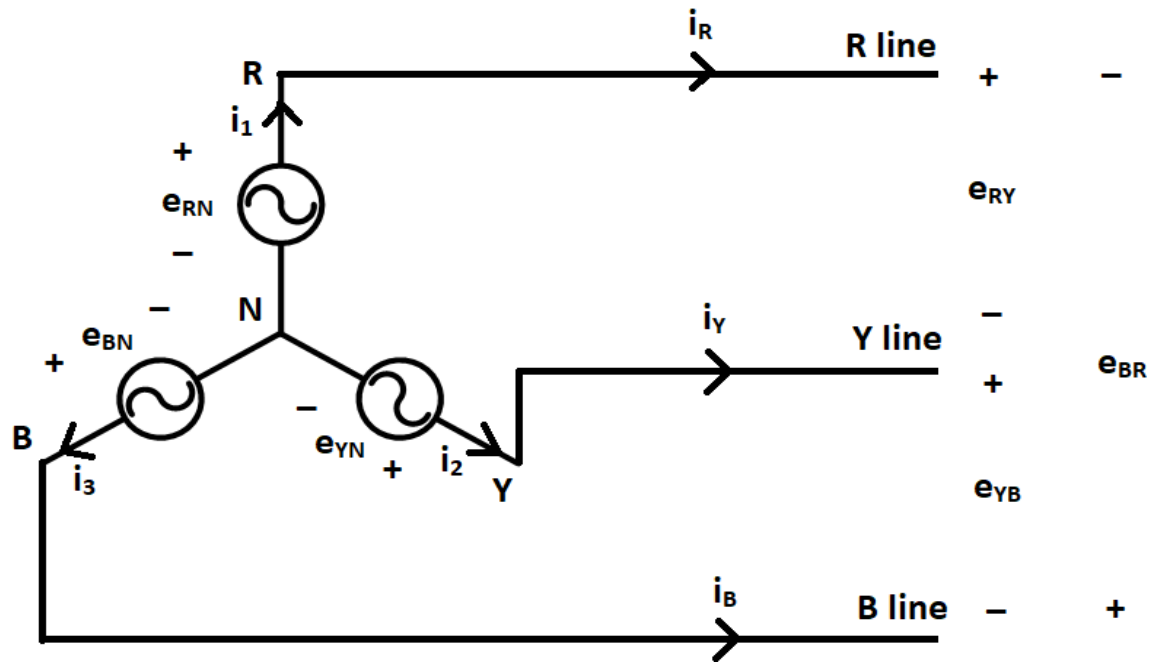- R', Y' & B' are connected together to form the 'Neutral' point of the system denoted by 'N'.
- $e_{RN}$ ,  $e_{YN}$  &  $e_{BN}$  represent phase voltages.



- $e_{RY}$ ,  $e_{YB}$  &  $e_{BR}$  represent Line (or) Line to line voltages.
- $i_1$ ,  $i_2$  &  $i_3$  represent phase currents.
- $i_R$ ,  $i_Y$  &  $i_B$  represent line currents.

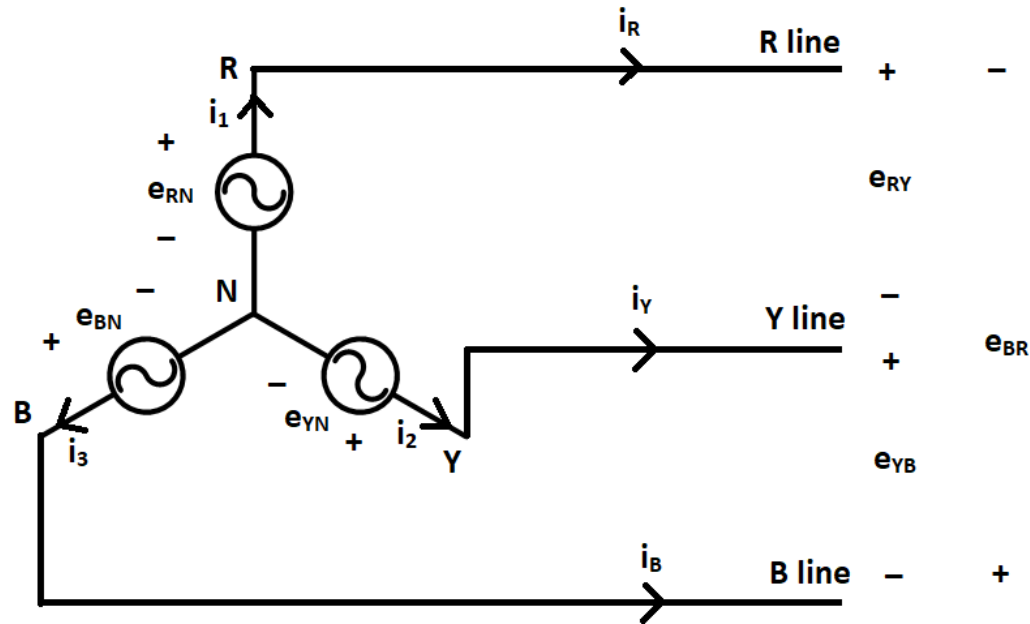In a balanced star connected three phase system,



Line current = Phase current


$$\text{i.e., } i_1 = i_R$$

$$i_2 = i_Y$$

$$i_3 = i_B$$

# ELEMENTS OF ELECTRICAL ENGINEERING
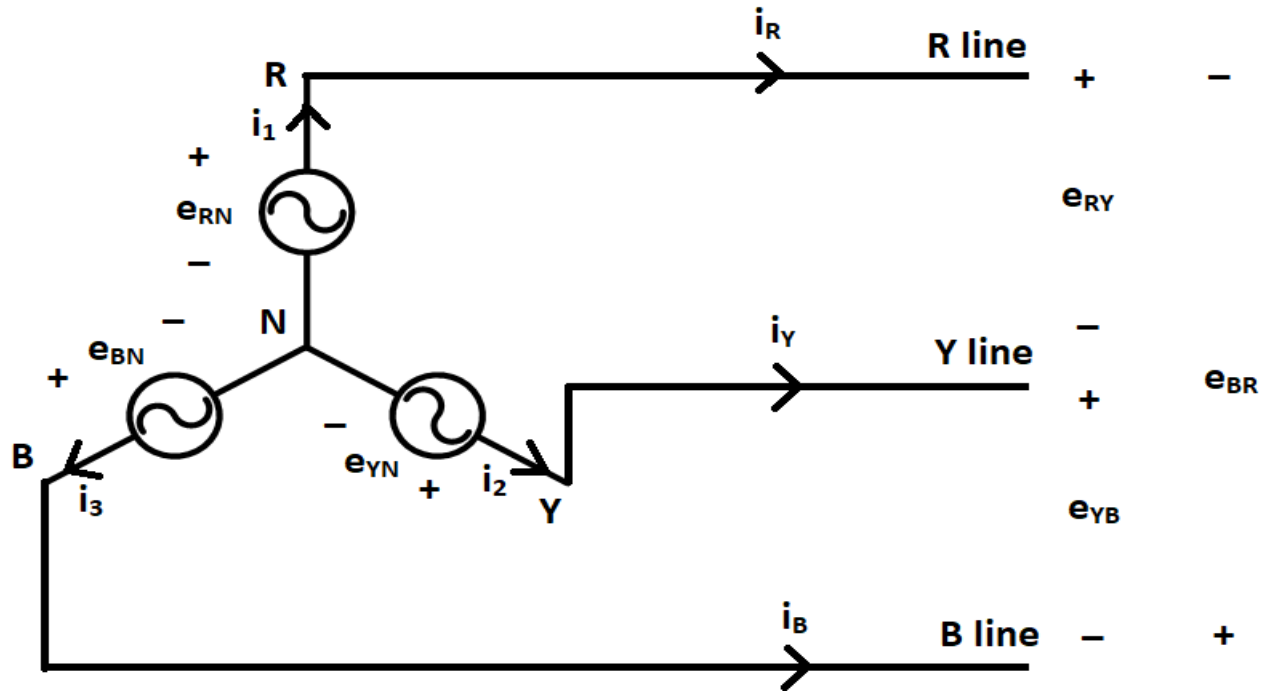
## Relation between Line & Phase voltages – Balanced Star System



By KVL in the path RYNR,  $-e_{RY} - e_{YN} + e_{RN} = 0$

Hence,  $e_{RY} = e_{RN} - e_{YN}$

### Relation between Line & Phase voltages – Balanced Star System

---

$$\overline{E_{RY}} = \overline{E_{RN}} - \overline{E_{YN}}$$

$$\overline{E_{RN}} = \frac{E_m}{\sqrt{2}} \angle 0^\circ = E_{ph} \angle 0^\circ$$

where,  $E_{ph}$  is the RMS value of phase voltage.

$$\overline{E_{YN}} = \frac{E_m}{\sqrt{2}} \angle -120^\circ = E_{ph} \angle -120^\circ$$

$$\overline{E_{BN}} = \frac{E_m}{\sqrt{2}} \angle -240^\circ = E_{ph} \angle -240^\circ$$

$$\begin{aligned}\overline{E_{RY}} &= E_{ph} \angle 0^\circ - E_{ph} \angle -120^\circ \\ &= E_{ph} (1 - (\cos 120^\circ - j \sin 120^\circ)) \\ &= E_{ph} \left( \frac{3}{2} + j \frac{\sqrt{3}}{2} \right)\end{aligned}$$

$$= \sqrt{3}E_{ph}(\cos 30^\circ + j\sin 30^\circ)$$

$$= \sqrt{3}E_{ph}\angle 30^\circ$$

$$\overline{E_{YB}} = \overline{E_{YN}} - \overline{E_{BN}} = \sqrt{3}E_{ph}\angle -90^\circ$$

$$\overline{E_{BR}} = \overline{E_{BN}} - \overline{E_{RN}} = \sqrt{3}E_{ph}\angle -210^\circ$$


Thus, in a balanced star connected three phase system,

- (i) Magnitude (RMS value) of Line Voltage =  $\sqrt{3} \times (\text{Magnitude of Phase Voltage})$
- (ii) Each line voltage leads the corresponding phase voltage by  $30^\circ$




# ELEMENTS OF ELECTRICAL ENGINEERING
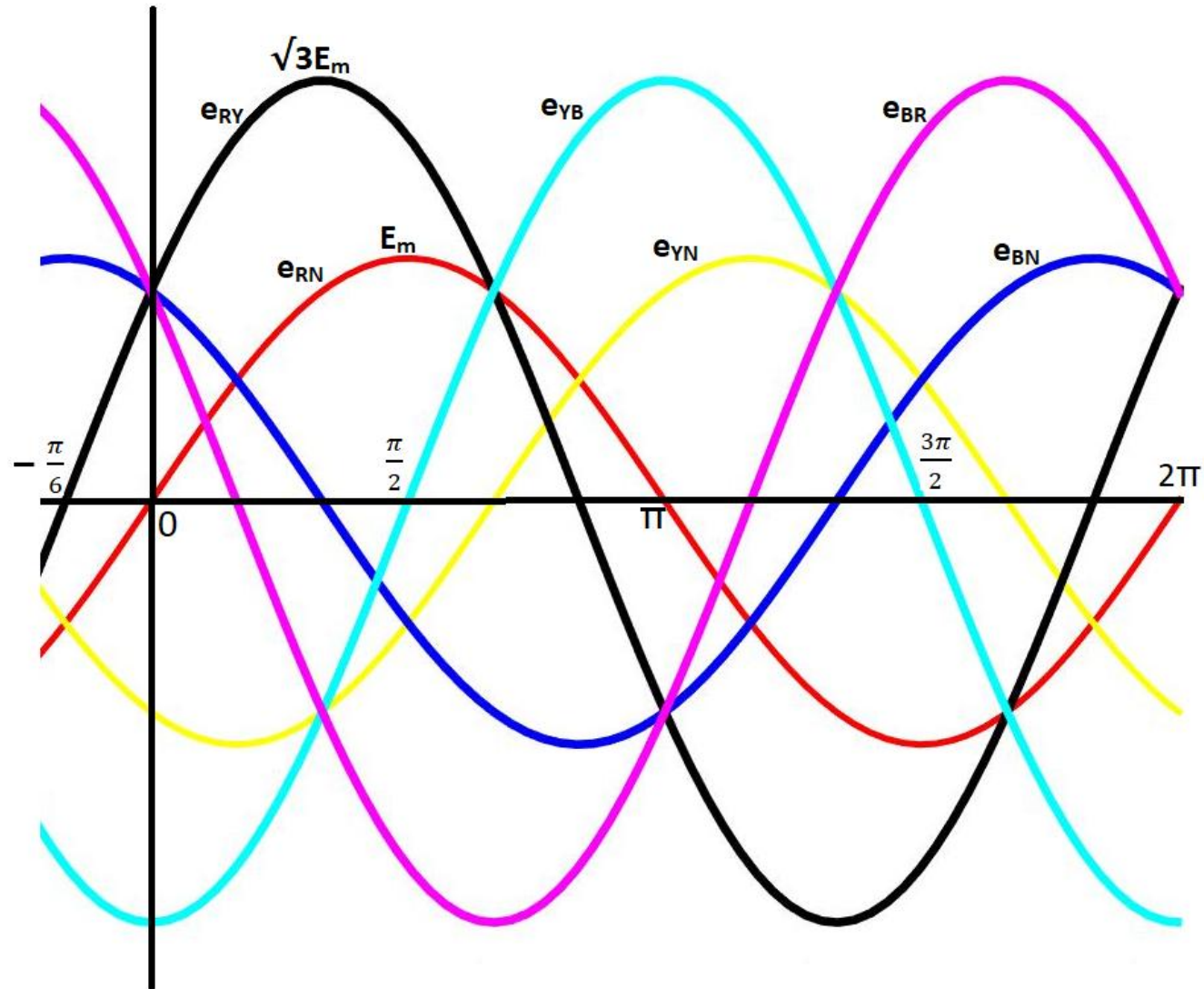
## Balanced Star System – Line and Phase Voltage Waveforms


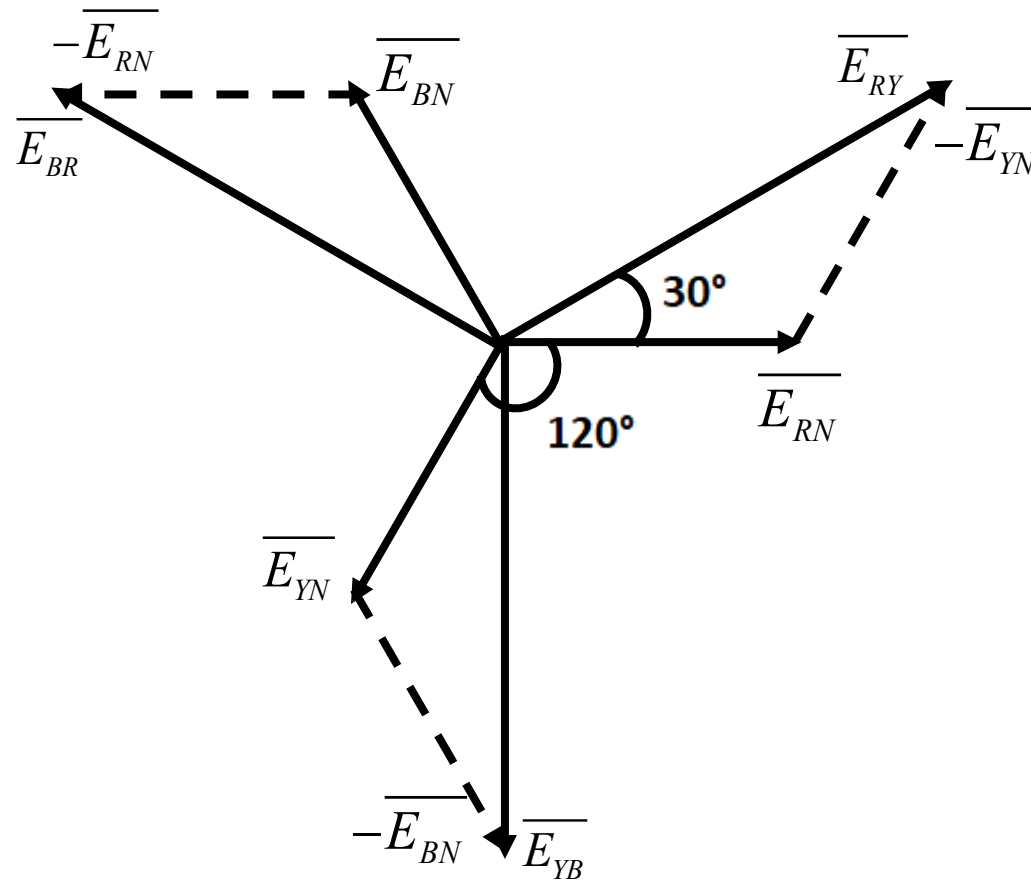
$$\overline{E_{RY}} = \overline{E_{RN}} - \overline{E_{YN}}$$



### **Question:**

**A balanced 3 phase load consists of three coils, each of  $4\Omega$  resistance and  $0.02H$  inductance. Determine the total active and reactive power when the coils are connected in star, if the supply voltage is  $400V$ ,  $50\text{ Hz}$ .**

### **Solution :**

### **Note:**

In three phase systems, by default, the voltages and currents given are line voltage and line current respectively.


Similarly, power given is three phase power by default.

# ELEMENTS OF ELECTRICAL ENGINEERING
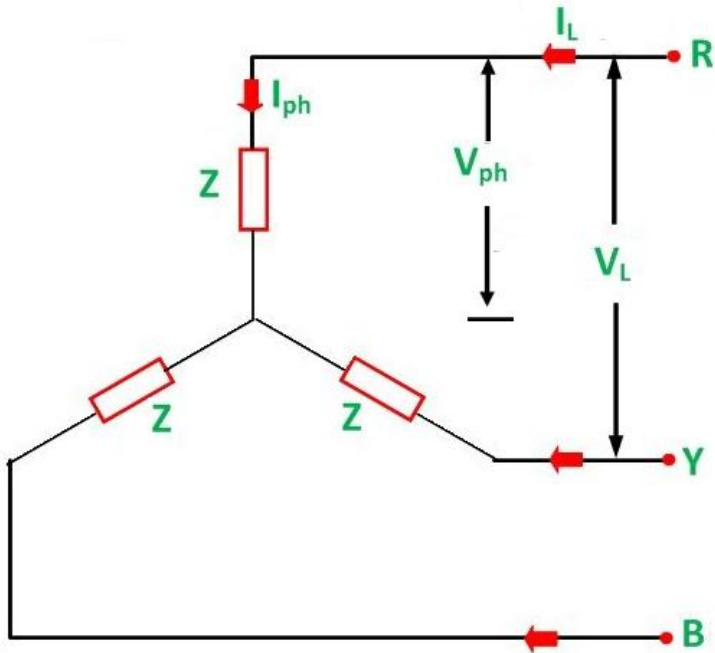
## Numerical Example 1 (contd..)

Given Data:

Line voltage,  $V_L = 400\text{V}$  ;  $f = 50\text{Hz}$



### Given Data:

Line voltage,  $V_L = 400\text{V}$  ;  $f = 50\text{Hz}$

Resistance per phase,  $R = 4\Omega$

Inductance per phase,  $L = 0.02\text{H}$

## Numerical Example 1 (contd..)

---

### Calculations:

Inductive reactance per phase,  $X_L = 2\pi fL = 6.28\Omega$

Impedance per phase,  $Z = R + jX_L = (4 + j6.28)\Omega$

Hence,  $|Z| = 7.45\Omega$  ; Phase Angle,  $\phi = 57.5^\circ$

Since star connected system,

Phase voltage,  $V_{ph} = \frac{V_L}{\sqrt{3}} = 230.94V$

Hence, Phase current,  $I_{ph} = \frac{V_{Ph}}{|Z|} = 31A$

Therefore, Line current,  $I_L = I_{ph} = 31A$

Three phase Active Power,

$$P_{3\text{-phase}} = 3 * P_{1\text{-phase}} = 3 * V_{ph} * I_{ph} * \cos(\phi) = 11.54 \text{KW}$$

$$\text{Alternatively, } P_{3\text{-phase}} = \sqrt{3} * V_L * I_L * \cos(\phi) = 11.54 \text{KW}$$

$$\text{Alternatively, } P_{3\text{-phase}} = 3 * I_{ph}^2 * R = 11.54 \text{KW}$$

Similarly, Three phase Reactive Power,

$$Q_{3\text{-phase}} = 3 * Q_{1\text{-phase}} = 3 * V_{ph} * I_{ph} * \sin(\phi) = 18.11 \text{KVAR}$$

$$\text{Alternatively, } Q_{3\text{-phase}} = \sqrt{3} * V_L * I_L * \sin(\phi) = 18.11 \text{KVAR}$$

$$\text{Alternatively, } Q_{3\text{-phase}} = 3 * I_{ph}^2 * X_L = 18.11 \text{KVAR}$$

### Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1<sup>st</sup>Edition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2<sup>nd</sup>Edition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

### Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10<sup>th</sup> Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12<sup>th</sup> Edition, Pearson Education, 2016.



**THANK YOU**

---

**Jyothi T N**

Department of Electrical & Electronics Engineering

**[jyothitn@pes.edu](mailto:jyothitn@pes.edu)**