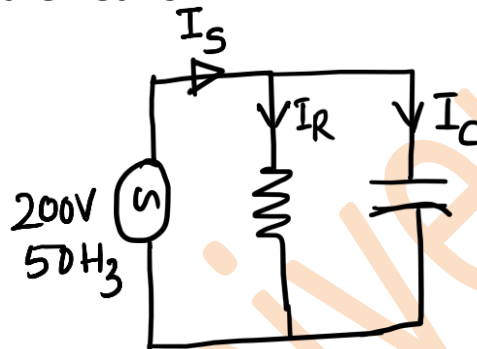


## Lecture -31

1. A parallel RC Circuit is connected across 200V, 50 Hz supply. If the supply current and current in resistor are 10A & 6A respectively, determine

- Current in capacitor
- Values of R & C
- Active, Reactive and Apparent Powers supplied by the source.
- Powerfactor of the network

Solution:



Supply current  $I_s = 10A$

Current in Resistor  $I_R = 6A$

$$I_s^2 = I_R^2 + I_C^2$$

$$\text{Capacitor current } I_C = \sqrt{I_s^2 - I_R^2}$$

$$= \sqrt{10^2 - 6^2}$$

$$I_C = 8A$$

$$\text{Resistance } R = \frac{V}{I_R} = \frac{200}{6} = 33.33\Omega$$

$$\text{Reactance } X_C = \frac{V}{I_C} = \frac{200}{8} = 25\Omega$$

$$\text{Capacitor } C = \frac{1}{2\pi f X_C} = 127 \mu\text{F}$$

$$\text{iii) Active power } P = \frac{V^2}{R} = \frac{(200)^2}{33.33} = 1200.12 \text{ W}$$

$$\text{Reactive power } Q = -\frac{V^2}{X_C} = \frac{(200)^2}{25} = -1600 \text{ VAR}$$

$$\begin{aligned} \text{Apparent power } S &= \sqrt{P^2 + Q^2} \\ &= 2000.07 \text{ VA} \end{aligned}$$

$$\begin{aligned} \text{Power factor of the Nhw } \cos \phi &= \frac{P}{S} \\ &= 0.6 \text{ Lead.} \end{aligned}$$