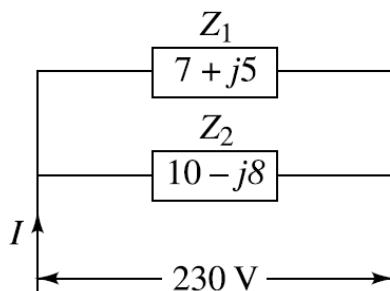


NOTES -Class 31

Numerical Examples on Parallel RLC Circuit:

1. An impedance of $(7 + j5) \Omega$ is connected in parallel with another impedance of $(10 - j8) \Omega$ across a 230-V, 50-Hz supply. Calculate (i) admittance, conductance and susceptance of the combined circuit, and (ii) total current and power factor.



Solution

Data

$$\bar{Z}_1 = (7 + j5) \Omega$$

$$\bar{Z}_2 = (10 - j8) \Omega$$

$$V = 230 \text{ V}$$

$$\bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{7 + j5} = 0.12 \angle -35.54^\circ \text{ S}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{10 - j8} = 0.08 \angle 38.66^\circ \text{ S}$$

$$\begin{aligned} \bar{Y} &= \bar{Y}_1 + \bar{Y}_2 \\ &= 0.12 \angle -35.54^\circ + 0.08 \angle 38.66^\circ \\ &= 0.16 \angle -7.04^\circ \text{ S} \\ &= 0.16 - j0.02 \text{ S} \end{aligned}$$

Admittance

$$Y = 0.16 \text{ S}$$

Conductance

$$G = 0.16 \text{ S}$$

Susceptance

$$B = 0.02 \text{ S}$$

$$\begin{aligned} \bar{I} &= \bar{V} \cdot \bar{Y} \\ &= (230 \angle 0^\circ) (0.16 \angle -7.04^\circ) = 36.8 \angle -7.04^\circ \text{ A} \end{aligned}$$

$$I = 36.8 \text{ A}$$

$$\text{pf} = \cos \phi = \cos (7.04^\circ) = 0.99 \text{ (lagging)}$$

Unit II : Single Phase AC Circuits
