

## Unit I: Assessment: Q & A (Selected)

### Lecture 23

1. A Capacitor of Capacitance  $100\mu\text{F}$  is connected across an AC voltage source  $100\sin(100\pi t)$  V. Determine
  - i) Capacitive Reactance
  - ii) Impedance
  - iii) Instantaneous expression for the current

Also, draw the phasor diagram.

#### SOLUTION:

Given,  $V(t) = 100\sin(100\pi t)$  V

Hence,  $\omega = 100\pi$  rad/s

i) Capacitive Reactance,  $X_c = \frac{1}{\omega C} = 31.83\Omega$

ii) Impedance,  $Z = -jX_c = -j31.83\Omega$

iii) Instantaneous current,  $i(t) = V_m \omega C \sin(\omega t + 90^\circ)$  A  
 $= 3.14\sin(\omega t + 90^\circ)$  A

#### Phasor Diagram:

