

## Unit I: Assessment: Assignments

### Assignment – Lecture 15

1. Using Thevenin's Theorem, find the magnitude and direction of current in the branch BD in the network shown

