

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N
Prof. Vadhiraj K P P
Prof. Kruthika N
Prof. Suma S
Prof. Pushpa K R
Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L
Prof. Dhanashree G Bhate
Dr. Renuka R Kajur
Prof. Rajesh Chandrashekar
Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING (UE25EE141A/B)

NUMERICAL EXAMPLES ON POWER FACTOR IMPROVEMENT

Jyothi T N

Department of Electrical & Electronics Engineering


Numerical Example 1

Question:

The load connected across an AC supply consists of a heating load of 15KW, a motor load of 40KVA at 0.6 lag and a load of 20KW at 0.8 lag. Calculate the total power drawn from the supply in (KW and KVA) and its power factor. What would be the KVAR rating of a capacitor to bring the power factor to unity and how must the capacitor be connected?

Numerical Example 1

Solution:

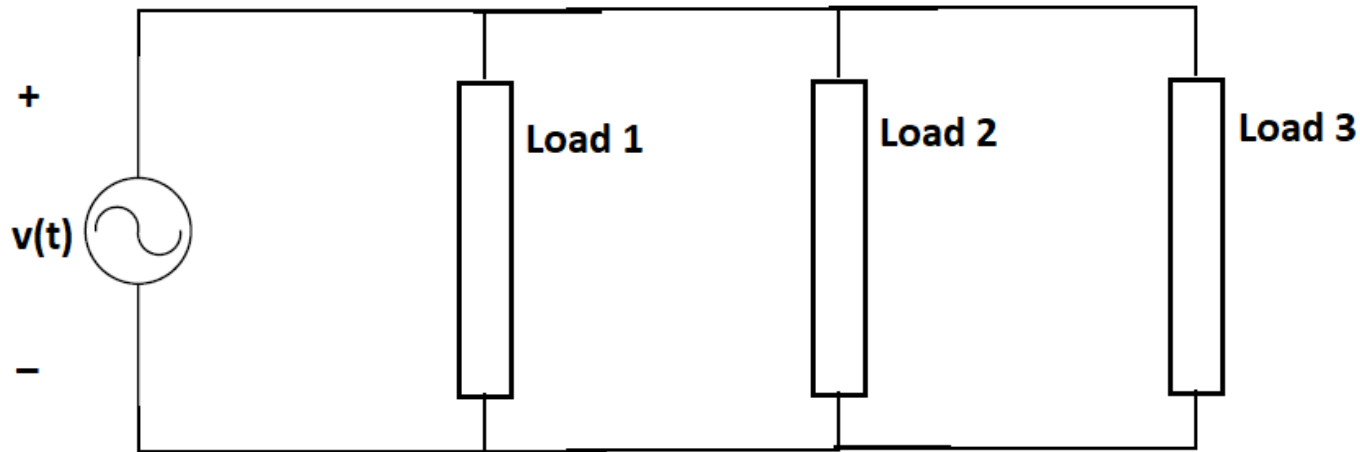

Load 1 : Heating Load \Rightarrow Resistive $\Rightarrow \cos\phi_1 = 1$


$P_1 = 15\text{KW}$ (given)

$Q_1 = 0$

$S_1 = \sqrt{P_1^2 + Q_1^2} = 15\text{KVA}$

Numerical Example 1

Solution:

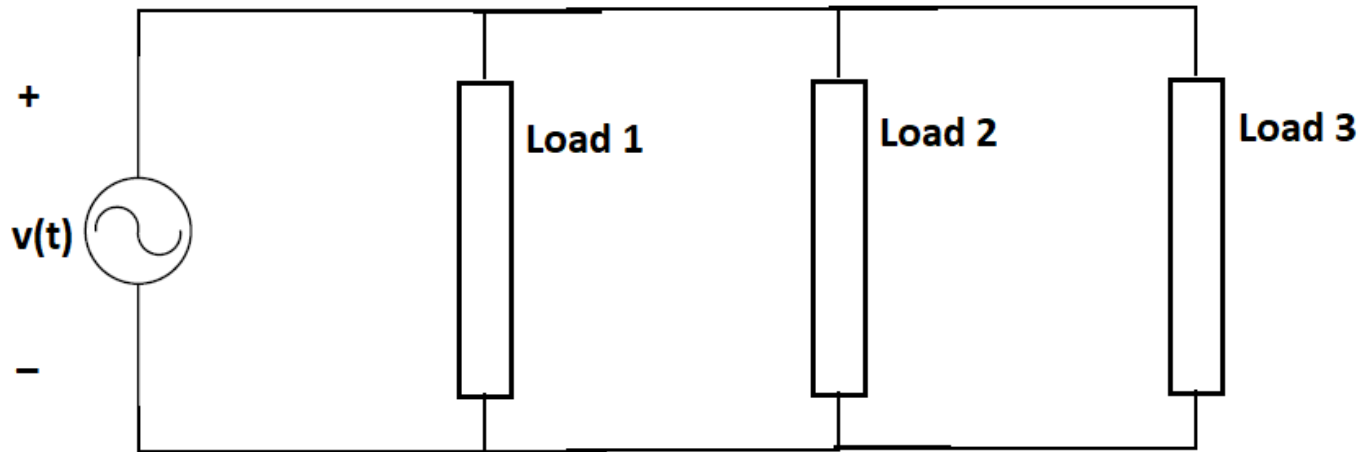

Load 2 : Motor Load \Rightarrow Inductive


$S_2 = 40\text{KVA}$ & $\cos\phi_2 = 0.6$ Lag (given)

$P_2 = S_2 \cos\phi_2 = 24\text{KW}$

$Q_2 = \sqrt{S_2^2 - P_2^2} = 32\text{KVAR}$

Numerical Example 1

Solution:

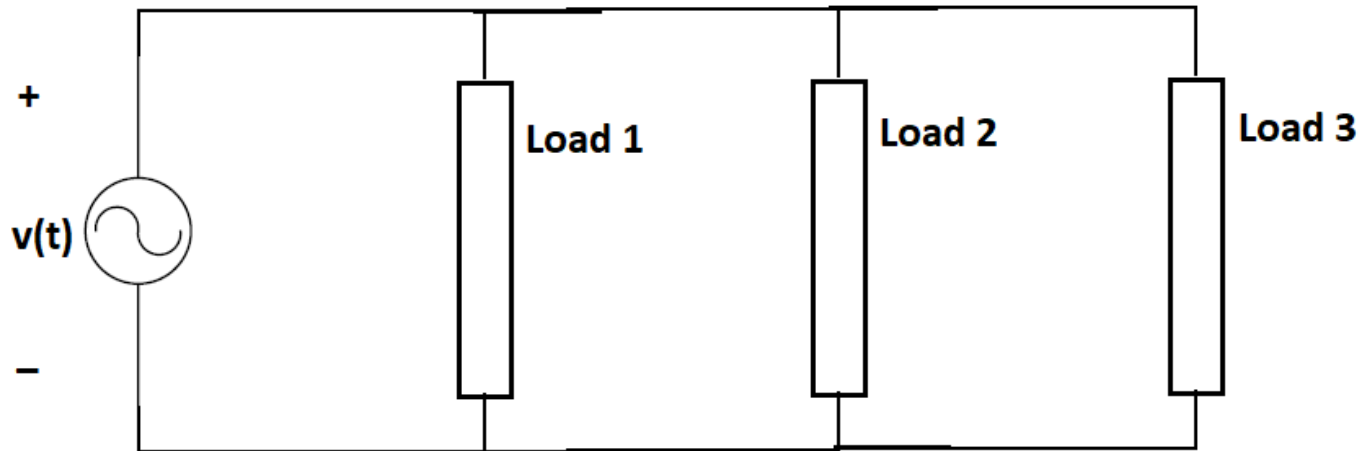

Load 3 : Inductive Load


$P_3 = 20\text{KW}$ & $\cos\phi_3 = 0.8$ Lag (given)

$$S_3 = \frac{P_3}{\cos\phi_3} = 25\text{KVA}$$

$$Q_3 = \sqrt{S_3^2 - P_3^2} = 15\text{KVAR}$$

Numerical Example 1

Solution:

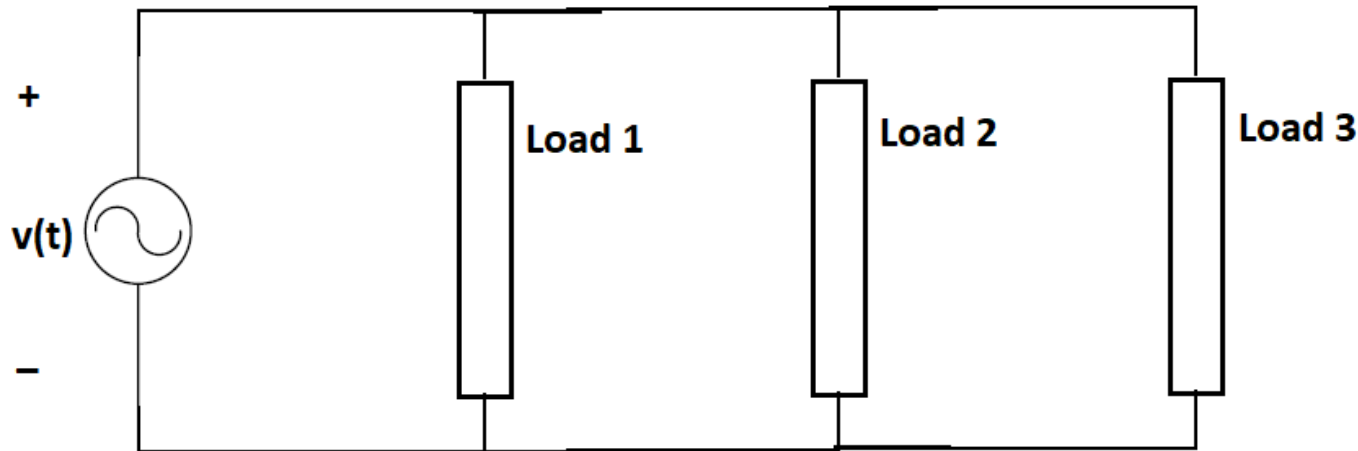

Net Active Power, $P_T = P_1 + P_2 + P_3 = 59\text{KW}$

Net Reactive Power, $Q_T = Q_1 + Q_2 + Q_3 = 47\text{KVAR}$

Net Apparent Power, $S_T = \sqrt{P_T^2 + Q_T^2} = 75.43\text{KVA}$

To make overall power factor unity, net reactive power must be zero. Hence, connect a capacitor of rating 47KVAR in parallel to achieve this.

Numerical Example 2

Question:

The power consumed in the inductive load is 2.5 kW at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.


Solution:

$$P = VI \cos \phi$$

$$I = 15.309 \text{ A}$$

$$\phi = \cos^{-1} 0.71 = 44.76^\circ$$
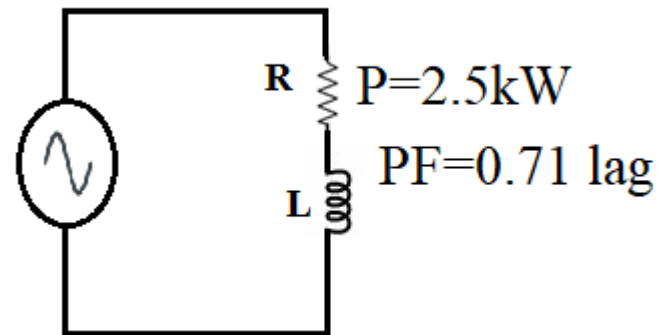
$$\therefore I = 15.309 \angle -44.76^\circ \text{ A}$$



Numerical Example 2

By KCL

$$I_T \angle -30^\circ = (15.309 \angle -44.76^\circ) + (I_C \angle 90^\circ)$$

By equating real parts.

$$I_T \cos 30^\circ = (15.309 \cos 44.76^\circ) + (I_C \cos 90^\circ)$$

$$I_T = 12.55A$$


$$I_C = I_T - I_L \quad (\text{phasor sum})$$

$$I_C = (12.55 \angle -30^\circ) - (15.309 \angle -44.76^\circ)$$

$$\therefore I_C = 4.504 \angle 90^\circ$$

$$\therefore X_C = \frac{V_C}{I_C} = \frac{230}{4.504} = 51.065 \Omega$$
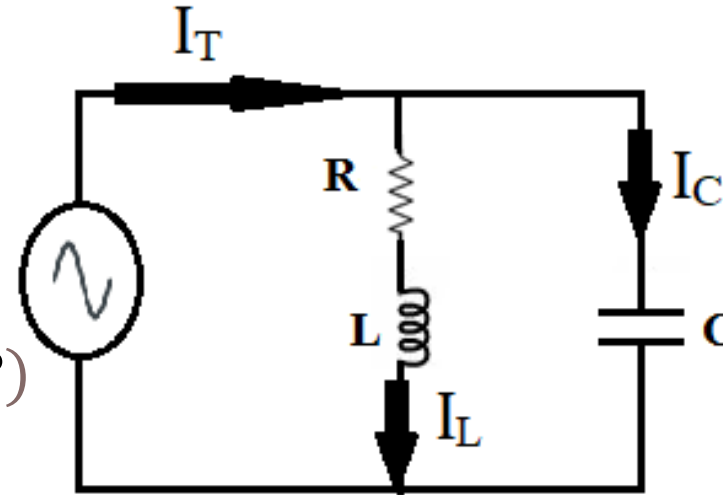
$$C = \frac{1}{2\pi f X_C} = 62.33 \mu f$$



Text Book:

1. **“Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017**
2. **“Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019**
3. **“Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014**

Reference Books:

1. **“Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023**
2. **“Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.**



THANK YOU

Jyothi T.N

Department of Electrical & Electronics Engineering
jyothitn@pes.edu