

### Unit III: Assessment: Assignments

---

#### Assignment Class 48

1. The power input to a three phase load is measured by two wattmeters both of which indicate 50kW. If the power factor of the load be changed to 0.866 lead, determine the readings of the two wattmeters the total input power remaining the same.