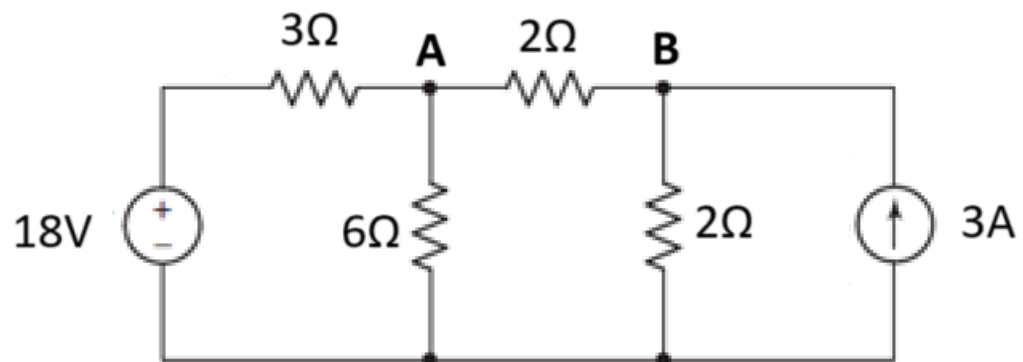


## Unit I: Assessment Question Bank

### Lecture 6

1. Apply Source Transformation to find the current flowing through branch AB in the given network.



(Ans : 1A)

PESU