

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING


Numerical Examples on Superposition Theorem

Jyothi T N

Department of Electrical & Electronics Engineering

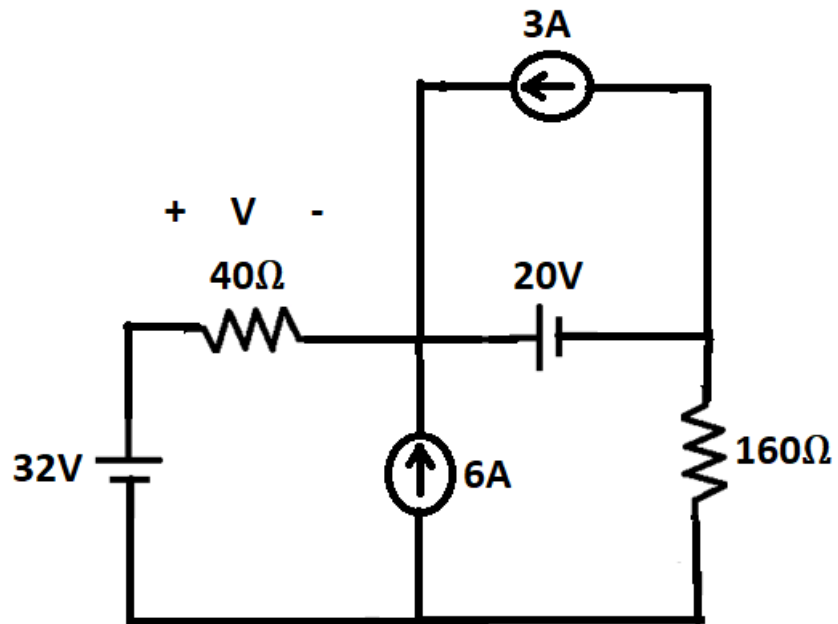Question:

Obtain voltage 'V' using Superposition Theorem.




ELEMENTS OF ELECTRICAL ENGINEERING

Numerical Example 1

$$V' = 32V * \frac{40\Omega}{200\Omega} = 6.4V$$

Solution :



Considering 32V source alone,

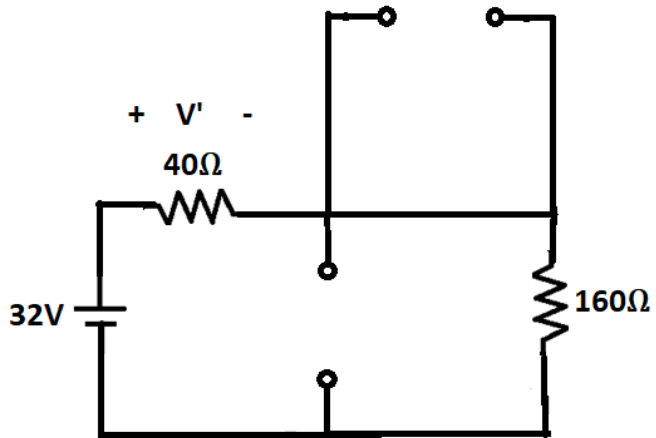

$$V' = 32V * \frac{40\Omega}{200\Omega} = 6.4V$$

Solution (Continued..) :

Considering 6A source alone,

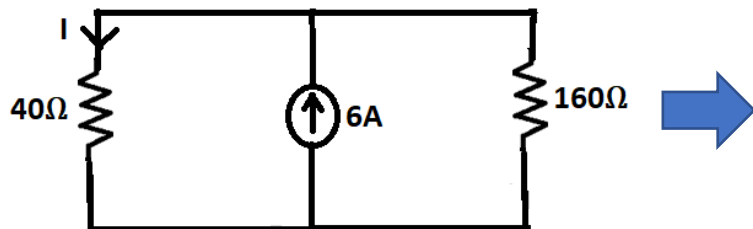
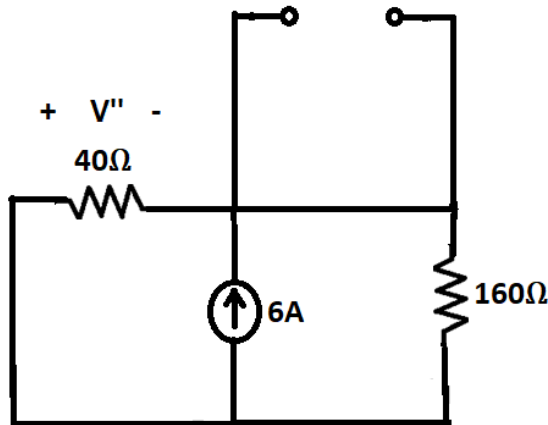


$$I = 6A * \frac{160\Omega}{200\Omega} = 4.8A$$

$$V'' = -4.8A * 40\Omega = -192V$$

Solution (Continued..) :

Considering 20V source alone,

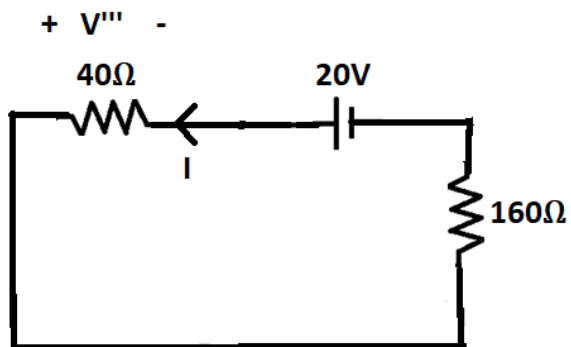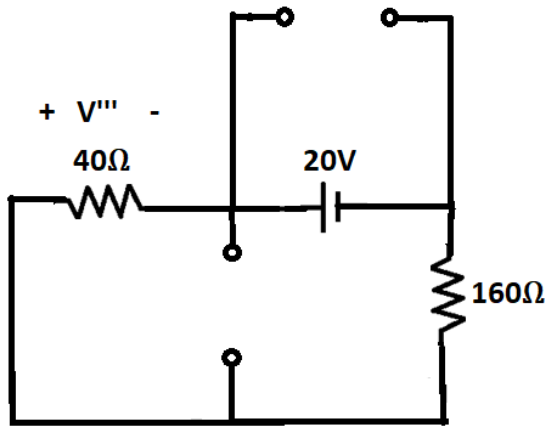


$$I = \frac{20V}{200\Omega} = 0.1A$$

$$V''' = -0.1A * 40\Omega = -4V$$

Solution (Continued..) :

Considering 3A source alone,

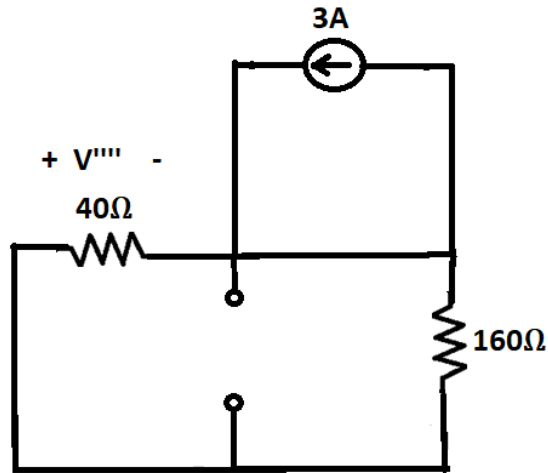


$$V'''' = 0$$

By Superposition Theorem,


$$V = V' + V'' + V''' + V'''' = -189.6V$$

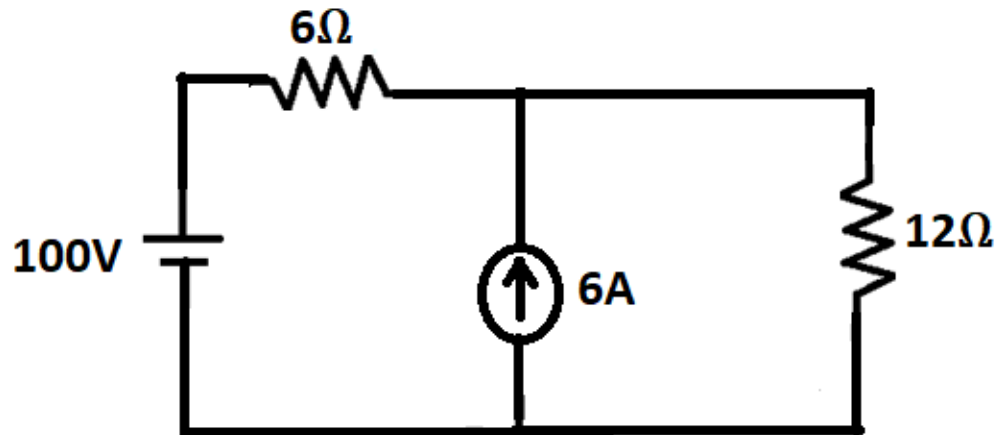Question:

Find the power absorbed by 12Ω resistor using Superposition Theorem.



Solution :

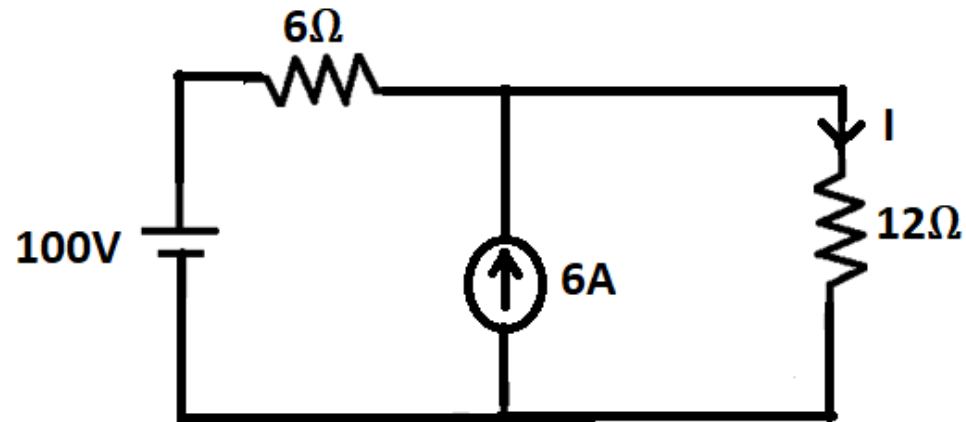


Let us consider individual current & Power responses due to 100V source acting alone as I' & P'

Let us consider individual current & Power responses due to 6A source acting alone as I'' & P''

Solution (Continued..) :


Considering 100V source alone,

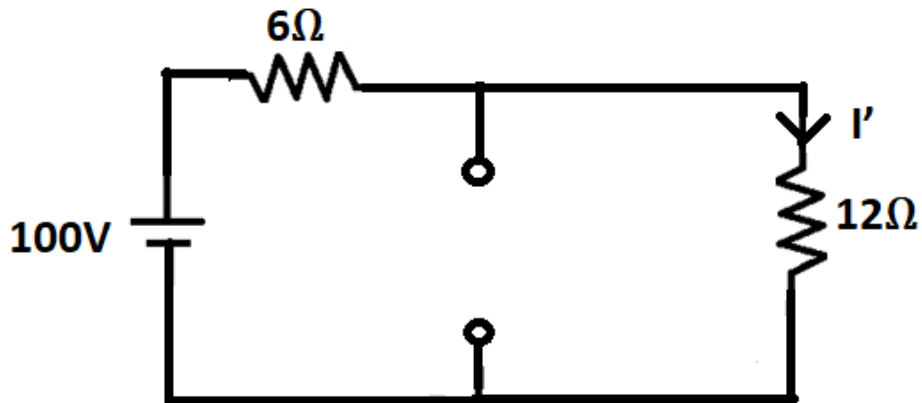

$$I' = \frac{100V}{18\Omega} = 5.56A \quad \& \quad P' = (I')^2 * 12 = 370.96W$$

Solution (Continued..) :

Considering 6A source alone,

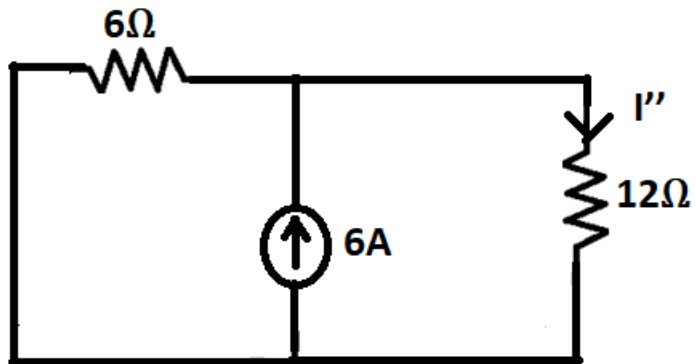

$$I'' = 6A * \frac{6\Omega}{18\Omega} = 2A \quad \& \quad P'' = (I'')^2 * 12 = 48W$$

Solution (Continued..) :

By Superposition, current in 12Ω resistor = $I = I' + I'' = 7.56A$


Hence, Power absorbed by 12Ω resistor = $I^2 * 12 = 685.84W$

Adding the individual Power responses, $P' + P'' = 418.96W$, which is not equal to the actual power absorbed.

Hence, individual power responses cannot be superposed to get total power because power is a quadratic term.

Thus, to get total power response, apply superposition principle to get total current or total voltage & using that find the power.

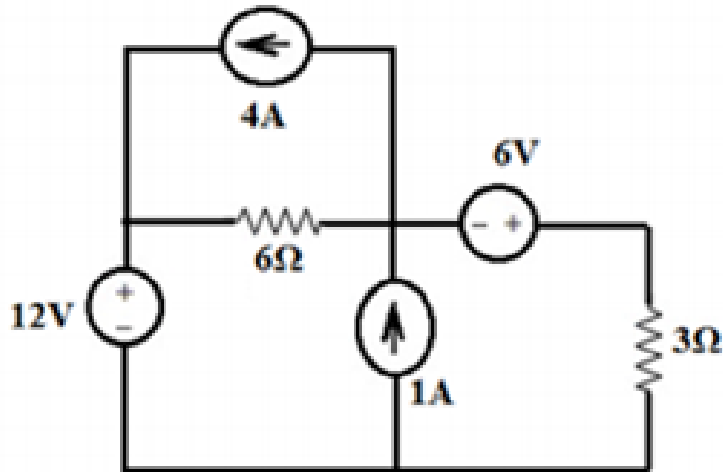Find the current through 3Ω resistor in the circuit shown below using Superposition Theorem



Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu