

## Unit I: Assessment: Assignments

### Assignment – Lecture 11

1. Why can't we apply KVL in a Mesh containing current sources?
2. Find current in  $5\Omega$  resistor using Mesh Analysis.

