

ELEMENTS OF ELECTRICAL ENGINEERING

Course Code : UE25EE141A/B



FACULTY CONTRIBUTED:

Department of EEE, RR Campus

Prof . Jyothi T N

Prof. Vadhiraj K P P

Prof. Kruthika N

Prof. Suma S

Prof. Pushpa K R

Prof. Sangeeta Modi

Department of ECE, EC Campus

Prof. Lokesh L

Prof. Dhanashree G Bhate

Dr. Renuka R Kajur

Prof. Rajesh Chandrashekar

Prof. Sangam Kumar G H

ELEMENTS OF ELECTRICAL ENGINEERING




Concept of ideal sources, Voltage and Current Division Rules


Jyothi T N

Department of Electrical & Electronics Engineering

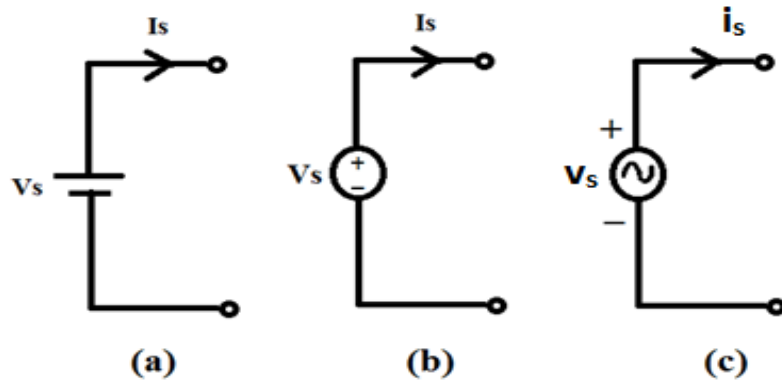Its terminal voltage is independent of current flowing through it.




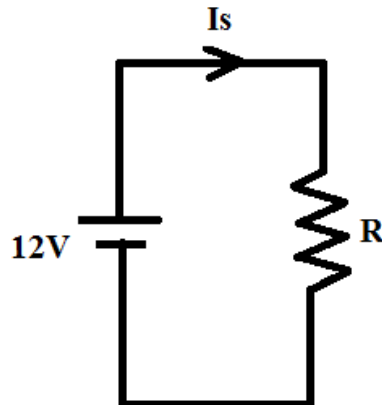The current delivered by it depends on the circuit to which it is connected.




When $R = 10\Omega$, $I_s = 1.2A$

When $R = 1\Omega$, $I_s = 12A$

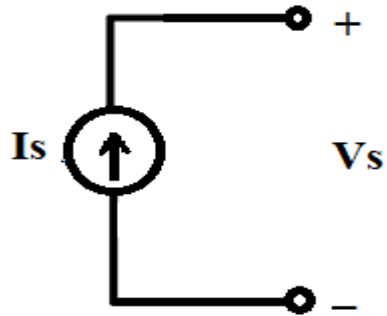

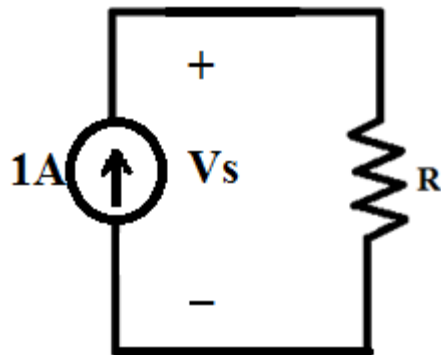
The voltage across it depends on the circuit to which it is connected.



When $R = 1\Omega$, $V_s = 1V$

When $R = 10\Omega$, $V_s = 10V$

It is applicable to Series Networks

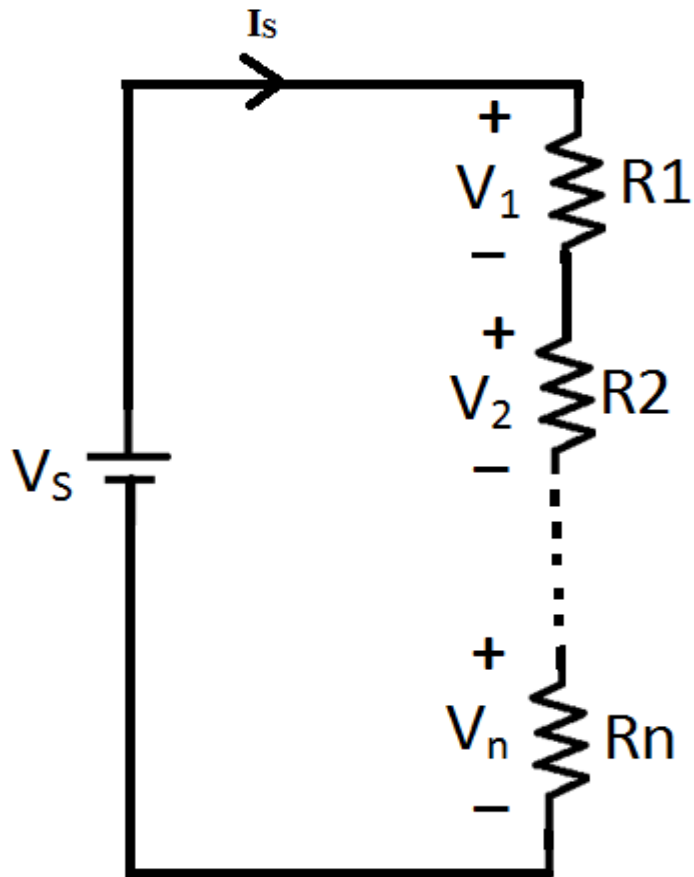

$$V_1 = I_S * R_1$$

$$V_2 = I_S * R_2$$

.


.

.

$$V_n = I_S * R_n$$

By KVL,

$$V_S = V_1 + V_2 + \dots + V_n$$

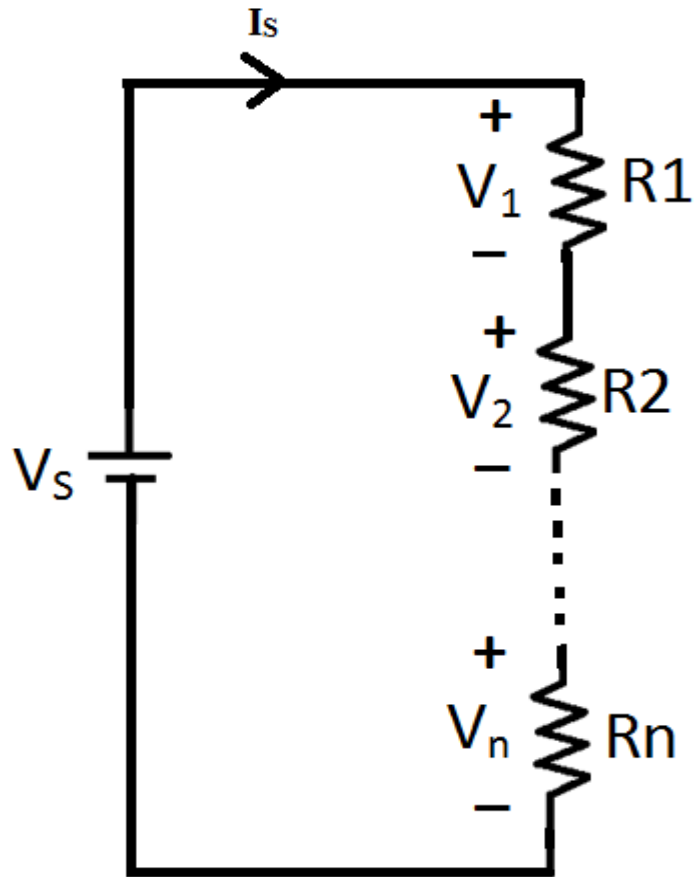

$$\text{Hence, } I_S = \frac{V_S}{(R_1 + R_2 + \dots + R_n)}$$


Therefore,

$$V_1 = \frac{V_S * R_1}{(R_1 + R_2 + \dots + R_n)}$$


.

.
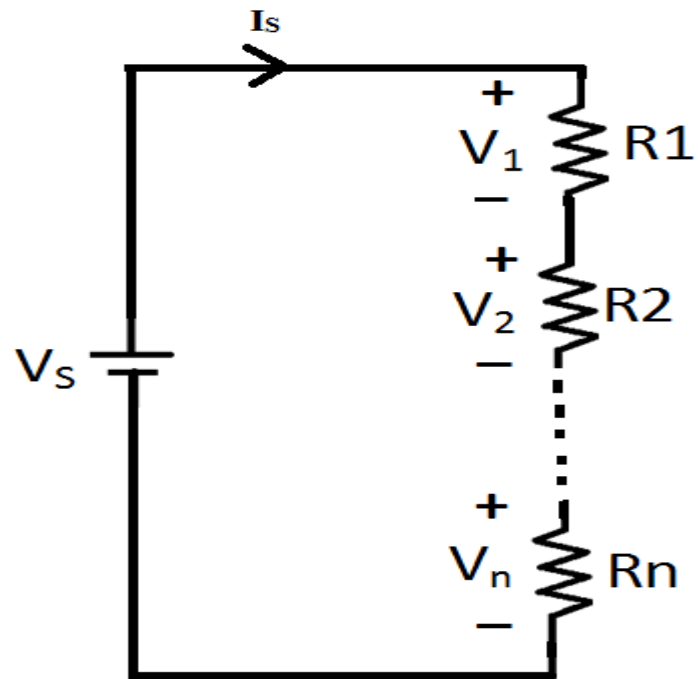
$$V_n = \frac{V_S * R_n}{(R_1 + R_2 + \dots + R_n)}$$



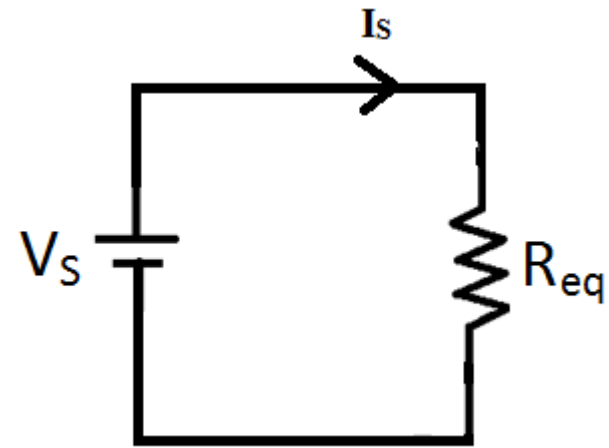
$$I_S = \frac{V_S}{(R_1 + R_2 + \dots + R_n)}$$



$$I_S = \frac{V_S}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

It is applicable to Parallel Networks

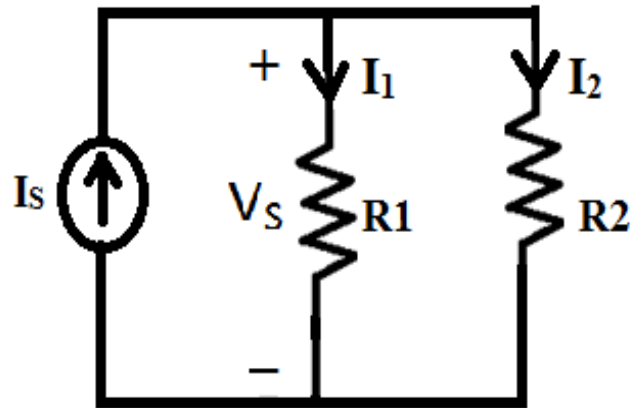


$$I_1 = \frac{V_S}{R_1}$$

$$I_2 = \frac{V_S}{R_2}$$

By KCL,

$$I_S = I_1 + I_2$$

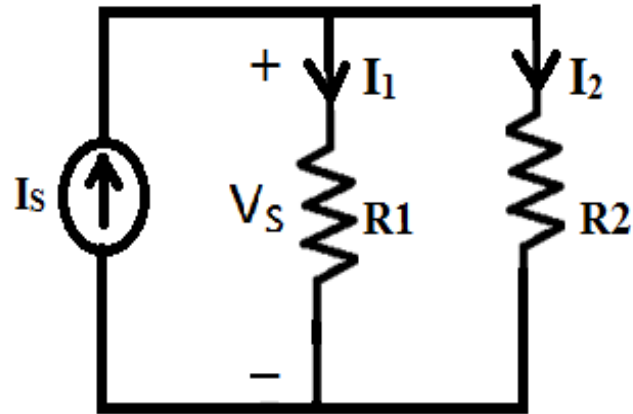
$$I_S = V_S * \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



$$V_s = I_s * \frac{R_1 * R_2}{(R_1 + R_2)}$$

$$I_1 = I_s * \frac{R_2}{(R_1 + R_2)}$$


$$I_2 = I_s * \frac{R_1}{(R_1 + R_2)}$$

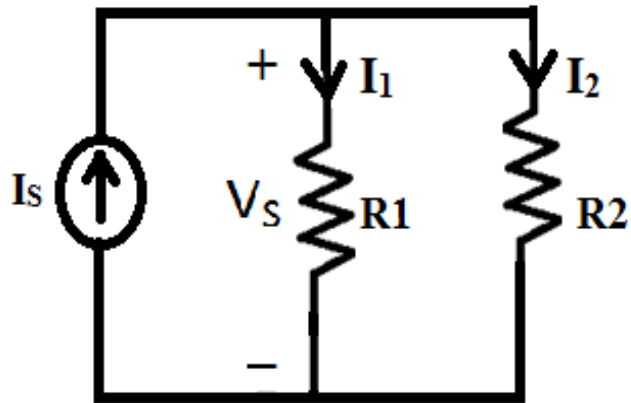

$$\frac{V_S}{I_S} = R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 * R_2}{(R_1 + R_2)}$$


In general, For n Resistors in Parallel,
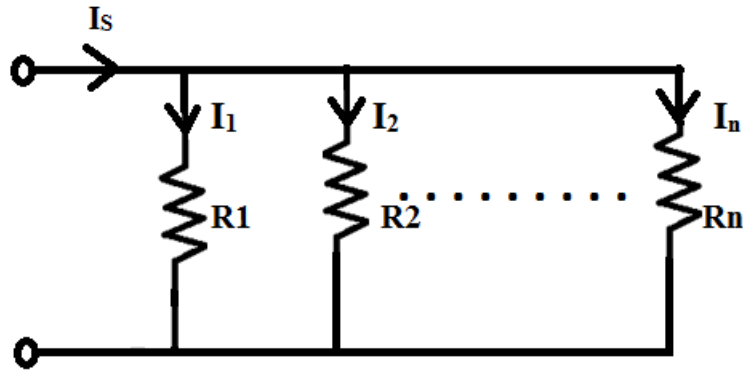
$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$




- Obtain R_{eq} using
$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$
- Find V using
$$V = I_S * R_{eq}$$
- Use Ohm's Law to find branch currents



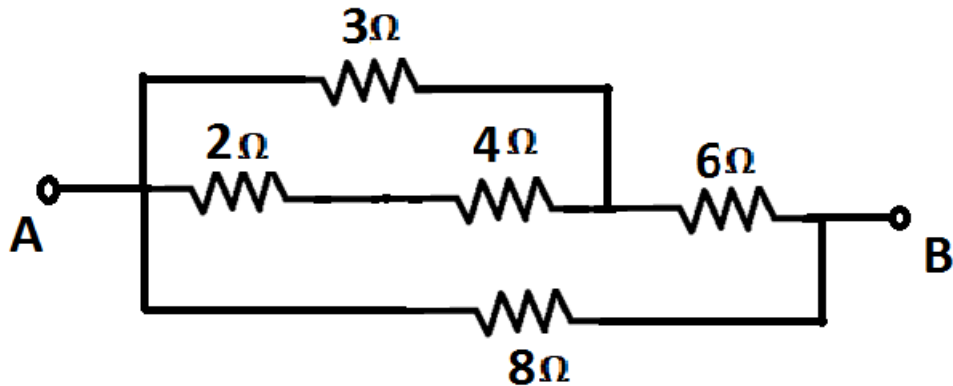
Find the equivalent resistance between A & B



Solution:

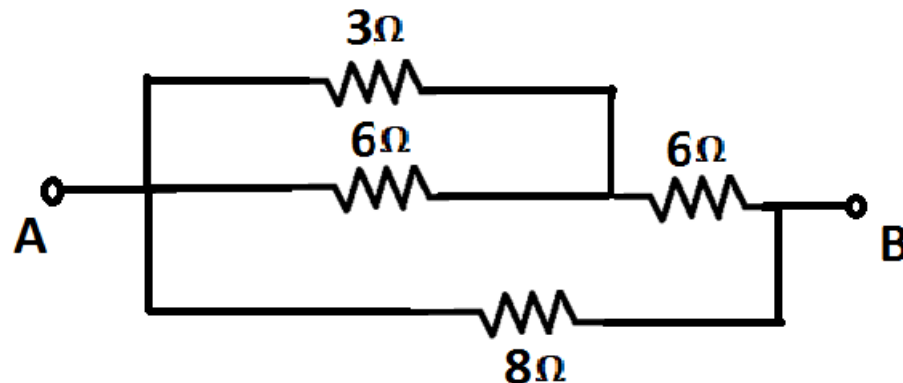

Solution: (Continued..)

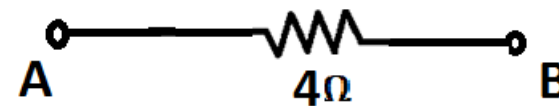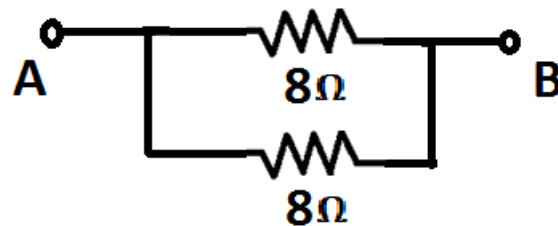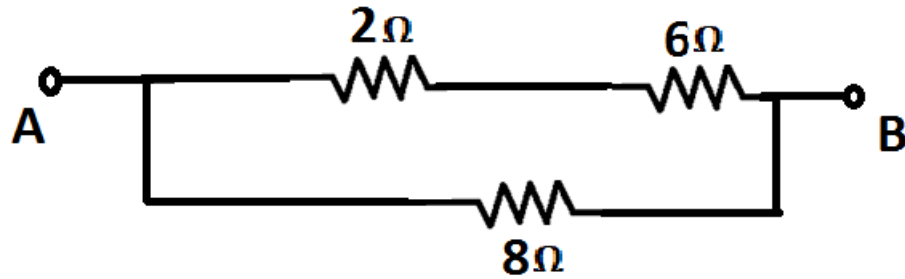

Text Book:

1. “Basic Electrical Engineering” S.K Bhattacharya, 1stEdition Pearson India Education Services Pvt. Ltd., 2017
2. “Basic Electrical Engineering”, D. C. Kulshreshta, 2ndEdition, McGraw-Hill. 2019
3. “Special Electrical Machines” E G Janardanan, PHI Learning Pvt. Ltd., 2014

Reference Books:

1. “Engineering Circuit Analysis” William Hayt, Jack Kemmerly, Jamie Phillips and Steven Durbin, 10th Edition McGraw Hill, 2023
2. “Electrical and Electronic Technology” E. Hughes (Revised by J. Hiley, K. Brown & I.M Smith), 12th Edition, Pearson Education, 2016.



THANK YOU

Jyothi T N

Department of Electrical & Electronics Engineering

jyothitn@pes.edu